

ANALOG INTEGRATED CIRCUIT DESIGN

David Johns

Ken Martin

University of Toronto



John Wiley & Sons, Inc.

Contents

CHAPTER 1	INTEGRATED-CIRCUIT DEVICES AND MODELING	1
1.1	Semiconductors and pn Junctions	1
1.2	MOS Transistors	16
1.3	Advanced MOS Modelling	39
1.4	Bipolar-Junction Transistors	42
1.5	Device Model Summary	56
1.6	SPICE-Modelling Parameters	61
1.7	Appendix	65
1.8	References	78
1.9	Problems	78
CHAPTER 2	PROCESSING AND LAYOUT	82
2.1	CMOS Processing	82
2.2	Bipolar Processing	95
2.3	CMOS Layout and Design Rules	96
2.4	Analog Layout Considerations	105
2.5	Latch-Up	118
2.6	References	121
2.7	Problems	121
CHAPTER 3	BASIC CURRENT MIRRORS AND SINGLE-STAGE AMPLIFIERS	125
3.1	Simple CMOS Current Mirror	125
3.2	Common-Source Amplifier	128
3.3	Source-Follower or Common-Drain Amplifier	129
3.4	Common-Gate Amplifier	132
3.5	Source-Degenerated Current Mirrors	135
3.6	High-Output-Impedance Current Mirrors	137
3.7	Cascode Gain Stage	140
3.8	MOS Differential Pair and Gain Stage	142
3.9	Bipolar Current Mirrors	146
3.10	Bipolar Gain Stages	149

3.11	Frequency Response	154
3.12	SPICE Simulation Examples	169
3.13	References	176
3.14	Problems	176
CHAPTER 4 NOISE ANALYSIS AND MODELLING		181
4.1	Time-Domain Analysis	181
4.2	Frequency-Domain Analysis	186
4.3	Noise Models for Circuit Elements	196
4.4	Noise Analysis Examples	204
4.5	References	216
4.6	Problems	217
CHAPTER 5 BASIC OPAMP DESIGN AND COMPENSATION		221
5.1	Two-Stage CMOS Opamp	221
5.2	Feedback and Opamp Compensation	232
5.3	SPICE Simulation Examples	251
5.4	References	252
5.5	Problems	253
CHAPTER 6 ADVANCED CURRENT MIRRORS AND OPAMPS		256
6.1	Advanced Current Mirrors	256
6.2	Folded-Cascode Opamp	266
6.3	Current-Mirror Opamp	273
6.4	Linear Settling Time Revisited	278
6.5	Fully Differential Opamps	280
6.6	Common-Mode Feedback Circuits	287
6.7	Current-Feedback Opamps	291
6.8	SPICE Simulation Examples	295
6.9	References	299
6.10	Problems	300
CHAPTER 7 COMPARATORS		304
7.1	Using an Opamp for a Comparator	304
7.2	Charge-Injection Errors	308
7.3	Latched Comparators	317
7.4	Examples of CMOS and BiCMOS Comparators	321
7.5	Examples of Bipolar Comparators	328
7.6	References	330
7.7	Problems	331

CHAPTER 8	SAMPLE AND HOLDS, VOLTAGE REFERENCES, AND TRANSLINEAR CIRCUITS	334
8.1	Performance of Sample-and-Hold Circuits	334
8.2	MOS Sample-and-Hold Basics	336
8.3	Examples of CMOS S/H Circuits	343
8.4	Bipolar and BiCMOS Sample and Holds	349
8.5	Bandgap Voltage Reference Basics	353
8.6	Circuits for Bandgap References	357
8.7	Translinear Gain Cell	364
8.8	Translinear Multiplier	366
8.9	References	368
8.10	Problems	370
CHAPTER 9	DISCRETE-TIME SIGNALS	373
9.1	Overview of Some Signal Spectra	373
9.2	Laplace Transforms of Discrete-Time Signals	374
9.3	z -Transform	377
9.4	Downsampling and Upsampling	379
9.5	Discrete-Time Filters	382
9.6	Sample-and-Hold Response	389
9.7	References	391
9.8	Problems	391
CHAPTER 10	SWITCHED-CAPACITOR CIRCUITS	394
10.1	Basic Building Blocks	394
10.2	Basic Operation and Analysis	398
10.3	First-Order Filters	409
10.4	Biquad Filters	415
10.5	Charge Injection	423
10.6	Switched-Capacitor Gain Circuits	427
10.7	Correlated Double-Sampling Techniques	433
10.8	Other Switched-Capacitor Circuits	434
10.9	References	441
10.10	Problems	443
CHAPTER 11	DATA CONVERTER FUNDAMENTALS	445
11.1	Ideal D/A Converter	445
11.2	Ideal A/D Converter	447
11.3	Quantization Noise	448
11.4	Signed Codes	452

11.5	Performance Limitations	454
11.6	References	461
11.7	Problems	461
CHAPTER 12	NYQUIST-RATE D/A CONVERTERS	463
12.1	Decoder-Based Converters	463
12.2	Binary-Scaled Converters	469
12.3	Thermometer-Code Converters	475
12.4	Hybrid Converters	481
12.5	References	484
12.6	Problems	484
CHAPTER 13	NYQUIST-RATE A/D CONVERTERS	487
13.1	Integrating Converters	487
13.2	Successive-Approximation Converters	492
13.3	Algorithmic (or Cyclic) A/D Converter	504
13.4	Flash (or Parallel) Converters	507
13.5	Two-Step A/D Converters	513
13.6	Interpolating A/D Converters	516
13.7	Folding A/D Converters	519
13.8	Pipelined A/D Converters	523
13.9	Time-Interleaved A/D Converters	526
13.10	References	527
13.11	Problems	528
CHAPTER 14	OVERSAMPLING CONVERTERS	531
14.1	Oversampling without Noise Shaping	531
14.2	Oversampling with Noise Shaping	538
14.3	System Architectures	547
14.4	Digital Decimation Filters	551
14.5	Higher-Order Modulators	555
14.6	Bandpass Oversampling Converters	557
14.7	Practical Considerations	559
14.8	Multi-Bit Oversampling Converters	565
14.9	Third-Order A/D Design Example	568
14.10	References	571
14.11	Problems	572
CHAPTER 15	CONTINUOUS-TIME FILTERS	574
15.1	Introduction to G_m -C Filters	575
15.2	Bipolar Transconductors	584

15.3	CMOS Transconductors Using Triode Transistors	597
15.4	CMOS Transconductors Using Active Transistors	607
15.5	BiCMOS Transconductors	616
15.6	MOSFET-C Filters	620
15.7	Tuning Circuitry	626
15.8	Dynamic Range Performance	635
15.9	References	643
15.10	Problems	645

CHAPTER 16 PHASE-LOCKED LOOPS **648**

16.1	Basic Loop Architecture	648
16.2	PLLs with Charge-Pump Phase Comparators	663
16.3	Voltage-Controlled Oscillators	670
16.4	Computer Simulation of PLLs	680
16.5	Appendix	689
16.6	References	692
16.7	Problems	693

INDEX **696**