

# **Capacitive** Power Transfer for Contactless Charging

Mitchell Kline

Igor Izyumin

Prof. Bernhard Boser

Prof. Seth Sanders



**Why Wireless Power?**



# The Powermat

“...I started to wonder if the **magnet** on the iPhone case was safe in my pocket where I also keep my **credit cards**...

I was told that I should remove my iPhone from the case after charging because [it] was **not intended for daily use.**”

**Thomas Scholle**

**1 star** amazon review

“you'll need to invest **another \$40** per device to get the full functionality as you see it advertised. **Too pricey** for me!”


**J. Lincoln**

**2star** amazon review

# Wireless Power Technology


Close-coupled wireless power transfer

Power Source ))) Load

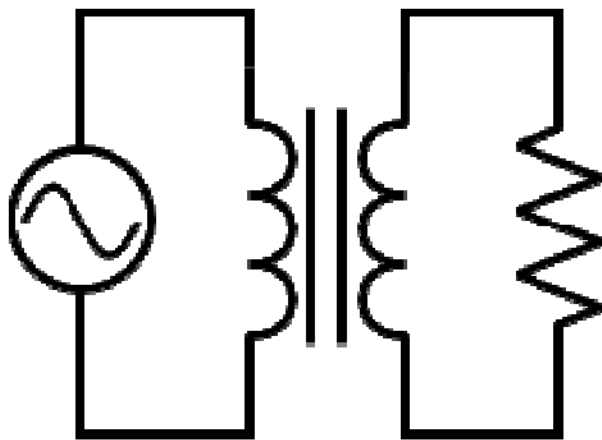

1. Inductive


Power Source ))) Load

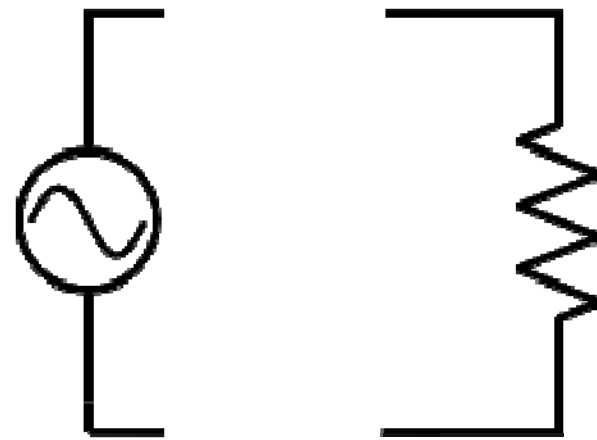

2. Capacitive


# Capacitive Power Transfer System

1

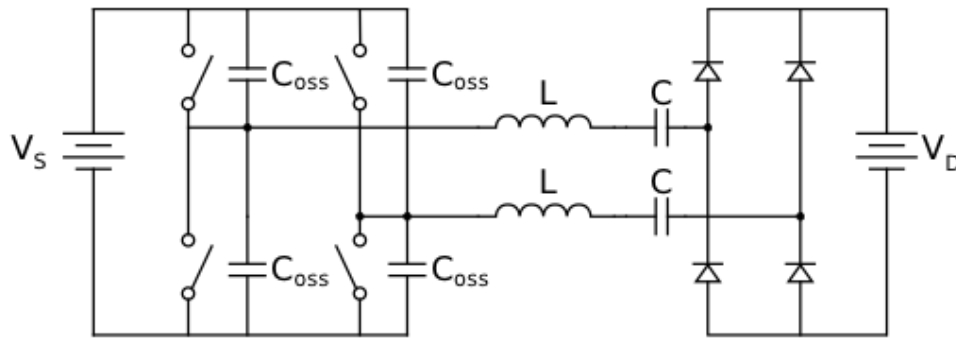

**Powertrain  
optimization**

2

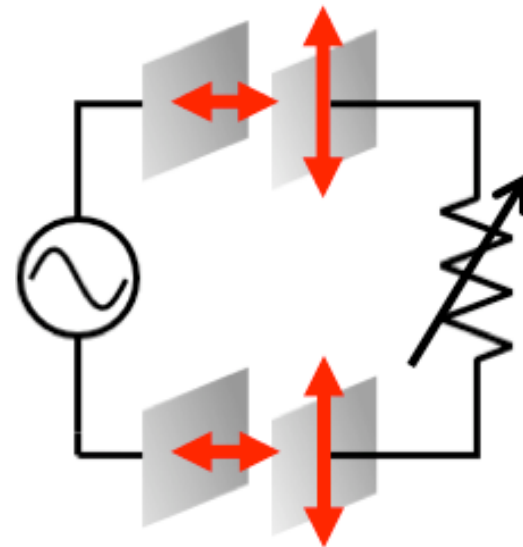


**Alignment and  
load sensitivity**

# Requirements


- 3.5 pF/cm<sup>2</sup> (1/4 mm air gap)  
with ~50 cm<sup>2</sup> gives 150 pF
- Need >2.5 W (USB spec.)



# Prior Art

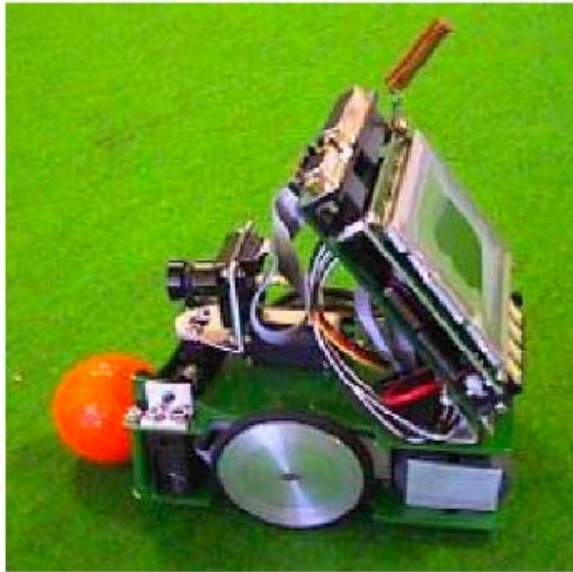


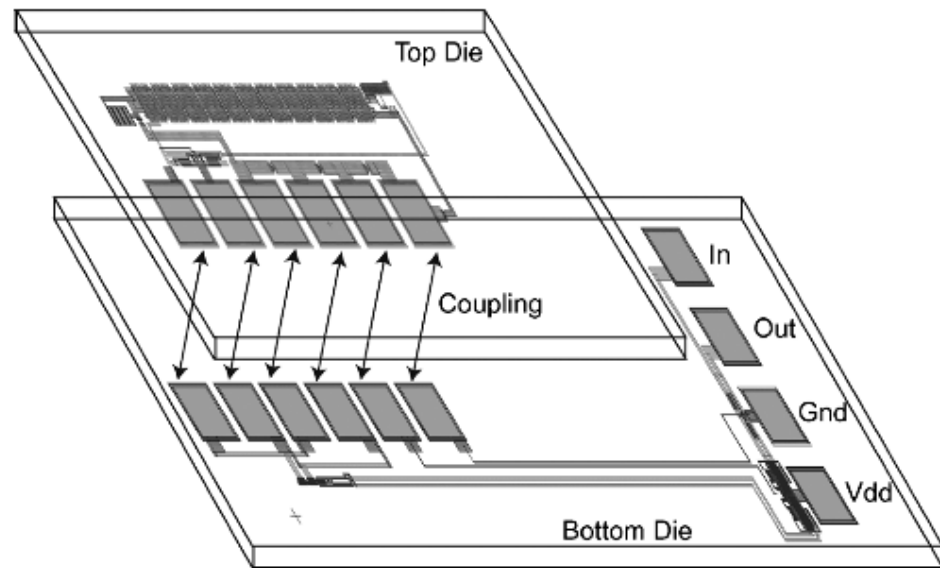A. Hu. 2008.  
Soccer Playing Robot  
**13.9 nF**  
217 kHz  
~40 W?  
44% efficient



E. Culurciello. 2008.  
Inter-chip power transfer  
**10 fF**  
15 MHz  
~100  $\mu$ W?  
~1% efficient?

# Optimization Approach

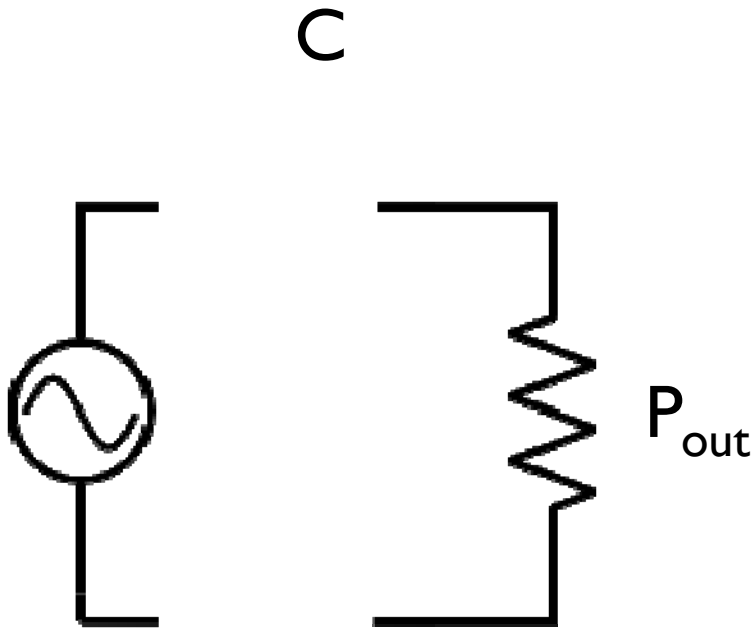


Given  $P_{out}$  and C, how do we maximize the efficiency?

or

What is the minimum required C to achieve a particular  $P_{out}$  and efficiency?

# Powertrain Architecture

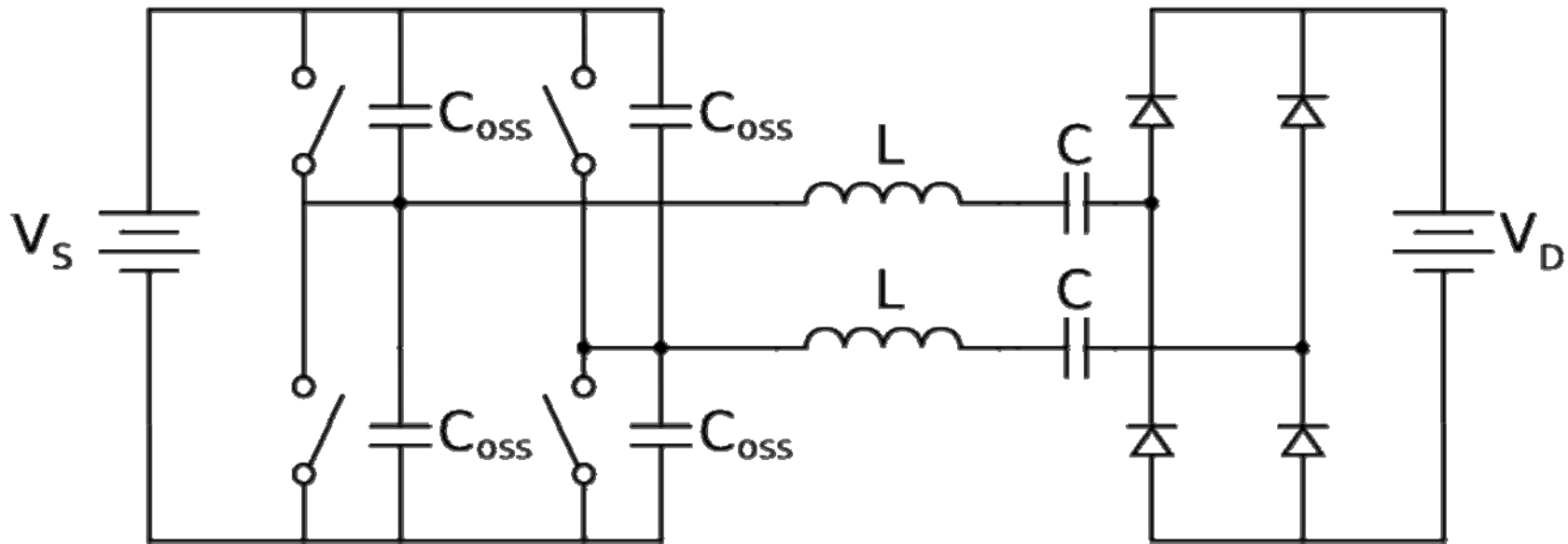

# Efficiency Expression

Minimize:

Increase voltage

Minimize:

Large switch

Small inductor


$$\eta = 1 - \frac{1}{2} \frac{\|i_t\|^2 R_S}{P_{out}}$$

Maximize

Fixed



Does not consider switching losses => Eliminate with ZVS

# Approximate ZVS Analysis

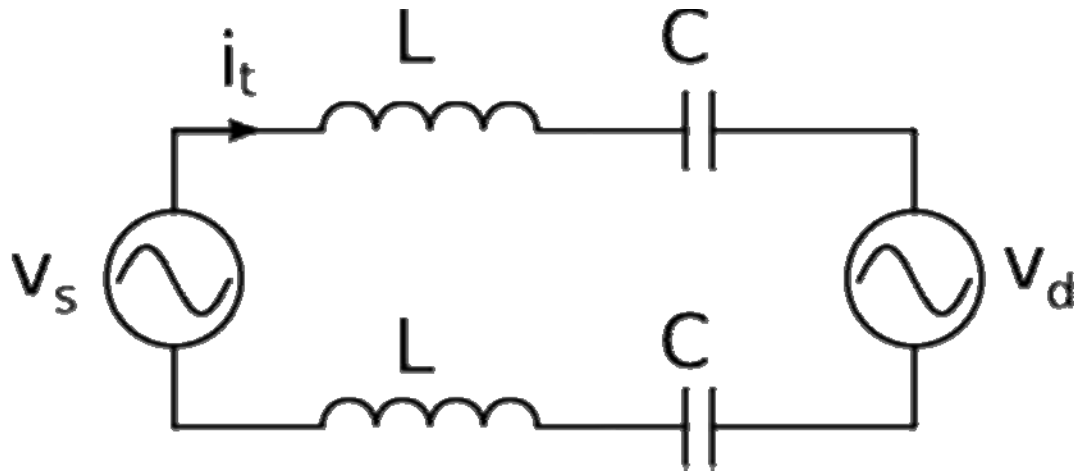

$$\phi = \angle\left(\frac{i_t}{v_s}\right) = \arctan\left(-\sqrt{\frac{V_s^2}{V_D^2} - 1}\right)$$

# Approximate ZVS Analysis

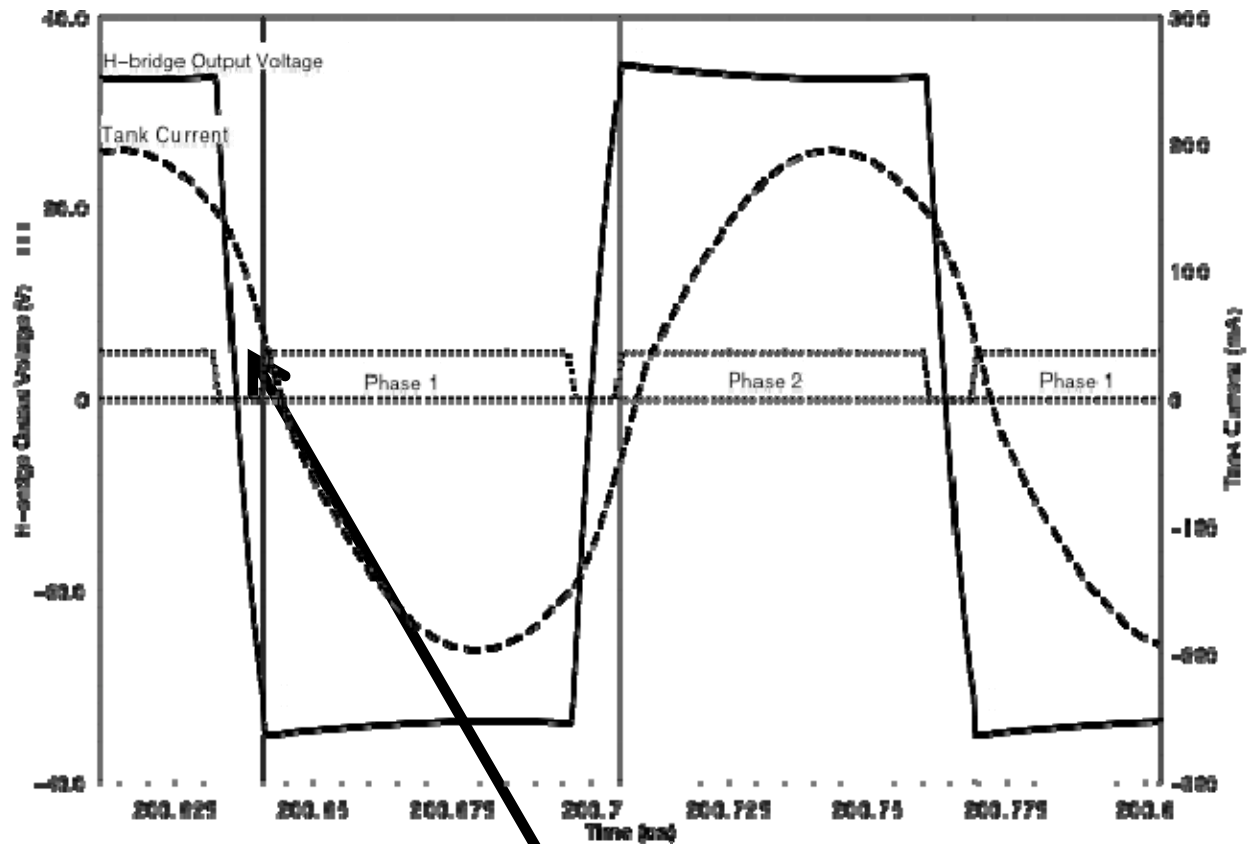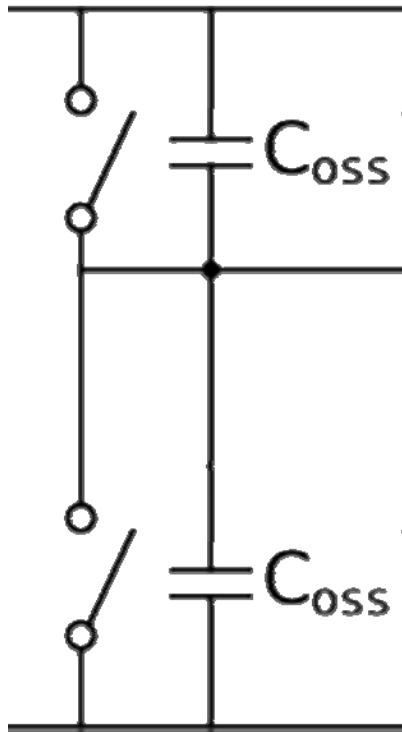

Initial charge

$$q_{sw} = 2C_{oss} V_S$$

$q_t =$  Charge removed by inductor

# ZVS Condition

From integration:

$$q_t = \frac{\|i_t\|}{\omega} (1 - \cos \phi)$$


ZVS requires:

$$q_t \geq q_{sw}$$

Refactored as:


$$\omega \leq \frac{P_{out}}{0.64V_D V_S 2C_{oss}} \left( 1 - \frac{V_D}{V_S} \right)$$

$q_t =$  Charge removed by inductor

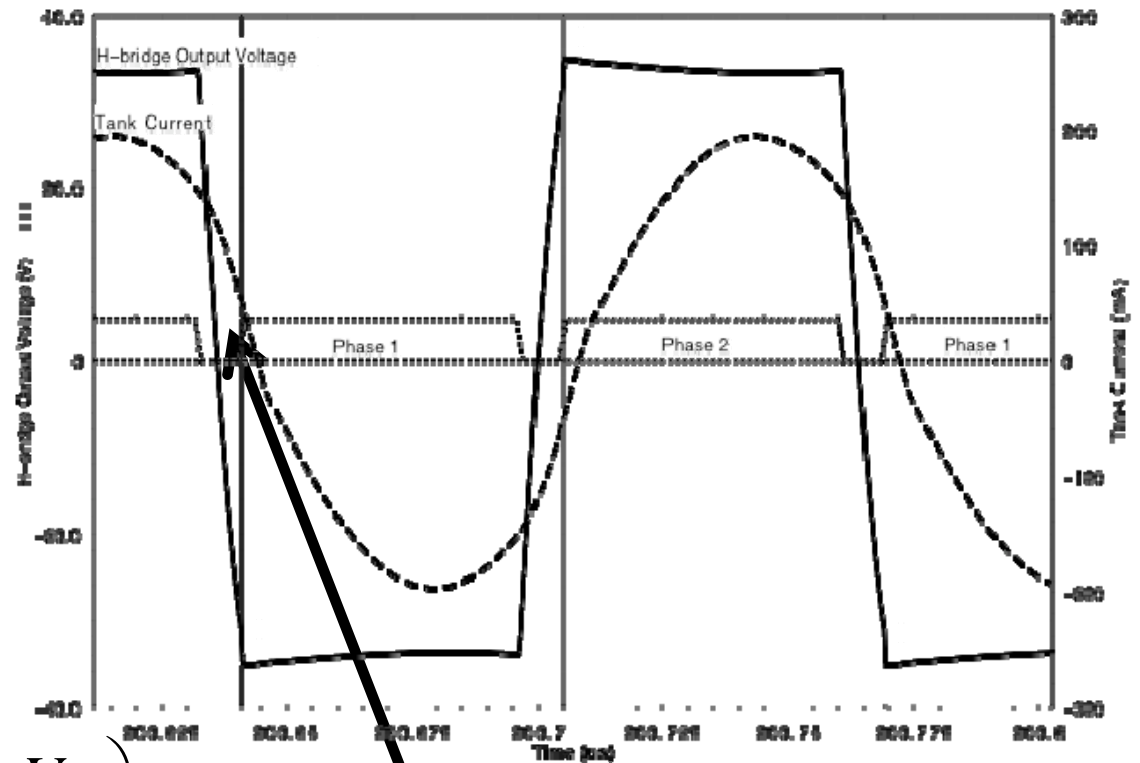
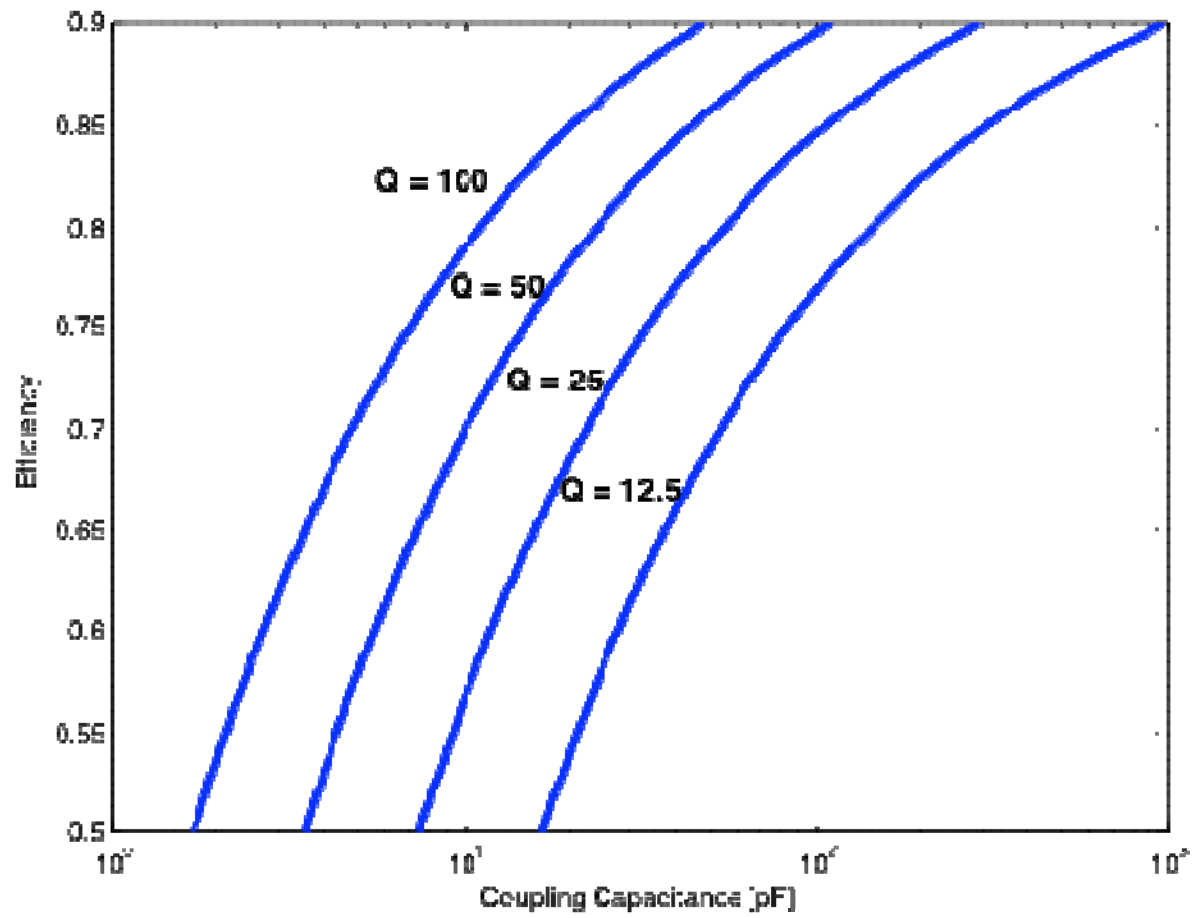
# Example Design

$P_{out} = 4 \text{ W}$ ,  $V_S = 35 \text{ V}$ , and  $R_{on} C_{oss} = 44 \text{ ps}$





# Example Design

**Choose**


**$\eta = 0.9, Q = 40$**

- Minimum C is 147 pF
- Optimum  $V_D/V_S$  is 0.8
- Optimum switch size  $C_{oss} = 13$  pF


Parameter	Expression	Value
$\omega$	$\frac{P_{out}}{0.64A_V V_S^2 2C_{oss}} (1 - A_V)$	$2\pi 7.8$ Mrad/s
$L$	$\frac{1}{\omega^2 C} \left( \frac{0.64}{2} \frac{\omega C A_V V_S^2 \sqrt{1 - A_V^2}}{P_{out}} + 1 \right)$	$3.8 \mu\text{H}$
$R_{on}$	$\frac{\tau_{sw}}{C_{oss}}$	$3.4 \Omega$
$V_D$	$A_V V_S$	28 V
$\omega_0$	$\frac{1}{\sqrt{LC}}$	$2\pi 6.7$ Mrad/s
$R_L$	$\frac{2 \times 0.64^2 V_D^2}{P_{out}}$	$161 \Omega$
$Q_L$	$\frac{2}{R_L} \sqrt{\frac{L}{C}}$	1.9
$\ i_t\ $	$\frac{P_{out}}{(0.64V_D)}$	223 mA
$\phi$	$\arctan \left( -\sqrt{\frac{1}{A_V^2} - 1} \right)$	$-37^\circ$
$I_{out}$	$\frac{P_{out}}{V_D}$	143 mA

# Simulation Results

Parameter	Design	Simulation
$P_{out}$	4 W	4 W
$\eta$	0.8	0.81
$\ i_t\ $	223 mA	222 mA
$I_{out}$	143 mA	142 mA
$\angle(v_d/v_s)$	$-37^\circ$	$-32^\circ$

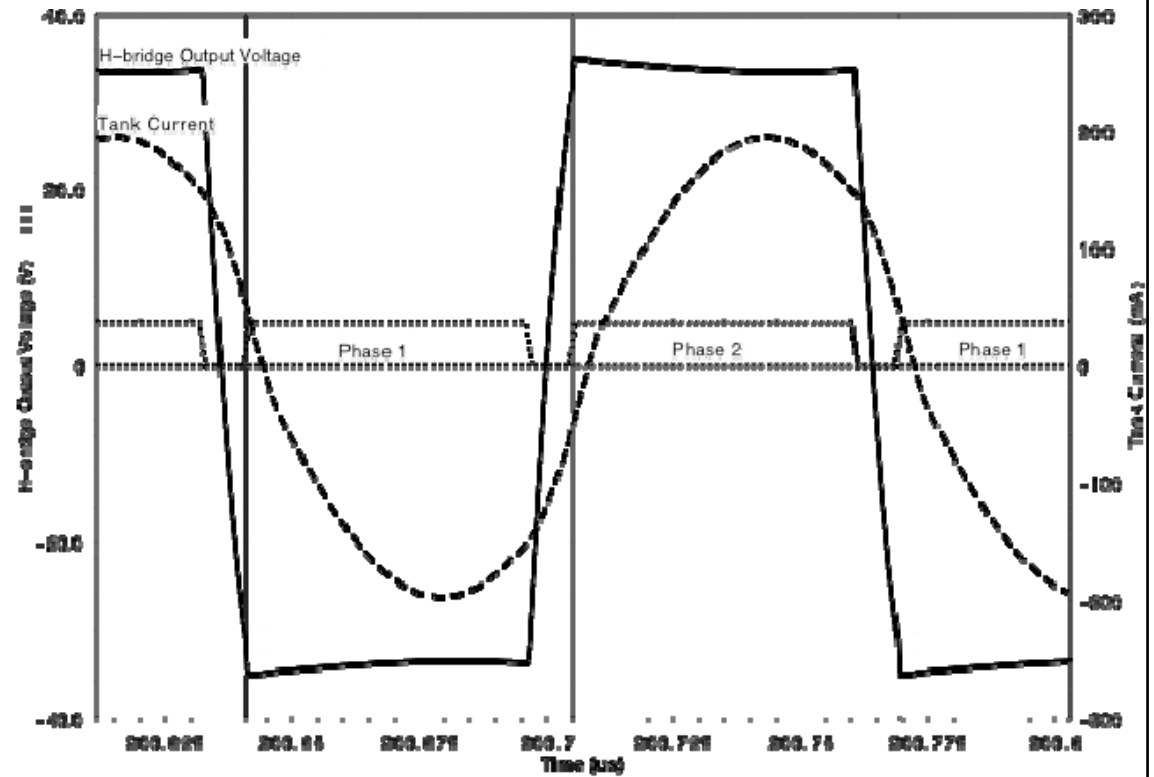


# Prototype Powertrain Circuit

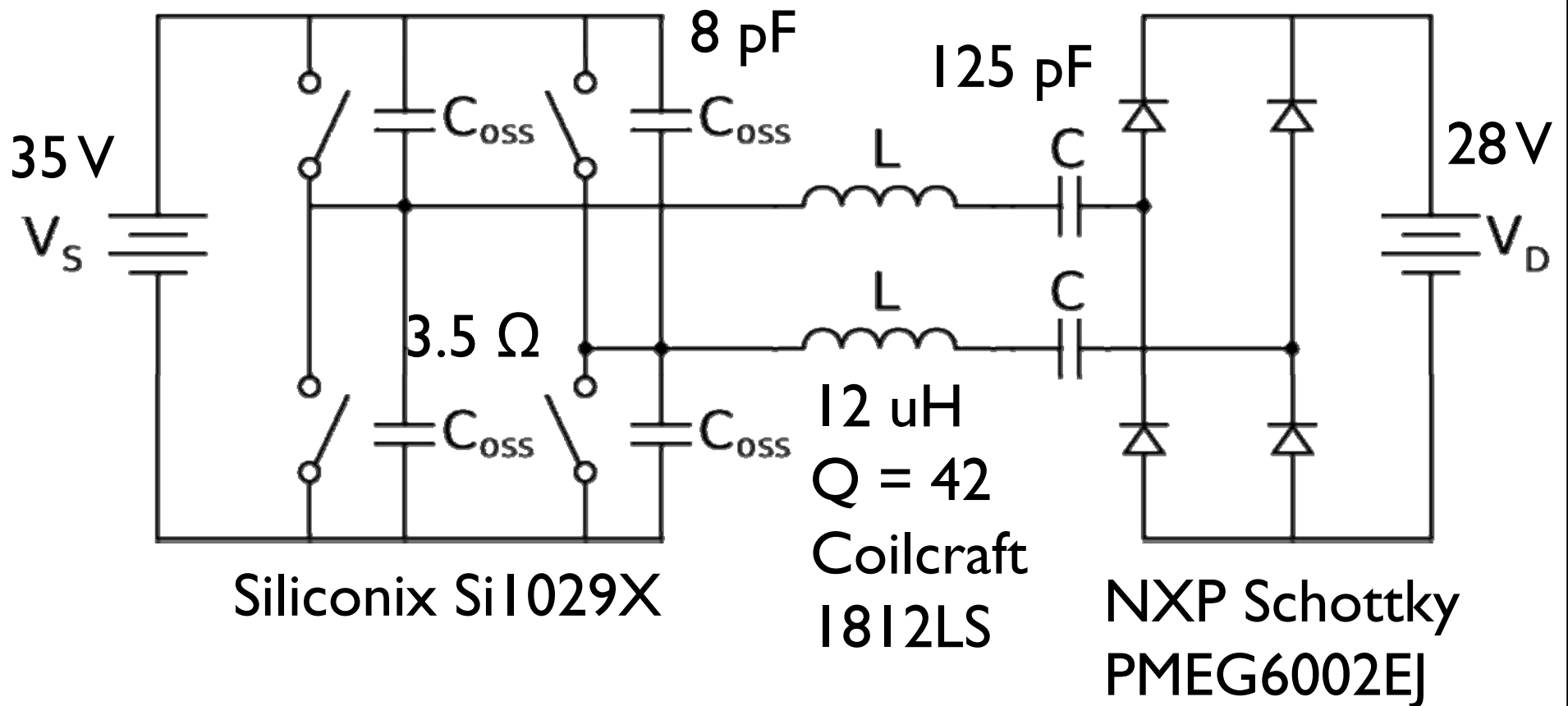


# Experimental Results

Parameter	Design	Simulation	Experimental
$P_{out}$	4 W	4 W	3.72 W
$\eta$	0.8	0.81	0.77
$\ i_t\ $	223 mA	222 mA	—
$I_{out}$	143 mA	142 mA	133 mA
$\angle(v_d/v_s)$	$-37^\circ$	$-32^\circ$	$-48^\circ$

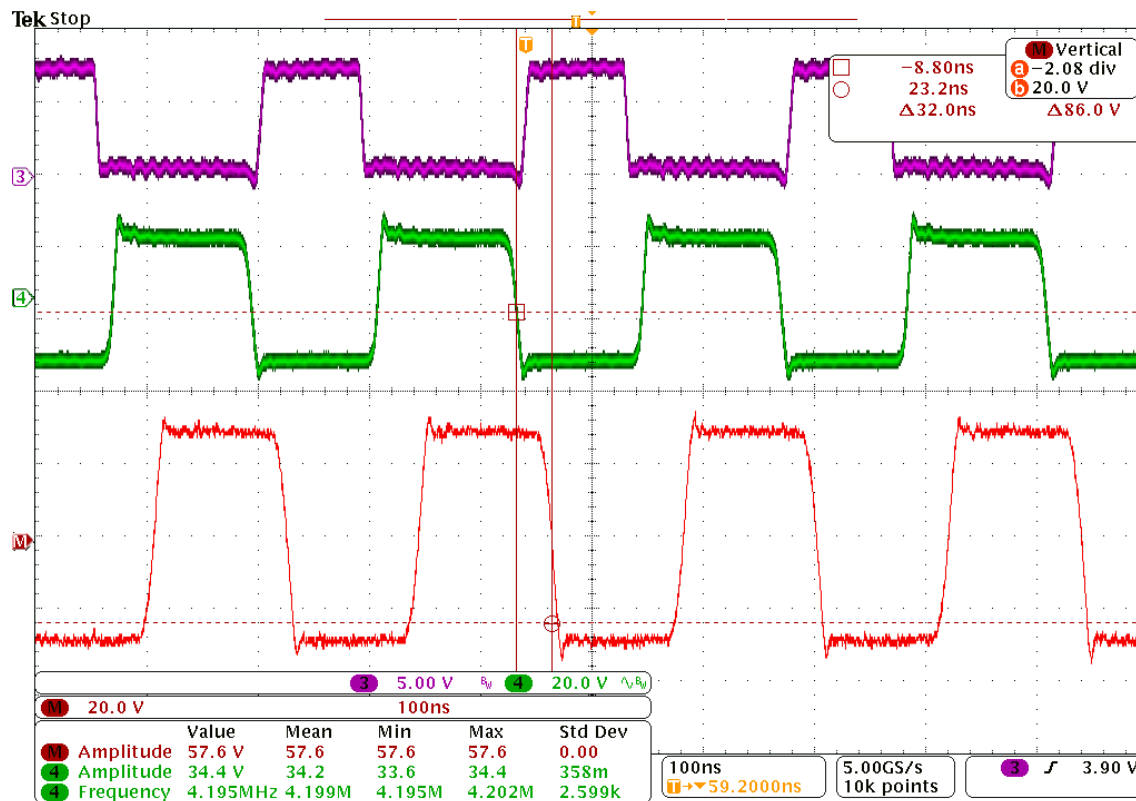


# Capacitive Power Transfer System

1

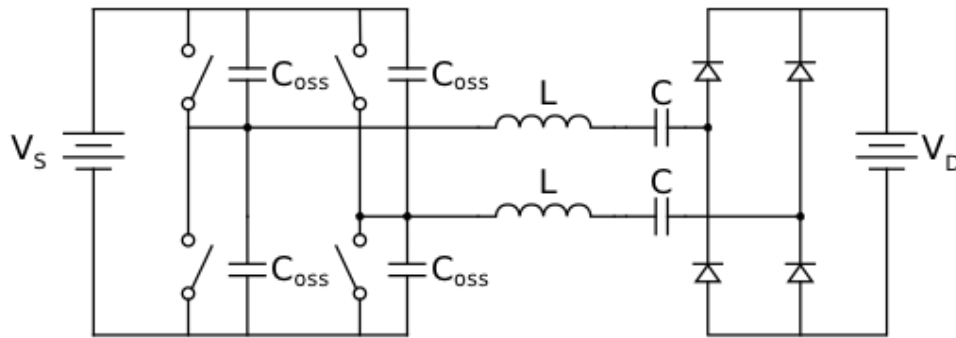


**Powertrain  
optimization**

2

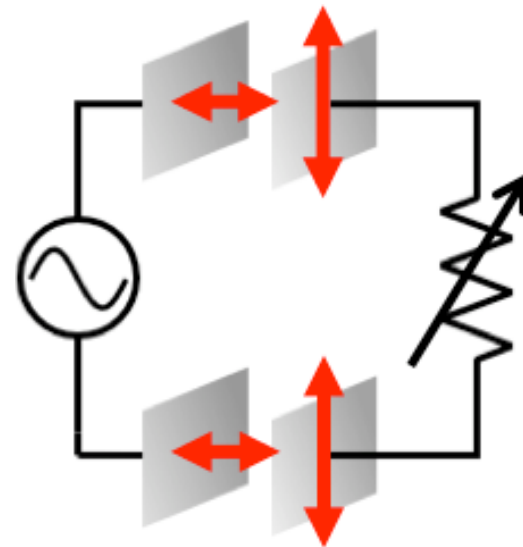


**Alignment and  
load sensitivity**


# Automatic Frequency Tuning

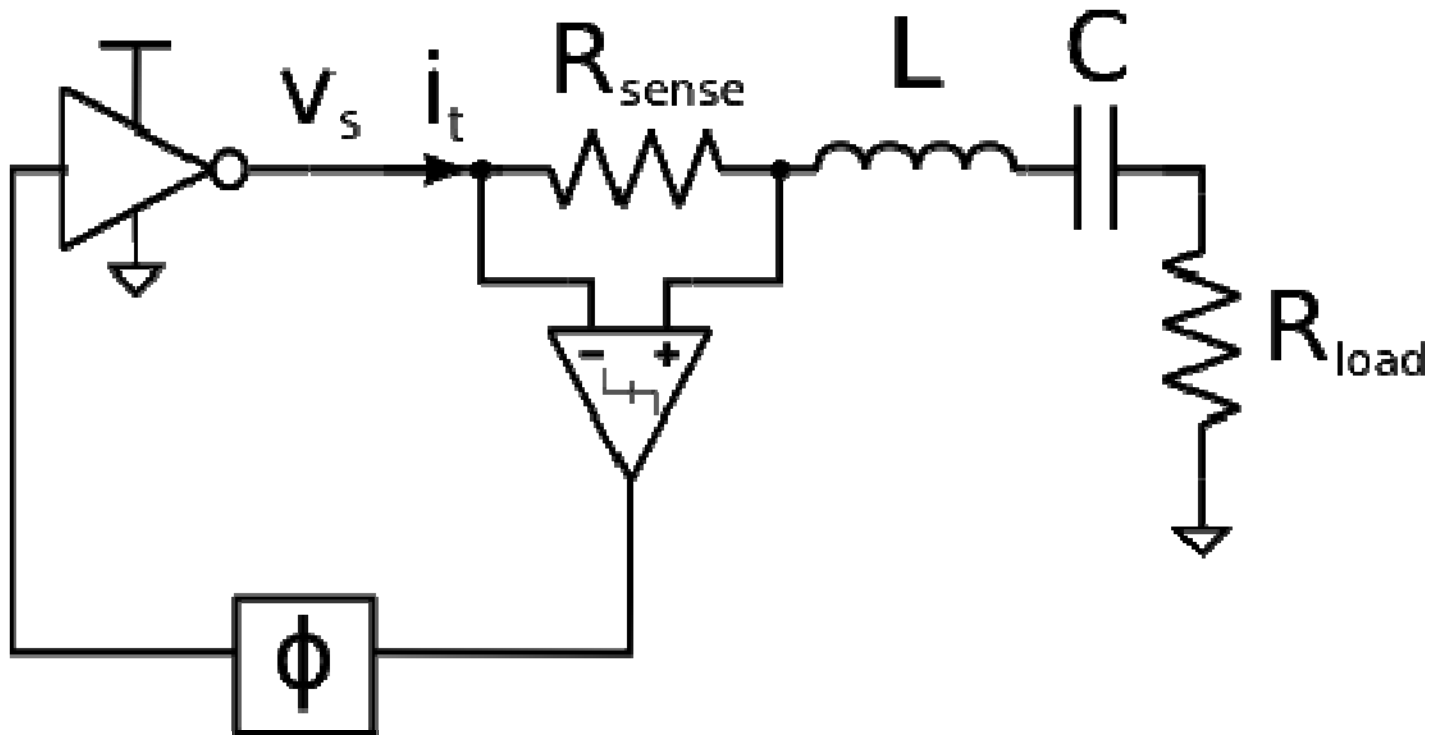

# Automatic Frequency Tuning

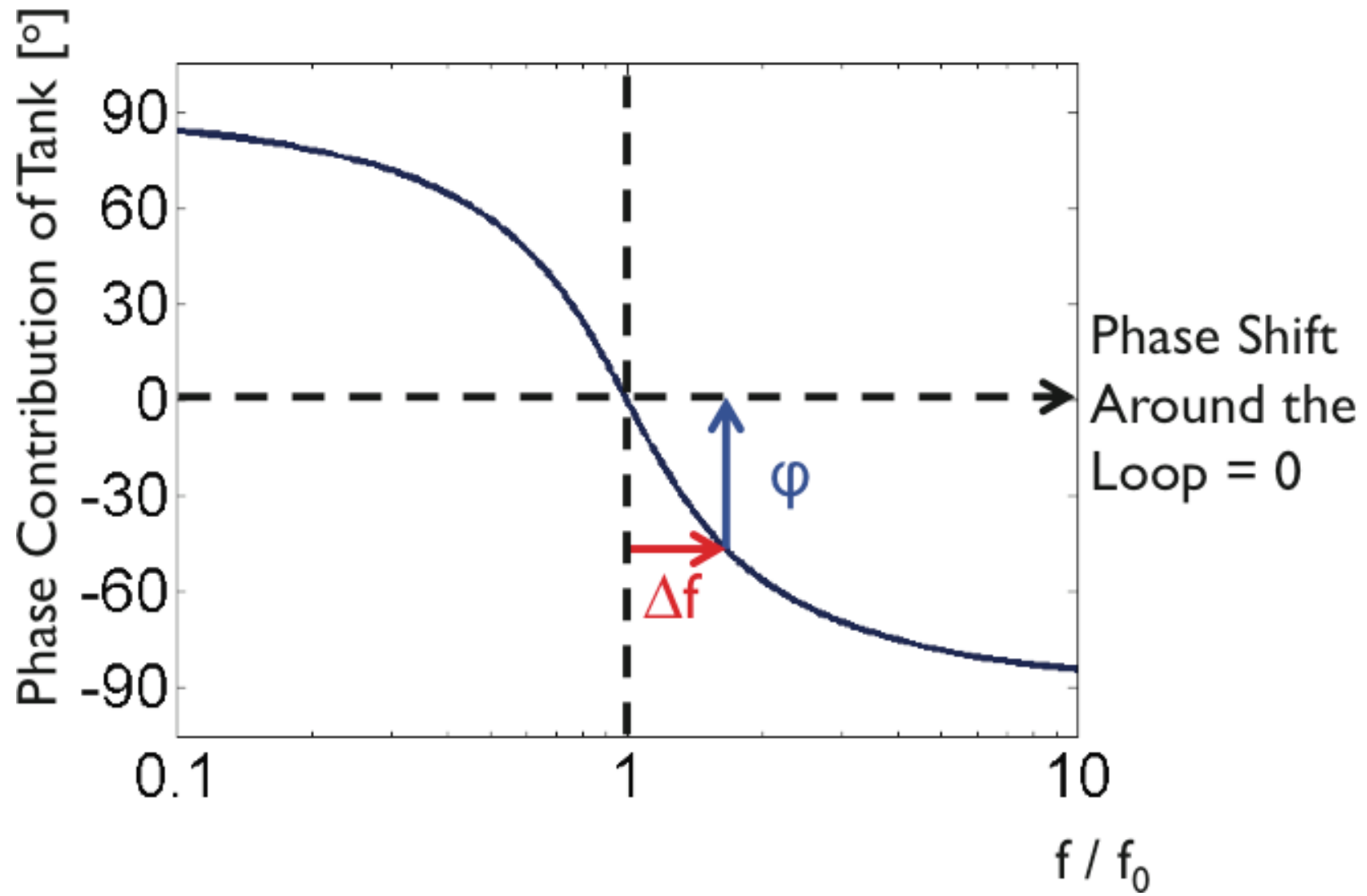

# Automatic Duty Cycle Control

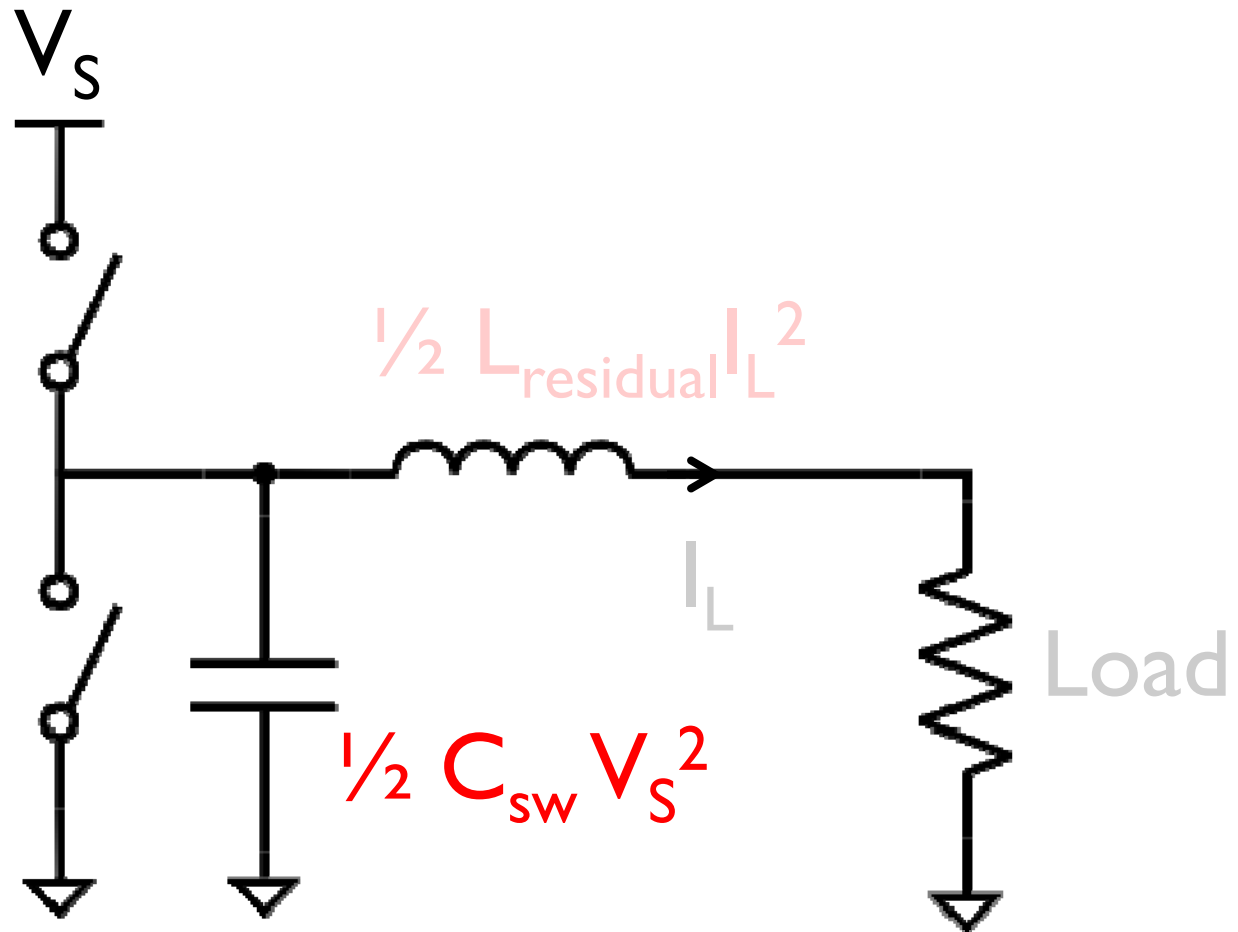

**Light-load condition:** not enough current in tank to get Zero Voltage Switching (ZVS)




# Automatic Duty Cycle Control


SHUTDOWN


Supply  
Current

DC  
Output  
Voltage

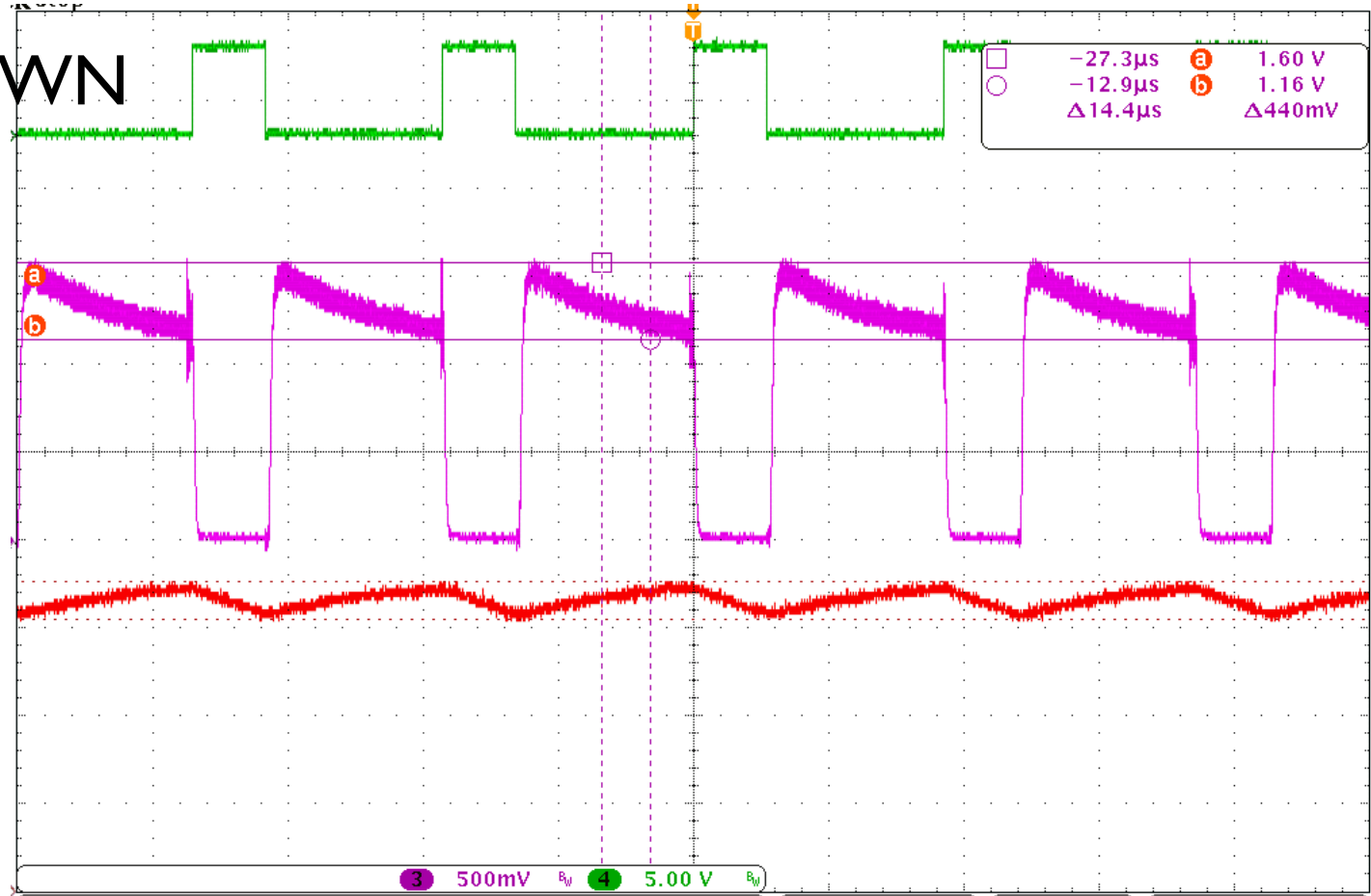

# Capacitive Power Transfer System

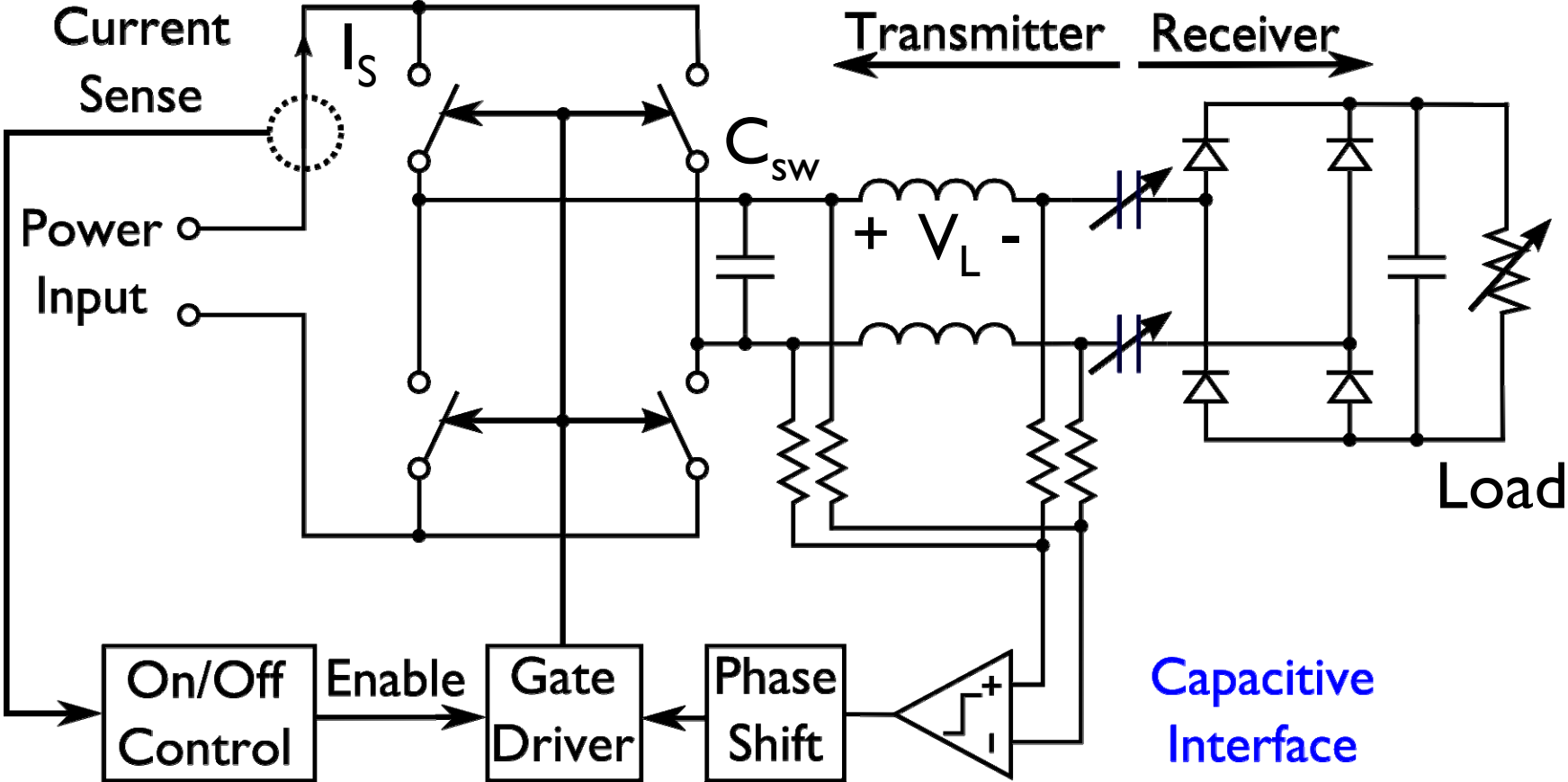

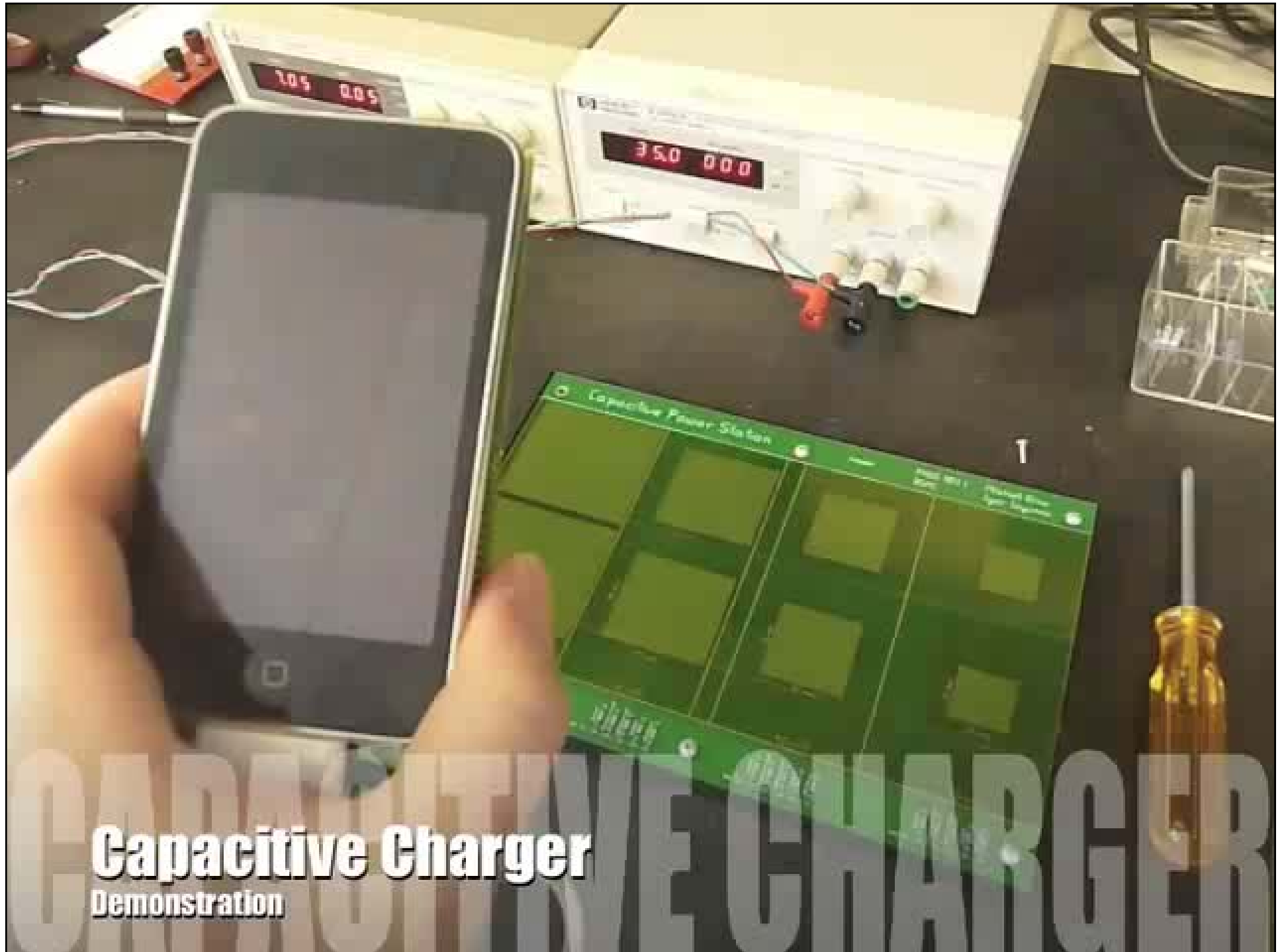



# Capacitive Charger

Demonstration

CAPACITIVE CHARGER

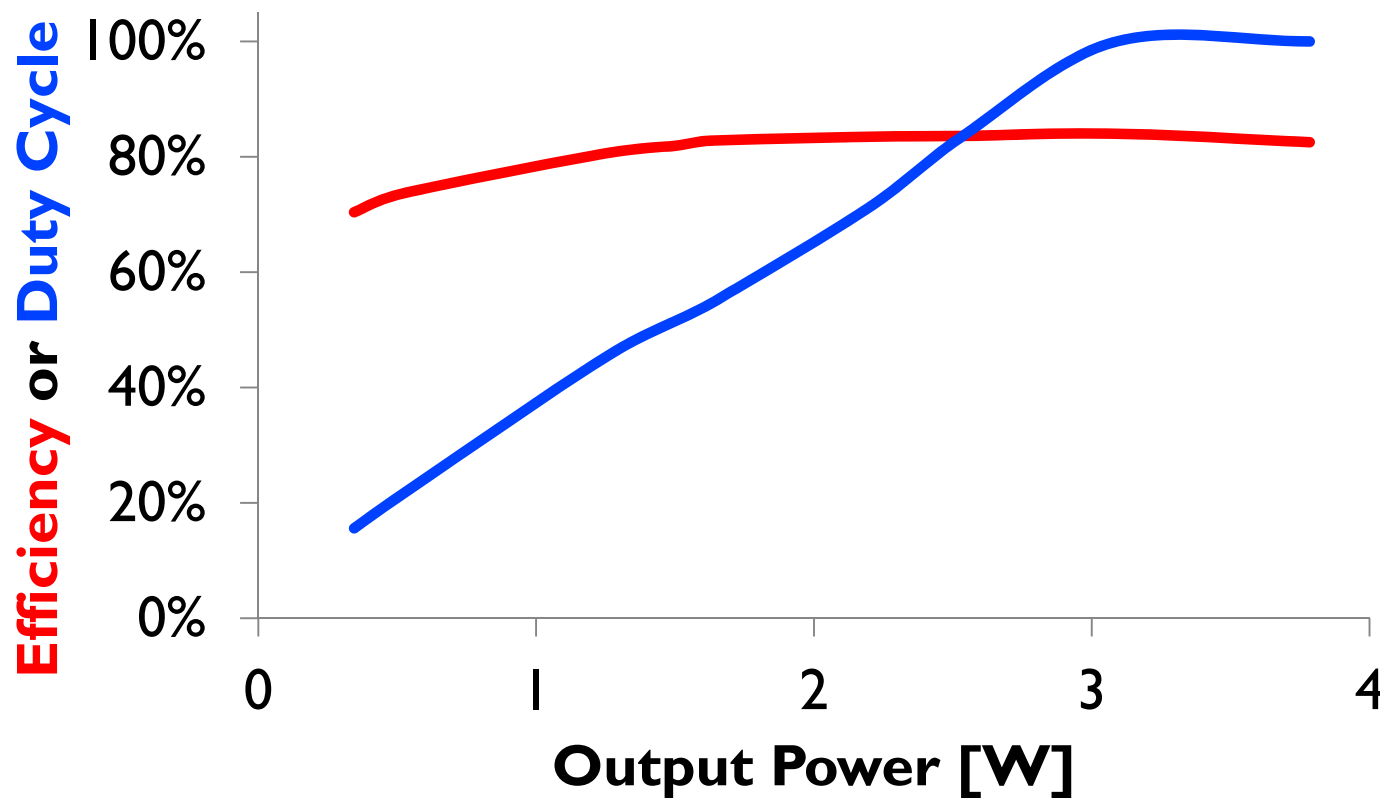
With **6 by 10 cm<sup>2</sup>**, we transfer **3.8 W** at **83%** efficiency over a **0.5 mm** air gap.



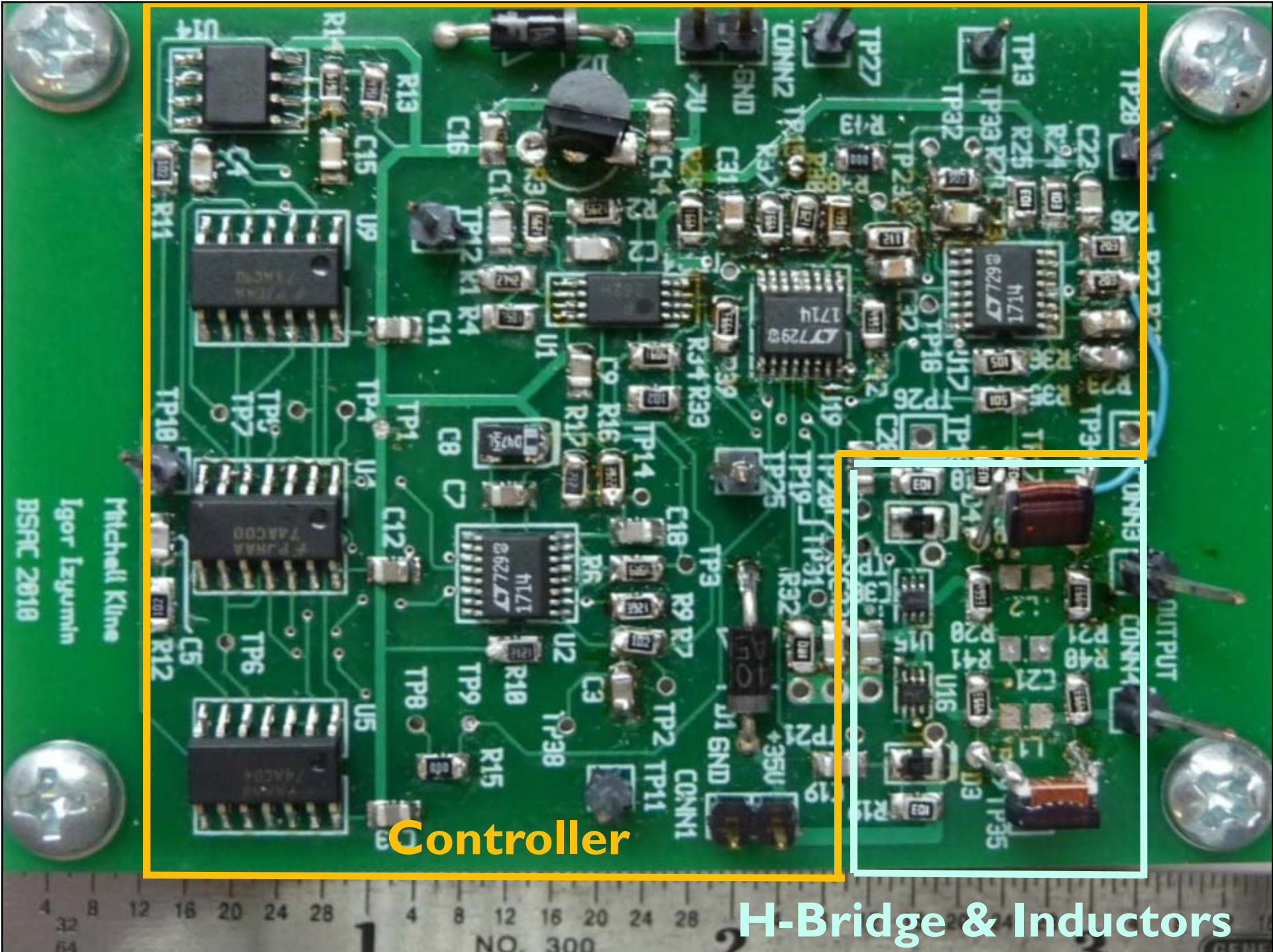


**Controller**

**H-Bridge & Inductors**

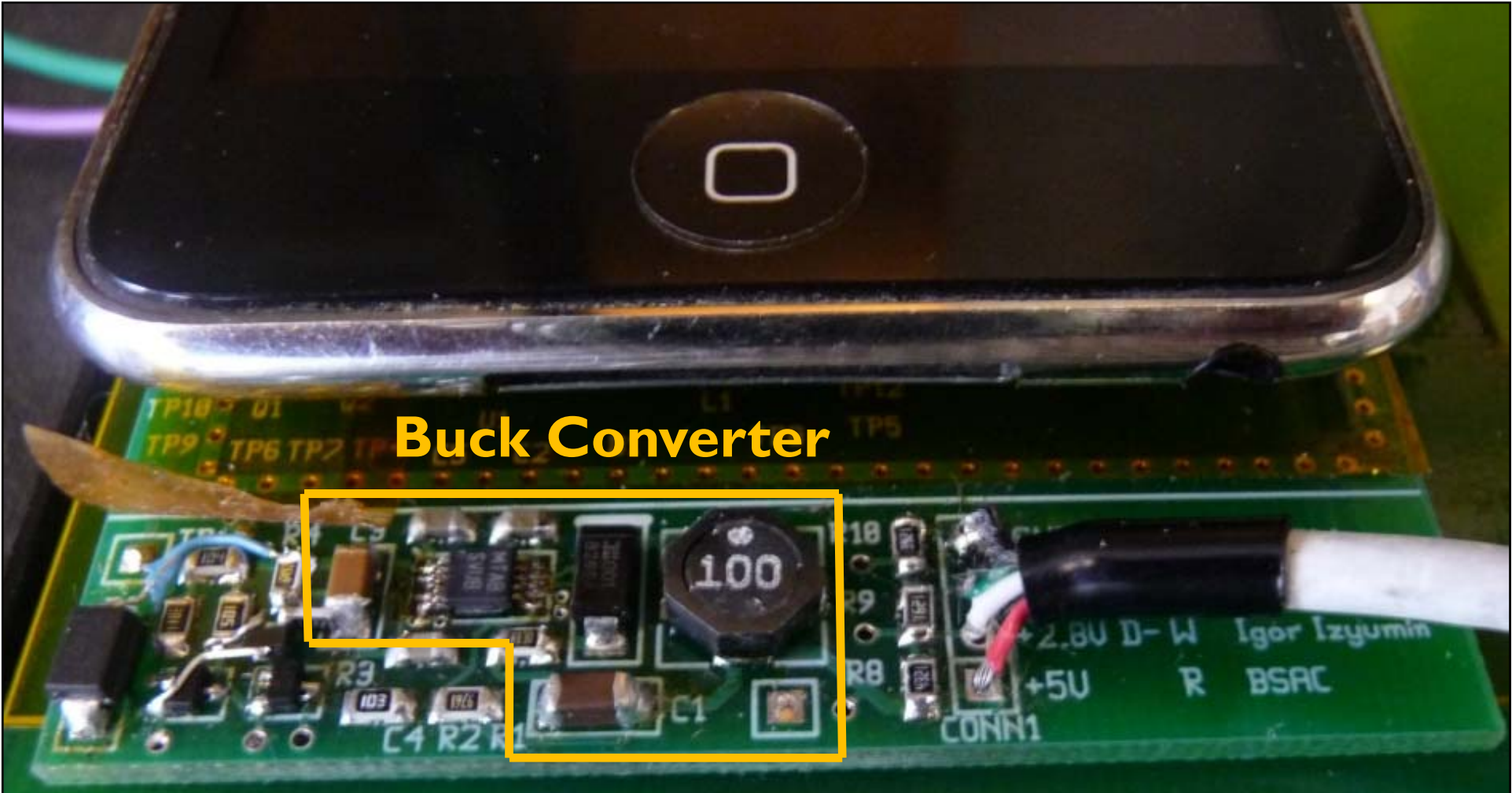

**Buck Converter**

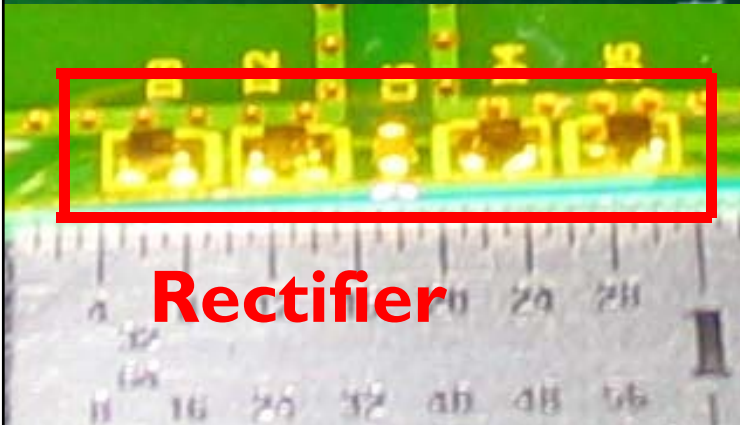

**Rectifier**

# Conclusion

Power transfer over small capacitors is enabled by

1. Zero Voltage Switching

Enable moderate voltage, high frequency operation

2. Automatic Tuning

Robust to changes in coupling capacitance

3. Duty cycle adjustment without RX feedback

Preserve efficiency at light loads

# *Thank You!*

## **Acknowledgements**

Dr. Mei-Lin Chan

Dr. Simone Gambini

Prof. David Horsley

Dr. Mischa Megens

James Peng

Richard Przybyla

Kun Wang

Prof. Ming Wu

This material is based upon  
work supported by the  
Defense Advanced  
Research Projects Agency  
(DARPA) under Contract  
No. W31P4Q-10-1-0002