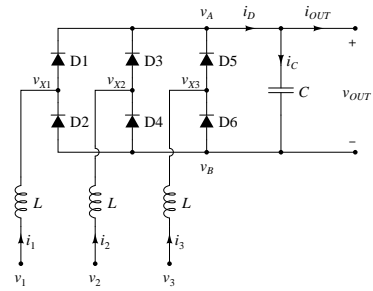


## An Analysis of Three-Phase Rectifiers with Constant Voltage Loads

Predrag Pejović<sup>1</sup>, Johann W. Kolar<sup>2</sup>

<sup>1</sup>University of Belgrade, Faculty of Electrical Engineering  
peja@etf.rs

<sup>2</sup>Swiss Federal Institute of Technology, Zürich  
kolar@lem.ee.ethz.ch




### The rectifier, properties

- ▶ simple
- ▶ inexpensive
- ▶ robust
- ▶ AC side parameters?
- ▶ AC side compliance with regulations?
- ▶ DC side parameters, dependence of  $V_{OUT}$  on  $I_{OUT}$ ?

### The rectifier, available information

- ▶ old rectifier, well known?
- ▶ V. Caliskan, D. J. Perreault, T. M. Jahns, and J. G. Kassakian, "Analysis of three-phase rectifiers with constant-voltage loads," *IEEE Trans. Circuits Syst. I, Fundam. Theory Appl.*, vol. 50, no. 9, pp. 1220–1226, Sep. 2003.
- ▶ P. Pejović, J. W. Kolar, "Exact analysis of three-phase rectifiers with constant voltage loads," *IEEE Trans. Circuits Syst. II, Express Briefs*, vol. 55, no. 8, pp. 743–747, Aug. 2008.
- ▶ continuous conduction mode (CCM) covered, three diodes conduct
- ▶ what about the discontinuous conduction mode(s) (DCM)?


### The rectifier to be analyzed

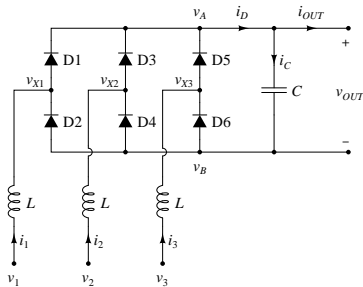

### Assumptions

- ▶ output ripple neglected,  $v_{OUT} = V_{OUT}$
- ▶ symmetrical undistorted three-phase system
- ▶  $v_k = V_m \cos\left(\omega t - (k-1)\frac{2\pi}{3}\right)$ , for  $k \in \{1, 2, 3\}$
- ▶ resistance neglected
- ▶ line inductance can be included in the model
- ▶ ideal diodes assumed,  $V_D$  could be included

### The rectifier model

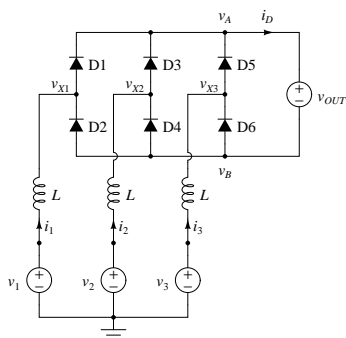

### Normalization

- ▶  $v_k = V_m \cos\left(\omega t - (k-1)\frac{2\pi}{3}\right)$ , for  $k \in \{1, 2, 3\}$
- ▶  $m = \frac{v}{V_m}$
- ▶  $j = \frac{\omega L}{V_m} i$
- ▶  $\varphi = \omega t$
- ▶  $L \frac{di_k}{dt} = v_k - v_{Xk}$
- ▶  $\frac{dj_k}{d\varphi} = m_k - m_{Xk}$

- ▶ ideal diodes assumed
- ▶ one bit sufficient to code diode state, either on or off
- ▶ 6 diodes,  $2^6 = 64$  combinations
- ▶ some combinations forbidden
- ▶  $V_{OUT} > 0$ , diodes in pairs (D1, D2), (D3, D4), and (D5, D6) cannot conduct simultaneously
- ▶ pair coded as +1, 0, or -1, reduction to  $3^3 = 27$  states
- ▶  $i_1 + i_2 + i_3 = 0$ , combinations like (+1, +1, +1), (-1, 0, -1), or (0, 0, +1) cannot occur, 14 of them
- ▶ final reduction to 13 combinations (out of 64)

combination	phase leg state		
	1	2	3
0	0	0	0
1	+1	-1	0
2	+1	0	-1
3	-1	+1	0
4	0	+1	-1
5	-1	0	+1
6	0	-1	+1
7	+1	+1	-1
8	+1	-1	+1
9	-1	+1	+1
10	+1	-1	-1
11	-1	+1	-1
12	-1	-1	+1


Circuit description

- ▶ equations over inductor currents
- ▶ equations for the output terminal voltages
- ▶ boundary conditions, theoretically 6 of them
- ▶ combination transition rules

Equations for state 0, without conducting diodes

- ▶  $j_k = j_l = j_n = 0$
- ▶  $m_A - m_B = M_{OUT}$
- ▶  $m_{kl} < M_{OUT}$
- ▶ the system order is zero

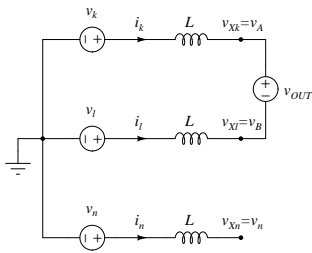
Equivalent circuit for two conducting diodes



Equations for two conducting diodes

- ▶  $state(k) = +1, state(l) = -1, state(n) = 0$
- ▶  $\frac{dj_k}{d\varphi} = \frac{1}{2}(m_k - m_l - M_{OUT}), j_l = -j_k, j_n = 0$
- ▶  $m_A = \frac{1}{2}(M_{OUT} - m_n), m_B = \frac{1}{2}(M_{OUT} + m_n)$
- ▶  $j_k > 0$ , to combination 0 if violated
- ▶  $m_n < \frac{1}{3}M_{OUT}$  leg n to state +1 if violated
- ▶  $m_n > -\frac{1}{3}M_{OUT}$  leg n to state -1 if violated
- ▶ the circuit is of the first order

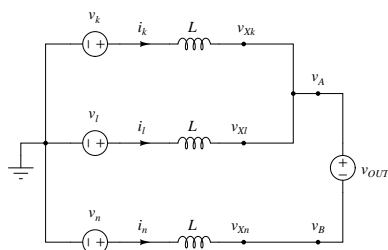
Equivalent circuit for three conducting diodes, two to the positive output terminal



Equations for three conducting diodes, two to the positive output terminal

- ▶  $\frac{dj_k}{d\varphi} = m_k - \frac{1}{3}M_{OUT}$
- ▶  $\frac{dj_l}{d\varphi} = m_l - \frac{1}{3}M_{OUT}$
- ▶  $j_n = -j_k - j_l$
- ▶  $m_A = \frac{1}{3}M_{OUT}, m_B = -\frac{2}{3}M_{OUT}$
- ▶  $j_k > 0, j_l > 0, j_n < 0$
- ▶ possible instantaneous combination transitions, additional inequalities
- ▶ the system is of the second order

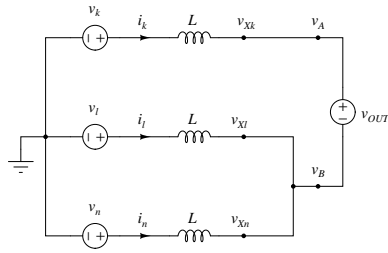Equivalent circuit for three conducting diodes, one to the positive output terminal




Equations for three conducting diodes, one to the positive output terminal

- ▶  $\frac{dj_k}{d\varphi} = m_k - \frac{2}{3}M_{OUT}$
- ▶  $\frac{dj_l}{d\varphi} = m_l + \frac{1}{3}M_{OUT}$
- ▶  $j_n = -j_k - j_l$
- ▶  $m_A = \frac{2}{3}M_{OUT}, m_B = -\frac{1}{3}M_{OUT}$
- ▶  $j_k > 0, j_l < 0, j_n < 0$
- ▶ possible instantaneous combination transitions, additional inequalities
- ▶ the system is of the second order


Modes

- ▶ mode 0, only combination 0
- ▶ mode 1, combinations with 0 and 2 conducting diodes
- ▶ mode 2, combinations with 0, 2, and 3 conducting diodes
- ▶ mode 3, combinations with 2, and 3 conducting diodes
- ▶ mode 4, only combinations with 3 conducting diodes, CCM

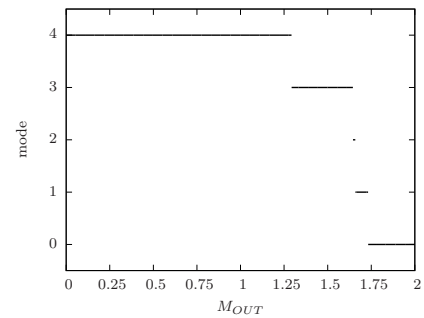
Dependence of the operating mode on  $M_{OUT}$



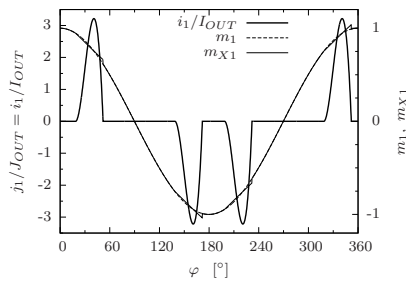
Mode 1, waveforms of  $i_1, v_1,$  and  $v_{X1}, M_{OUT} = 1.7$



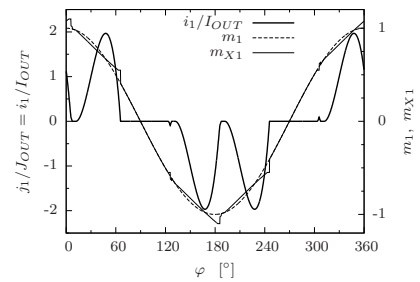
Mode 2, waveforms of  $i_1, v_1,$  and  $v_{X1}, M_{OUT} = 1.6475$



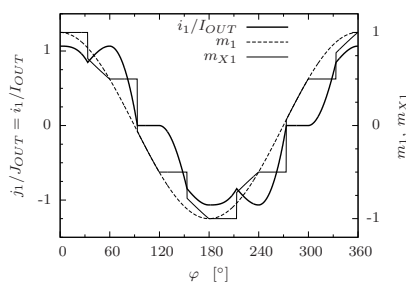
Mode 3, waveforms of  $i_1, v_1,$  and  $v_{X1}, M_{OUT} = 1.5$



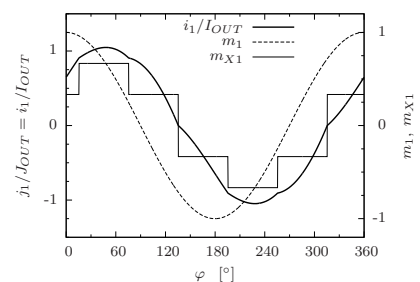
Mode 4, waveforms of  $i_1, v_1,$  and  $v_{X1}, M_{OUT} = 1$




## Dependence of $M_{OUT}$ on $J_{OUT}$

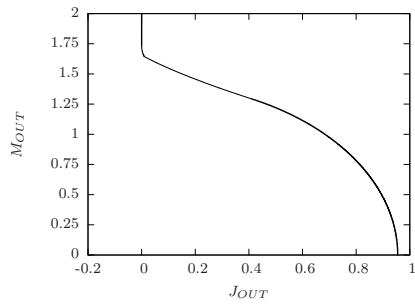

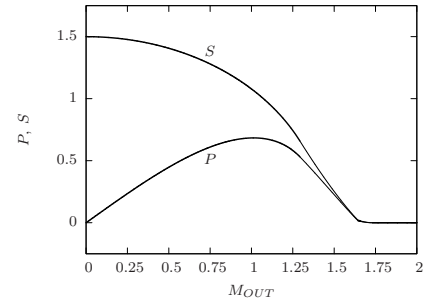
## Dependence of the rectifier power and apparent power on $M_{OUT}$



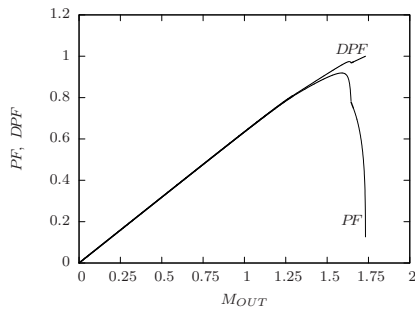
## Dependence of the rectifier power factor and the displacement power factor on $M_{OUT}$ .



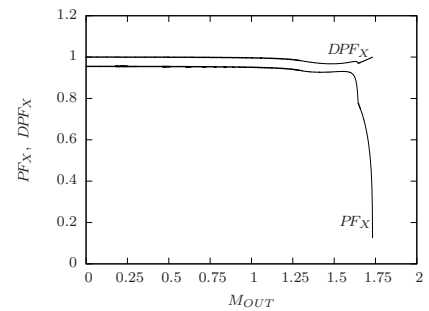
## Dependence of $PF_X$ and $DPF_X$ on $M_{OUT}$


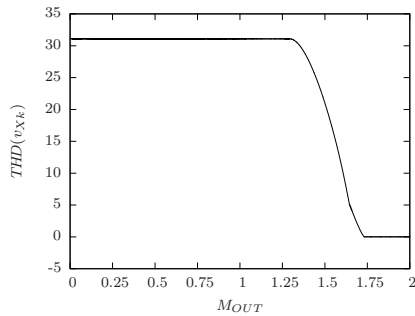
## Dependence of $THD(v_{Xk})$ on $M_{OUT}$



## Dependence of $THD(i_k)$ on $M_{OUT}$

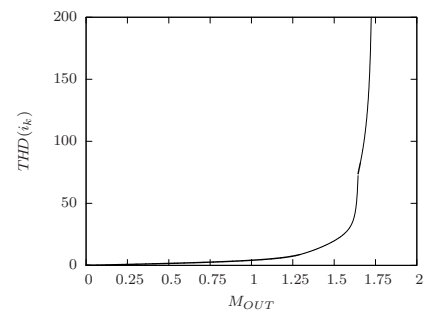

## Conclusions 1

- ▶ numerical analysis of a three-phase voltage loaded rectifier
- ▶ analysis performed on the equation system level, normalization
- ▶ insight in the rectifier operation, identification of the operating modes
- ▶ combinations of diode states, combinatorial approach
- ▶ out of  $2^6 = 64$  combinations of diode states only 13 might occur
- ▶ for all 13 circuit equations are derived
- ▶ circuit order might be zero, one, or two, depending on the diode state combination

## Conclusions 2

- ▶ boundary inequalities are derived, combination transition rules
- ▶ instantaneous combination transitions
- ▶ modes of the circuit operation are defined
- ▶ simulation,  $M_{OUT}$  from 2 to 0 in steps of 0.0005
- ▶ dependence of  $M_{OUT}$  on  $J_{OUT}$  is presented
- ▶ dependence on  $M_{OUT}$  of  $P$ ,  $S$ ,  $PF$ ,  $PF_X$ ,  $DPF$ ,  $DPF_X$ ,  $THD(i_k)$ ,  $THD(v_{Xk})$
- ▶ obtained diagrams quick reference guide for the rectifier design
- ▶ some interest in education