

HIGH-SPEED DIGITAL DESIGN

A Handbook of Black Magic

HOWARD W. JOHNSON, PH.D.
Signal Consulting, Inc.

MARTIN GRAHAM, PH.D.
University of California at Berkeley

For book and bookstore information



<http://www.phptr.com>



Prentice Hall PTR, Upper Saddle River, New Jersey 07458

Contents

Preface *ix*

1 Fundamentals 1

- 1.1 Frequency and Time 1
- 1.2 Time and Distance 6
- 1.3 Lumped Versus Distributed Systems 7
- 1.4 A Note About 3 dB and RMS Frequencies 8
- 1.5 Four Kinds of Reactance 10
- 1.6 Ordinary Capacitance 11
- 1.7 Ordinary Inductance 17
- 1.8 A Better Method for Estimating Decay Time 22
- 1.9 Mutual Capacitance 25
- 1.10 Mutual Inductance 29

2 High-Speed Properties of Logic Gates 37

- 2.1 Historical Development of a Very Old Digital Technology 37
- 2.2 Power 39
- 2.3 Speed 59
- 2.4 Packaging 66

3	Measurement Techniques	83
3.1	Rise Time and Bandwidth of Oscilloscope Probes	83
3.2	Self-inductance of a Probe Ground Loop	86
3.3	Spurious Signal Pickup from Probe Ground Loops	92
3.4	How Probes Load Down a Circuit	95
3.5	Special Probing Fixtures	98
3.6	Avoiding Pickup from Probe Shield Currents	104
3.7	Viewing a Serial Data Transmission System	108
3.8	Slowing Down the System Clock	110
3.9	Observing Crosstalk	111
3.10	Measuring Operating Margins	113
3.11	Observing Metastable States	120
4	Transmission Lines	133
4.1	Shortcomings of Ordinary Point-to-Point Wiring	133
4.2	Infinite Uniform Transmission Line	140
4.3	Effects of Source and Load Impedance	160
4.4	Special Transmission Line Cases	167
4.5	Line Impedance and Propagation Delay	178
5	Ground Planes and Layer Stacking	189
5.1	High-Speed Current Follows the Path of Least Inductance	189
5.2	Crosstalk in Solid Ground Planes	191
5.3	Crosstalk in Slotted Ground Planes	194
5.4	Crosstalk in Cross-Hatched Ground Planes	197
5.5	Crosstalk with Power and Ground Fingers	199
5.6	Guard Traces	201
5.7	Near-End and Far-End Crosstalk	204
5.8	How to Stack Printed Circuit Board Layers	212
6	Terminations	223
6.1	End Terminators	223
6.2	Source Terminators	231
6.3	Middle Terminators	235
6.4	AC Biasing for End Terminators	236
6.5	Resistor Selection	239
6.6	Crosstalk in Terminators	244
7	Vias	249
7.1	Mechanical Properties of Vias	249
7.2	Capacitance of Vias	257
7.3	Inductance of Vias	258
7.4	Return Current and Its Relation to Vias	260

8	Power Systems	263
8.1	Providing a Stable Voltage Reference	263
8.2	Distributing Uniform Voltage	268
8.3	Everyday Distribution Problems	279
8.4	Choosing a Bypass Capacitor	281
9	Connectors	295
9.1	Mutual Inductance—How Connectors Create Crosstalk	295
9.2	Series Inductance—How Connectors Create EMI	300
9.3	Parasitic Capacitance—Using Connectors on a Multidrop Bus	305
9.4	Measuring Coupling in a Connector	309
9.5	Continuity of Ground Underneath a Connector	312
9.6	Fixing EMI Problems with External Connections	314
9.7	Special Connectors for High-Speed Applications	316
9.8	Differential Signaling Through a Connector	319
9.9	Power Handling Features of Connectors	321
10	Ribbon Cables	323
10.1	Ribbon Cable Signal Propagation	324
10.2	Ribbon Cable Crosstalk	329
10.3	Ribbon Cable Connectors	336
10.4	Ribbon Cable EMI	338
11	Clock Distribution	341
11.1	Timing Margin	341
11.2	Clock Skew	343
11.3	Using Low-Impedance Drivers	346
11.4	Using Low-Impedance Clock Distribution Lines	348
11.5	Source Termination of Multiple Clock Lines	350
11.6	Controlling Crosstalk on Clock Lines	352
11.7	Delay Adjustments	353
11.8	Differential Distribution	360
11.9	Clock Signal Duty Cycle	361
11.10	Canceling Parasitic Capacitance of a Clock Repeater	362
11.11	Decoupling Clock Receivers from the Clock Bus	364
12	Clock Oscillators	367
12.1	Using Canned Clock Oscillators	367
12.2	Clock Jitter	376

	Collected References	385
A	Points to Remember	389
B	Calculation of Rise Time	399
C	MathCad Formulas	409
	Index	441