
INTRODUCTION TO CMOS OP-AMPS AND COMPARATORS

ROUBIK GREGORIAN



A Wiley-Interscience Publication

JOHN WILEY & SONS, INC.

New York / Chichester / Weinheim / Brisbane / Singapore / Toronto

CONTENTS

PREFACE	ix
1 INTRODUCTION	1
1.1 Classification of Signal Processing Techniques / 1	
1.2 Examples of Applications of Op-Amps and Comparators in Analog MOS Circuits / 6	
Problems / 16	
References / 16	
2 MOS DEVICES AS CIRCUIT ELEMENTS	17
2.1 Semiconductors / 17	
2.2 MOS Transistors / 21	
2.3 MOS Transistor Types: Body Effect / 27	
2.4 Small-Signal Operation and Equivalent Circuit of MOSFET Transistors / 30	
2.5 Weak Inversion / 39	
2.6 Impact Ionization / 40	
2.7 Noise in MOSFETS / 41	
2.8 CMOS Process / 44	
Problems / 45	
References / 47	

3 BASIC ANALOG CMOS SUBCIRCUITS	48
3.1 Bias Circuits in MOS Technology / 48	
3.2 MOS Current Mirrors and Current Sources / 55	
3.3 MOS Gain Stages / 63	
3.4 MOS Source Followers / 74	
3.5 MOS Differential Amplifiers / 77	
3.6 Frequency Response of MOS Amplifier Stages / 84	
Problems / 92	
References / 94	
4 CMOS OPERATIONAL AMPLIFIERS	95
4.1 Operational Amplifiers / 95	
4.2 Single-Stage Operational Amplifiers / 100	
4.3 Two-Stage Operational Amplifiers / 106	
4.4 Stability and Compensation of CMOS Amplifiers / 112	
4.5 Dynamic Range of CMOS Op-Amps / 126	
4.6 Frequency Response, Transient Response, and Slew Rate of Compensated CMOS Op-Amps / 132	
4.7 Noise Performance of CMOS Op-Amps / 137	
4.8 Fully Differential Op-Amps / 140	
4.9 CMOS Output Stages / 149	
4.10 Op-Amps with Rail-to-Rail Input Common-Mode Range / 164	
Problems / 170	
References / 173	
5 COMPARATORS	175
5.1 Circuit Modeling of a Comparator / 175	
5.2 Single-Ended Auto-Zeroing Comparators / 177	
5.3 Differential Comparators / 182	
5.4 Regenerative Comparators (Schmitt Triggers) / 192	
5.5 Fully Differential Comparators / 198	
5.6 Latches / 205	
Problems / 212	
References / 213	
6 DIGITAL-TO-ANALOG CONVERTERS	214
6.1 Digital-to-Analog Conversion: Basic Principles / 214	
6.2 Voltage-Mode D/A Converter Stages / 218	

6.3	Charge-Mode D/A Converter Stages /	231
6.4	Hybrid D/A Converter Stages /	234
6.5	Current-Mode D/A Converter Stages /	238
6.6	Segmented Current-Mode D/A Converter Stages /	244
	Problems /	252
	References /	254
7	ANALOG-TO-DIGITAL CONVERTERS	255
7.1	Analog-to-Digital Conversion: Basic Principles /	255
7.2	Flash A/D Converters /	263
7.3	Interpolating Flash A/D Converters /	270
7.4	Two-Step A/D Converters /	273
7.5	Successive-Approximation A/D Converters /	282
7.6	Counting and Tracking A/D Converters /	294
7.7	Integrating A/D Converters /	295
	Problems /	300
	References /	301
8	PRACTICAL CONSIDERATIONS AND DESIGN EXAMPLES	303
8.1	Practical Considerations in CMOS Op-Amp Design /	303
8.2	Op-Amp Design Techniques and Examples /	316
8.3	Comparator Design Techniques and Examples /	349
	Problems /	355
	References /	355
	INDEX	357