

INTRODUCTION TO MODERN POWER ELECTRONICS

SECOND EDITION

Andrzej M. Trzynadlowski



WILEY

A JOHN WILEY & SONS, INC., PUBLICATION

CONTENTS

Preface

xiii

1 Principles and Methods of Electric Power Conversion

1

- 1.1 What Is Power Electronics? 1
- 1.2 Generic Power Converter 3
- 1.3 Waveform Components and Figures of Merit 8
- 1.4 Phase Control 17
- 1.5 Pulse Width Modulation 22
- 1.6 Calculation of Current Waveforms 30
 - 1.6.1 Analytical Solution 31
 - 1.6.2 Numerical Solution 36
 - 1.6.3 Practical Examples: Single-Phase Diode Rectifiers 39
- 1.7 Summary 44
- Example 44
- Problems 52
- Computer Assignments 54
- Literature 57

2 Semiconductor Power Switches

59

- 2.1 General Properties of Semiconductor Power Switches 59
- 2.2 Power Diodes 61
- 2.3 Semiconrolled Switches 65
 - 2.3.1 SCRs 66
 - 2.3.2 Triacs 69
- 2.4 Fully Controlled Switches 71
 - 2.4.1 GTOs 71
 - 2.4.2 IGCTs 72
 - 2.4.3 Power BJTs 72
 - 2.4.4 Power MOSFETs 76
 - 2.4.5 IGBTs 78
- 2.5 Comparison of Semiconductor Power Switches 80

2.6	Power Modules	82
2.7	Summary	85
	Literature	86

3 Supplementary Components and Systems

87

3.1	What Are Supplementary Components and Systems?	87
3.2	Drivers	88
3.2.1	Drivers for SCRs, Triacs, and BCTs	88
3.2.2	Drivers for GTOs and IGCTs	90
3.2.3	Drivers for BJTs	91
3.2.4	Drivers for Power MOSFETs and IGBTs	93
3.3	Overcurrent Protection Schemes	95
3.4	Snubbers	97
3.4.1	Snubbers for Power Diodes, SCRs, and Triacs	102
3.4.2	Snubbers for GTOs and IGCTs	102
3.4.3	Snubbers for Transistors	103
3.4.4	Energy Recovery from Snubbers	104
3.5	Filters	107
3.6	Cooling	109
3.7	Control	110
3.8	Summary	113
	Literature	113

4 AC-to-DC Converters

115

4.1	Diode Rectifiers	115
4.1.1	Three-Pulse Diode Rectifier	115
4.1.2	Six-Pulse Diode Rectifier	117
4.2	Phase-Controlled Rectifiers	130
4.2.1	Phase-Controlled Six-Pulse Rectifier	131
4.2.2	Dual Converters	144
4.3	PWM Rectifiers	149
4.3.1	Impact of Input Filter	150
4.3.2	Principles of Pulse Width Modulation	151
4.3.3	Current-Type PWM Rectifier	158
4.3.4	Voltage-Type PWM Rectifier	164
4.4	Device Selection for Rectifiers	175
4.5	Common Applications of Rectifiers	176
4.6	Summary	180
	Examples	181
	Problems	187
	Computer Assignments	189
	Literature	191

5 AC-to-AC Converters	192
5.1 AC Voltage Controllers	192
5.1.1 Phase-Controlled Single-Phase AC Voltage Controller	192
5.1.2 Phase-Controlled Three-Phase AC Voltage Controllers	199
5.1.3 PWM AC Voltage Controllers	209
5.2 Cycloconverters	212
5.3 Matrix Converters	218
5.4 Device Selection for AC-to-AC Converters	227
5.5 Common Applications of AC-to-AC Converters	228
5.6 Summary	229
Examples	230
Problems	234
Computer Assignments	236
Literature	237
6 DC-to-DC Converters	238
6.1 Static DC Switches	238
6.2 Step-Down Choppers	241
6.2.1 First-Quadrant Chopper	243
6.2.2 Second-Quadrant Chopper	247
6.2.3 First-and-Second-Quadrant Chopper	249
6.2.4 First-and-Fourth-Quadrant Chopper	251
6.2.5 Four-Quadrant Chopper	253
6.3 Step-Up Chopper	256
6.4 Current Control in Choppers	258
6.5 Device Selection for Choppers	258
6.6 Common Applications of Choppers	261
6.7 Summary	262
Example	263
Problems	265
Computer Assignments	267
Literature	268
7 DC-to-AC Converters	269
7.1 Voltage-Source Inverters	269
7.1.1 Single-Phase Voltage-Source Inverter	270
7.1.2 Three-Phase Voltage-Source Inverter	281
7.1.3 Voltage Control Techniques for Voltage-Source Inverters	288
7.1.4 Current Control Techniques for Voltage-Source Inverters	300
7.2 Current-Source Inverters	308
7.2.1 Three-Phase Square-Wave Current-Source Inverter	308
7.2.2 Three-Phase PWM Current-Source Inverter	311

- 7.3 Multilevel Inverters 315
- 7.4 Soft-Switching Inverters 322
- 7.5 Device Selection for Inverters 330
- 7.6 Common Applications of Inverters 333
- 7.7 Summary 341
- Examples 341
- Problems 348
- Computer Assignments 349
- Literature 351

8 Switching Power Supplies

353

- 8.1 Basic Types of Switching Power Supplies 353
- 8.2 Nonisolated Switched-Mode DC-to-DC Converters 354
 - 8.2.1 Buck Converter 355
 - 8.2.2 Boost Converter 358
 - 8.2.3 Buck–Boost Converter 361
 - 8.2.4 Ćuk Converter 363
 - 8.2.5 SEPIC and Zeta Converters 367
 - 8.2.6 Comparison of Nonisolated Switched-Mode DC-to-DC Converters 368
- 8.3 Isolated Switched-Mode DC-to-DC Converters 371
 - 8.3.1 Single-Switch Isolated DC-to-DC Converters 371
 - 8.3.2 Multiple-Switch Isolated DC-to-DC Converters 375
 - 8.3.3 Comparison of Isolated Switched-Mode DC-to-DC Converters 378
- 8.4 Resonant DC-to-DC Converters 379
 - 8.4.1 Quasi-Resonant Converters 379
 - 8.4.2 Load-Resonant Converters 384
 - 8.4.3 Comparison of Resonant DC-to-DC Converters 390
- 8.5 Summary 391
- Examples 392
- Problems 395
- Computer Assignments 397
- Literature 398

9 Power Electronics and Clean Energy

399

- 9.1 Why Is Power Electronics Indispensable in Clean Energy Systems? 399
- 9.2 Solar and Wind Renewable Energy Systems 401
 - 9.2.1 Solar Energy Systems 401
 - 9.2.2 Wind Energy Systems 404
- 9.3 Fuel Cell Energy Systems 409

9.4	Electric and Hybrid Cars	411
9.5	Power Electronics and Energy Conservation	416
9.6	Summary	417
	Literature	417
Appendix A	PSpice Simulations	418
Appendix B	Fourier Series	422
Appendix C	Three-Phase Systems	426
Index		431