

Switchmode RF Power Amplifiers

Andrei Grebennikov

Nathan O. Sokal



AMSTERDAM • BOSTON • HEIDELBERG • LONDON
NEW YORK • OXFORD • PARIS • SAN DIEGO
SAN FRANCISCO • SINGAPORE • SYDNEY • TOKYO

Newnes is an imprint of Elsevier



Table of Contents

About Andrei Grebennikov	ix
About Nathan O. Sokal	xi
Preface	xiii
Acknowledgments	xvii
Chapter 1: Power-Amplifier Design Principles	1
1.1 Spectral-Domain Analysis	1
1.2 Basic Classes of Operation: A, AB, B, and C	7
1.3 Active Device Models	15
1.4 High-Frequency Conduction Angle	20
1.5 Nonlinear Effect of Collector Capacitance	27
1.6 Push-Pull Power Amplifiers	30
1.7 Power Gain and Stability	35
1.8 Parametric Oscillations	46
References.....	50
Chapter 2: Class-D Power Amplifiers	55
2.1 Switched-Mode Power Amplifiers with Resistive Load	55
2.2 Complementary Voltage-Switching Configuration	64
2.3 Transformer-Coupled Voltage-Switching Configuration	69
2.4 Symmetrical Current-Switching Configuration	71
2.5 Transformer-Coupled Current-Switching Configuration.....	74
2.6 Voltage-Switching Configuration with Reactive Load	78
2.7 Drive and Transition Time	82
2.8 Practical Class-D Power Amplifier Implementation	89
References.....	92
Chapter 3: Class-F Power Amplifiers	95
3.1 Biharmonic Operation Mode.....	95

Table of Contents

3.2 Idealized Class-F Mode.....	104
3.3 Class F with Maximally Flat Waveforms.....	108
3.4 Class F with Quarter-wave Transmission Line	115
3.5 Effect of Saturation Resistance and Shunt Capacitance.....	119
3.6 Load Networks with Lumped Elements	123
3.7 Load Networks with Transmission Lines	129
3.8 LDMOSFET Power-Amplifier Design Examples	133
3.9 Practical RF and Microwave Class-F Power Amplifiers.....	138
References.....	145
Chapter 4: Inverse Class F.....	151
4.1 Biharmonic Operation Mode.....	151
4.2 Idealized Inverse Class-F Mode.....	158
4.3 Inverse Class F with Quarter-wave Transmission Line.....	161
4.4 Load Networks with Lumped Elements	162
4.5 Load Networks with Transmission Lines	164
4.6 LDMOSFET Power-Amplifier Design Examples	167
4.7 Practical Implementation.....	172
References.....	176
Chapter 5: Class E with Shunt Capacitance.....	179
5.1 Effect of Detuned Resonant Circuit.....	179
5.2 Load Network with Shunt Capacitor and Series Filter	183
5.3 Matching with Standard Load.....	192
5.4 Effect of Saturation Resistance	195
5.5 Driving Signal and Finite Switching Time	198
5.6 Effect of Nonlinear Shunt Capacitance	206
5.7 Push-Pull Operation Mode	208
5.8 Load Network with Transmission Lines.....	213
5.9 Practical RF and Microwave Class-E Power Amplifiers and Applications.....	218
References.....	227
Chapter 6: Class E with Finite dc-Feed Inductance	233
6.1 Class E with One Capacitor and One Inductor.....	233
6.2 Generalized Class-E Load Network with Finite dc-Feed Inductance.....	241
6.3 Subharmonic Class E.....	250
6.4 Parallel-Circuit Class E	253
6.5 Even-Harmonic Class E	257
6.6 Effect of Bondwire Inductance	260
6.7 Load Network with Transmission Lines.....	261
6.8 Broadband Class E	269

6.9 Power Gain	280
6.10 CMOS Class-E Power Amplifiers.....	283
References.....	287
Chapter 7: Class E with Quarter-wave Transmission Line	293
7.1 Load Network with Parallel Quarter-wave Line	293
7.2 Optimum Load Network Parameters	301
7.3 Load Network with Zero Series Reactance	302
7.4 Matching Circuit with Lumped Elements.....	307
7.5 Matching Circuit with Transmission Lines.....	310
7.6 Load Network with Series Quarter-wave Line and Shunt Filter	312
References.....	314
Chapter 8: Alternative and Mixed-Mode High-Efficiency Power Amplifiers.....	315
8.1 Class-DE Power Amplifier.....	316
8.2 Class-E/F Power Amplifiers.....	330
8.3 Biharmonic Class- E_M Power Amplifier.....	338
8.4 Inverse Class-E Power Amplifiers	344
8.5 Harmonic Tuning Using Load-Pull Techniques	352
References.....	359
Chapter 9: Computer-Aided Design of Switched-Mode Power Amplifiers.....	363
9.1 HB-PLUS Program for Half-Bridge and Full-Bridge Direct-Coupled Voltage-Switching Class-D and Class-DE Circuits.....	363
9.2 HEPA-PLUS CAD Program for Class E.....	368
9.3 Effect of Class-E Load-Network Parameter Variations	371
9.4 HB-PLUS CAD Examples for Class D and Class DE.....	375
9.5 HEPA-PLUS CAD Example for Class E	381
9.6 Class-E Power-Amplifier Design Using SPICE.....	392
9.7 ADS Circuit Simulator and Its Applicability to Switched-Mode Class E.....	398
9.8 ADS CAD Design Example: High-Efficiency Two-Stage <i>L</i> -Band HBT Power Amplifier	403
References.....	418
Index.....	421