



THE ART OF ELECTRONICS

Second Edition

Paul Horowitz HARVARD UNIVERSITY

Winfield Hill ROWLAND INSTITUTE FOR SCIENCE, CAMBRIDGE, MASSACHUSETTS



CONTENTS

List of tables	xvi	1.18	Frequency analysis of reactive circuits	30		
Preface	xix	1.19	<i>RC</i> filters	35		
Preface to first edition	xxi	1.20	Phasor diagrams	39		
CHAPTER 1						
FOUNDATIONS 1						
Introduction	1	1.21	"Poles" and decibels per octave	40		
Voltage, current, and resistance	2	1.22	Resonant circuits and active filters	41		
1.01 Voltage and current	2	1.23	Other capacitor applications	42		
1.02 Relationship between voltage and current: resistors	4	1.24	Thévenin's theorem generalized	44		
1.03 Voltage dividers	8	Diodes and diode circuits 44				
1.04 Voltage and current sources	9	1.25	Diodes	44		
1.05 Thévenin's equivalent circuit	11	1.26	Rectification	44		
1.06 Small-signal resistance	13	1.27	Power-supply filtering	45		
Signals	15	1.28	Rectifier configurations for power supplies	46		
1.07 Sinusoidal signals	15	1.29	Regulators	48		
1.08 Signal amplitudes and decibels	16	1.30	Circuit applications of diodes	48		
1.09 Other signals	17	1.31	Inductive loads and diode protection	52		
1.10 Logic levels	19	Other passive components 53				
1.11 Signal sources	19	1.32	Electromechanical devices	53		
Capacitors and ac circuits	20	1.33	Indicators	57		
1.12 Capacitors	20	1.34	Variable components	57		
1.13 <i>RC</i> circuits: <i>V</i> and <i>I</i> versus time	23	<i>Additional exercises</i> 58				
1.14 Differentiators	25	CHAPTER 2				
1.15 Integrators	26	TRANSISTORS 61				
Inductors and transformers	28	Introduction	61			
1.16 Inductors	28	2.01	First transistor model: current amplifier	62		
1.17 Transformers	28	Some basic transistor circuits 63				
Impedance and reactance	29	2.02	Transistor switch	63		
		2.03	Emitter follower	65		

2.04 Emitter followers as voltage regulators	68	Basic FET circuits	124
2.05 Emitter follower biasing	69	3.06 JFET current sources	125
2.06 Transistor current source	72	3.07 FET amplifiers	129
2.07 Common-emitter amplifier	76	3.08 Source followers	133
2.08 Unity-gain phase splitter	77	3.09 FET gate current	135
2.09 Transconductance	78	3.10 FETs as variable resistors	138
Ebers-Moll model applied to basic transistor circuits		FET switches	140
2.10 Improved transistor model: transconductance amplifier	79	3.11 FET analog switches	141
2.11 The emitter follower revisited	81	3.12 Limitations of FET switches	144
2.12 The common-emitter amplifier revisited	82	3.13 Some FET analog switch examples	151
2.13 Biasing the common-emitter amplifier	84	3.14 MOSFET logic and power switches	153
2.14 Current mirrors	88	3.15 MOSFET handling precautions	169
Some amplifier building blocks		Self-explanatory circuits	171
2.15 Push-pull output stages	91	3.16 Circuit ideas	171
2.16 Darlington connection	94	3.17 Bad circuits	171 vskip6pt
2.17 Bootstrapping	96	CHAPTER 4	
2.18 Differential amplifiers	98	FEEDBACK AND OPERATIONAL AMPLIFIERS	
2.19 Capacitance and Miller effect	102	Introduction	175
2.20 Field-effect transistors	104	4.01 Introduction to feedback	175
Some typical transistor circuits		4.02 Operational amplifiers	176
2.21 Regulated power supply	104	4.03 The golden rules	177
2.22 Temperature controller	105	Basic op-amp circuits	177
2.23 Simple logic with transistors and diodes	107	4.04 Inverting amplifier	177
Self-explanatory circuits		4.05 Noninverting amplifier	178
2.24 Good circuits	107	4.06 Follower	179
2.25 Bad circuits	107	4.07 Current sources	180
<i>Additional exercises</i>		4.08 Basic cautions for op-amp circuits	182
CHAPTER 3		An op-amp smorgasbord	183
FIELD-EFFECT TRANSISTORS		4.09 Linear circuits	183
Introduction		4.10 Nonlinear circuits	187
3.01 FET characteristics	114	A detailed look at op-amp behavior	188
3.02 FET types	117	4.11 Departure from ideal op-amp performance	189
3.03 Universal FET characteristics	119	4.12 Effects of op-amp limitations on circuit behavior	193
3.04 FET drain characteristics	121	4.13 Low-power and programmable op-amps	210
3.05 Manufacturing spread of FET characteristics	122		

A detailed look at selected op-amp circuits	213	4.37 Bad circuits	250
		<i>Additional exercises</i>	251
4.14 Logarithmic amplifier	213	CHAPTER 5	
4.15 Active peak detector	217	ACTIVE FILTERS AND	
4.16 Sample-and-hold	220	OSCILLATORS 263	
4.17 Active clamp	221	Active filters 263	
4.18 Absolute-value circuit	221	5.01 Frequency response with <i>RC</i> filters	263
4.19 Integrators	222	5.02 Ideal performance with <i>LC</i> filters	265
4.20 Differentiators	224	5.03 Enter active filters: an overview	266
Op-amp operation with a single power supply	224	5.04 Key filter performance criteria	267
4.21 Biasing single-supply ac amplifiers	225	5.05 Filter types	268
4.22 Single-supply op-amps	225	Active filter circuits	272
Comparators and Schmitt trigger	229	5.06 VCVS circuits	273
4.23 Comparators	229	5.07 VCVS filter design using our simplified table	274
4.24 Schmitt trigger	231	5.08 State-variable filters	276
Feedback with finite-gain amplifiers	232	5.09 Twin-T notch filters	279
4.25 Gain equation	232	5.10 Gyrator filter realizations	281
4.26 Effects of feedback on amplifier circuits	233	5.11 Switched-capacitor filters	281
4.27 Two examples of transistor amplifiers with feedback	236	Oscillators	284
Some typical op-amp circuits	238	5.12 Introduction to oscillators	284
4.28 General-purpose lab amplifier	238	5.13 Relaxation oscillators	284
4.29 Voltage-controlled oscillator	240	5.14 The classic timer chip: the 555	286
4.30 JFET linear switch with R_{ON} compensation	241	5.15 Voltage-controlled oscillators	291
4.31 TTL zero-crossing detector	242	5.16 Quadrature oscillators	291
4.32 Load-current-sensing circuit	242	5.17 Wien bridge and <i>LC</i> oscillators	296
Feedback amplifier frequency compensation	242	5.18 <i>LC</i> oscillators	297
4.33 Gain and phase shift versus frequency	243	5.19 Quartz-crystal oscillators	300
4.34 Amplifier compensation methods	245	Self-explanatory circuits	303
4.35 Frequency response of the feedback network	247	5.20 Circuit ideas	303
Self-explanatory circuits	250	<i>Additional exercises</i>	303
4.36 Circuit ideas	250	CHAPTER 6	
		VOLTAGE REGULATORS AND POWER CIRCUITS 307	
		Basic regulator circuits with the classic 723 307	

6.01	The 723 regulator	307	
6.02	Positive regulator	309	
6.03	High-current regulator	311	
Heat and power design		312	
6.04	Power transistors and heat sinking	312	
6.05	Foldback current limiting	316	
6.06	Overshoot crowbars	317	
6.07	Further considerations in high-current power-supply design	320	
6.08	Programmable supplies	321	
6.09	Power-supply circuit example	323	
6.10	Other regulator ICs	325	
The unregulated supply		325	
6.11	ac line components	326	
6.12	Transformer	328	
6.13	dc components	329	
Voltage references		331	
6.14	Zener diodes	332	
6.15	Bandgap (V_{BE}) reference	335	
Three-terminal and four-terminal regulators		341	
6.16	Three-terminal regulators	341	
6.17	Three-terminal adjustable regulators	344	
6.18	Additional comments about 3-terminal regulators	345	
6.19	Switching regulators and dc-dc converters	355	
Special-purpose power-supply circuits		368	
6.20	High-voltage regulators	368	
6.21	Low-noise, low-drift supplies	374	
6.22	Micropower regulators	376	
6.23	Flying-capacitor (charge pump) voltage converters	377	
6.24	Constant-current supplies	379	
6.25	Commercial power-supply modules	382	
Self-explanatory circuits		384	
6.26	Circuit ideas	384	
6.27	Bad circuits	384	
<i>Additional exercises</i>		384	
		CHAPTER 7	
		PRECISION CIRCUITS AND LOW-NOISE TECHNIQUES	391
		Precision op-amp design techniques	391
7.01	Precision versus dynamic range	391	
7.02	Error budget	392	
7.03	Example circuit: precision amplifier with automatic null offset	392	
7.04	A precision-design error budget	394	
7.05	Component errors	395	
7.06	Amplifier input errors	396	
7.07	Amplifier output errors	403	
7.08	Auto-zeroing (chopper-stabilized) amplifiers	415	
		Differential and instrumentation amplifiers	421
7.09	Differencing amplifier	421	
7.10	Standard three-op-amp instrumentation amplifier	425	
		Amplifier noise	428
7.11	Origins and kinds of noise	430	
7.12	Signal-to-noise ratio and noise figure	433	
7.13	Transistor amplifier voltage and current noise	436	
7.14	Low-noise design with transistors	438	
7.15	FET noise	443	
7.16	Selecting low-noise transistors	445	
7.17	Noise in differential and feedback amplifiers	445	
		Noise measurements and noise sources	449
7.18	Measurement without a noise source	449	
7.19	Measurement with noise source	450	
7.20	Noise and signal sources	452	
7.21	Bandwidth limiting and rms voltage measurement	453	
7.22	Noise potpourri	454	

Interference: shielding and grounding	455	Monostable multivibrators	517
7.23 Interference	455	8.20 One-shot characteristics	517
7.24 Signal grounds	457	8.21 Monostable circuit example	519
7.25 Grounding between instruments	457	8.22 Cautionary notes about monostables	519
Self-explanatory circuits	466	8.23 Timing with counters	522
7.26 Circuit ideas	466	Sequential functions available as ICs	523
<i>Additional exercises</i>	466	8.24 Latches and registers	523
CHAPTER 8		8.25 Counters	524
DIGITAL ELECTRONICS	471	8.26 Shift registers	525
Basic logic concepts	471	8.27 Sequential PALs	527
8.01 Digital versus analog	471	8.28 Miscellaneous sequential functions	541
8.02 Logic states	472	Some typical digital circuits	544
8.03 Number codes	473	8.29 Modulo- n counter: a timing example	544
8.04 Gates and truth tables	478	8.30 Multiplexed LED digital display	546
8.05 Discrete circuits for gates	480	8.31 Sidereal telescope drive	548
8.06 Gate circuit example	481	8.32 An n -pulse generator	548
8.07 Assertion-level logic notation	482	Logic pathology	551
TTL and CMOS	484	8.33 dc problems	551
8.08 Catalog of common gates	484	8.34 Switching problems	552
8.09 IC gate circuits	485	8.35 Congenital weaknesses of TTL and CMOS	554
8.10 TTL and CMOS characteristics	486	Self-explanatory circuits	556
8.11 Three-state and open-collector devices	487	8.36 Circuit ideas	556
Combinational logic	490	8.37 Bad circuits	556
8.12 Logic identities	491	<i>Additional exercises</i>	556
8.13 Minimization and Karnaugh maps	492	CHAPTER 9	
8.14 Combinational functions available as ICs	493	DIGITAL MEETS ANALOG	565
8.15 Implementing arbitrary truth tables	500	CMOS and TTL logic interfacing	565
Sequential logic	504	9.01 Logic family chronology	565
8.16 Devices with memory: flip-flops	504	9.02 Input and output characteristics	570
8.17 Clocked flip-flops	507	9.03 Interfacing between logic families	572
8.18 Combining memory and gates: sequential logic	512	9.04 Driving CMOS and TTL inputs	575
8.19 Synchronizer	515	9.05 Driving digital logic from comparators and op-amps	577

9.06 Some comments about logic inputs	579	9.33 Feedback shift register sequences	655
9.07 Comparators	580	9.34 Analog noise generation from maximal-length sequences	658
9.08 Driving external digital loads from CMOS and TTL	582	9.35 Power spectrum of shift register sequences	658
9.09 NMOS LSI interfacing	588	9.36 Low-pass filtering	660
9.10 Opto-electronics	590	9.37 Wrap-up	661
Digital signals and long wires	599	9.38 Digital filters	664
9.11 On-board interconnections	599	Self-explanatory circuits	667
9.12 Intercard connections	601	9.39 Circuit ideas	667
9.13 Data buses	602	9.40 Bad circuits	668
9.14 Driving cables	603	<i>Additional exercises</i>	668
Analog/digital conversion	612	 CHAPTER 10	
9.15 Introduction to A/D conversion	612	MICROCOMPUTERS 673	
9.16 Digital-to-analog converters (DACs)	614	Minicomputers, microcomputers, and microprocessors	673
9.17 Time-domain (averaging) DACs	618	10.01 Computer architecture	674
9.18 Multiplying DACs	619	A computer instruction set	678
9.19 Choosing a DAC	619	10.02 Assembly language and machine language	678
9.20 Analog-to-digital converters	621	10.03 Simplified 8086/8 instruction set	679
9.21 Charge-balancing techniques	626	10.04 A programming example	683
9.22 Some unusual A/D and D/A converters	630	Bus signals and Interfacing	684
9.23 Choosing an ADC	631	10.05 Fundamental bus signals: data, address, strobe	684
Some A/D conversion examples	636	10.06 Programmed I/O: data out	685
9.24 16-Channel A/D data-acquisition system	636	10.07 Programmed I/O: data in	689
9.25 3½-Digit voltmeter	638	10.08 Programmed I/O: status registers	690
9.26 Coulomb meter	640	10.09 Interrupts	693
Phase-locked loops	641	10.10 Interrupt handling	695
9.27 Introduction to phase-locked loops	641	10.11 Interrupts in general	697
9.28 PLL design	646	10.12 Direct memory access	701
9.29 Design example: frequency multiplier	647	10.13 Summary of the IBM PC's bus signals	704
9.30 PLL capture and lock	651	10.14 Synchronous versus asynchronous bus communication	707
9.31 Some PLL applications	652	10.15 Other microcomputer buses	708
Pseudo-random bit sequences and noise generation	655	10.16 Connecting peripherals to the computer	711
9.32 Digital noise generation	655		

Software system concepts	714	CHAPTER 12	
10.17 Programming	714	ELECTRONIC CONSTRUCTION	
10.18 Operating systems, files, and use of	716	TECHNIQUES	827
		Prototyping methods	827
Data communications concepts	719	12.01 Breadboards	827
10.19 Serial communication and		12.02 PC prototyping boards	828
ASCII	720	12.03 Wire-Wrap panels	828
10.20 Parallel communication:		Printed circuits	830
Centronics, SCSI, IPI,		12.04 PC board fabrication	830
GPIB (488)	730	12.05 PC board design	835
10.21 Local area networks	734	12.06 Stuffing PC boards	838
10.22 Interface example: hardware data		12.07 Some further thoughts on PC	
packing	736	boards	840
10.23 Number formats	738	12.08 Advanced techniques	841
CHAPTER 11		Instrument construction	852
MICROPROCESSORS	743	12.09 Housing circuit boards in an	
A detailed look at the 68008	744	instrument	852
11.01 Registers, memory, and I/O	744	12.10 Cabinets	854
11.02 Instruction set and		12.11 Construction hints	855
addressing	745	12.12 Cooling	855
11.03 Machine-language		12.13 Some electrical hints	858
representation	750	12.14 Where to get components	860
11.04 Bus signals	753	CHAPTER 13	
A complete design example: analog		HIGH-FREQUENCY AND HIGH-SPEED	
signal averager	760	TECHNIQUES	863
11.05 Circuit design	760	High-frequency amplifiers	863
11.06 Programming: defining the		13.01 Transistor amplifiers at high	
task	774	frequencies: first look	863
11.07 Programming: details	777	13.02 High-frequency amplifiers: the ac	
11.08 Performance	796	model	864
11.09 Some afterthoughts	797	13.03 A high-frequency calculation	
Micropocessor support chips	799	example	866
11.10 Medium-scale integration	800	13.04 High-frequency amplifier	
11.11 Peripheral LSI chips	802	configurations	868
11.12 Memory	812	13.05 A wideband design example	869
11.13 Other microprocessors	820	13.06 Some refinements to the ac	
11.14 Emulators, development systems,		model	872
logic analyzers, and evaluation		13.07 The shunt-series pair	872
boards	821	13.08 Modular amplifiers	873
		Radiofrequency circuit elements	879
		13.09 Transmission lines	879

13.10 Stubs, baluns, and transformers	881	Power sources	920
13.11 Tuned amplifiers	882	14.02 Battery types	920
13.12 Radiofrequency circuit elements	884	14.03 Wall-plug-in units	931
13.13 Measuring amplitude or power	888	14.04 Solar cells	932
Radiofrequency communications:		14.05 Signal currents	933
AM	892	Power switching and micropower regulators	
13.14 Some communications concepts	892	14.06 Power switching	938
13.15 Amplitude modulation	894	14.07 Micropower regulators	941
13.16 Superheterodyne receiver	895	14.08 Ground reference	944
Advanced modulation methods		14.09 Micropower voltage references and temperature sensors	948
13.17 Single sideband	897	Linear micropower design techniques	
13.18 Frequency modulation	898	14.10 Problems of micropower linear design	950
13.19 Frequency-shift keying	900	14.11 Discrete linear design example	950
13.20 Pulse-modulation schemes	900	14.12 Micropower operational amplifiers	951
Radiofrequency circuit tricks		14.13 Micropower comparators	965
13.21 Special construction techniques	902	14.14 Micropower timers and oscillators	965
13.22 Exotic RF amplifiers and devices	903	Micropower digital design	
High-speed switching		904	969
13.23 Transistor model and equations	905	14.15 CMOS families	969
13.24 Analog modeling tools	908	14.16 Keeping CMOS low power	970
Some switching-speed examples		14.17 Micropower microprocessors and peripherals	974
13.25 High-voltage driver	909	14.18 Microprocessor design example: degree-day logger	978
13.26 Open-collector bus driver	910	Self-explanatory circuits	
13.27 Example: photomultiplier preamp	911	985	
Self-explanatory circuits		14.19 Circuit ideas	985
13.28 Circuit ideas	913	CHAPTER 15	
<i>Additional exercises</i>	913	MEASUREMENTS AND SIGNAL PROCESSING	
CHAPTER 14		987	
LOW-POWER DESIGN	917	Overview	
Introduction		987	
14.01 Low-power applications	918	Measurement transducers	
		988	
		15.01 Temperature	988
		15.02 Light level	996
		15.03 Strain and displacement	1001

15.04 Acceleration, pressure, force, velocity 1004	APPENDICES 1043
15.05 Magnetic field 1007	Appendix A The oscilloscope 1045
15.06 Vacuum gauges 1007	Appendix B Math review 1050
15.07 Particle detectors 1008	Appendix C The 5% resistor color code 1053
15.08 Biological and chemical voltage probes 1012	Appendix D 1% Precision resistors 1054
Precision standards and precision measurements 1016	Appendix E How to draw schematic diagrams 1056
15.09 Frequency standards 1016	Appendix F Load lines 1059
15.10 Frequency, period, and time- interval measurements 1019	Appendix G Transistor saturation 1062
15.11 Voltage and resistance standards and measurements 1025	Appendix H <i>LC</i> Butterworth filters 1064
Bandwidth-narrowing techniques 1026	Appendix I Electronics magazines and journals 1068
15.12 The problem of signal-to-noise ratio 1026	Appendix J IC prefixes 1069
15.13 Signal averaging and multichannel averaging 1026	Appendix K Data sheets 1072
15.14 Making a signal periodic 1030	2N4400-1 NPN transistor 1073
15.15 Lock-in detection 1031	LF411-12 JFET operational amplifier 1078
15.16 Pulse-height analysis 1034	LM317 3-terminal adjustable regulator 1086
15.17 Time-to-amplitude converters 1035	Bibliography 1095
Spectrum analysis and Fourier transforms 1035	Index 1101
15.18 Spectrum analyzers 1035	
15.19 Off-line spectrum analysis 1038	
Self-explanatory circuits 1038	
15.20 Circuit ideas 1038	