

THE SPICE BOOK

Andrei Vladimirescu



John Wiley & Sons, Inc.

New York Chichester Brisbane Toronto Singapore

CONTENTS

Introduction

SPICE—THE THIRD DECADE

I.1 THE EARLY DAYS OF SPICE	1
I.2 SPICE IN THE 1970s	2
I.3 SPICE IN THE 1980s	4
I.4 SPICE IN THE 1990s	7
I.5 CONCLUSION	8
REFERENCES	9

Chapter One

INTRODUCTION TO ELECTRICAL COMPUTER SIMULATION

12

1.1 PURPOSE OF COMPUTER SIMULATION OF ELECTRICAL CIRCUITS	12
1.2 WHAT IS SPICE?	14
1.3 USER INTERACTION WITH SPICE AND THE COMPUTER	17
1.3.1 Electric Circuit Specification—The SPICE Input	18
1.3.2 SPICE Simulation, DC Analysis	22
1.3.3 SPICE Results for AC and TRAN Analyses	28
1.4 SUMMARY	36
REFERENCES	37

Chapter Two

CIRCUIT ELEMENT AND NETWORK DESCRIPTION	38
2.1 ELEMENTS, MODELS, NODES, AND CONVENTIONS	38
2.2 TWO-TERMINAL ELEMENTS	39
2.2.1 Resistors	40
2.2.2 Semiconductor Resistors (SPICE3)	41
2.2.3 Capacitors	42
2.2.4 Semiconductor Capacitor (SPICE3)	44
2.2.5 Inductors	45
2.2.6 Independent Bias and Signal Sources	46
2.2.6.1 Pulse Function	48
2.2.6.2 Sinusoidal Function	50
2.2.6.3 Frequency-Modulated Sinusoidal Function	51
2.2.6.4 Exponential Function	53
2.2.6.5 Piecewise Linear Function	54
2.3 MULTITERMINAL ELEMENTS	56
2.3.1 Coupled (Mutual) Inductors	56
2.3.2 Dependent (Controlled) Sources	58
2.3.2.1 Voltage-Controlled Current Source (VCCS)	61
2.3.2.2 Voltage-Controlled Voltage Source (VCVS)	62
2.3.2.3 Current-Controlled Current Source (CCCS)	63
2.3.2.4 Current-Controlled Voltage Source (CCVS)	64
2.3.3 Switches	65
2.3.4 Transmission Lines	68
2.4 SUMMARY	71
REFERENCES	72

Chapter Three

SEMICONDUCTOR-DEVICE ELEMENTS	73
3.1 INTRODUCTION	73
3.2 DIODES	75
3.3 BIPOLAR JUNCTION TRANSISTORS	78
3.3.1 DC Model	79
3.3.2 Dynamic and Small-Signal Models	83
3.3.3 Model Parameters	86
3.4 JUNCTION FIELD EFFECT TRANSISTORS (JFETs)	96
3.5 METAL-OXIDE-SEMICONDUCTOR FIELD EFFECT TRANSISTORS (MOSFETs)	101
3.5.1 DC Model	102
3.5.2 Dynamic and Small-Signal Models	103
3.5.3 Model Parameters	108

3.6 METAL-SEMICONDUCTOR FIELD EFFECT TRANSISTORS (MESFETs)	109
3.7 SUMMARY	112
REFERENCES	113

Chapter Four

DC ANALYSIS	114
4.1 ANALYSIS OVERVIEW	114
4.1.1 Simulation Modes and Analysis Types	114
4.1.2 Result Processing and Output Variables	115
4.1.3 Analysis Parameters: Temperature	116
4.2 OPERATING (BIAS) POINT	117
4.3 DC TRANSFER CURVES	125
4.4 SMALL-SIGNAL TRANSFER FUNCTION	129
4.5 SENSITIVITY ANALYSIS	133
4.6 NODE VOLTAGE INITIALIZATION	136
4.7 SUMMARY	139
REFERENCES	140

Chapter Five

AC ANALYSIS	141
5.1 INTRODUCTION	141
5.2 AC FREQUENCY SWEEP	142
5.3 NOISE ANALYSIS	149
5.4 DISTORTION ANALYSIS	157
5.5 POLE-ZERO ANALYSIS	164
5.6 SUMMARY	165
REFERENCES	167

Chapter Six

TIME-DOMAIN ANALYSIS	168
6.1 ANALYSIS DESCRIPTION	168
6.2 TRANSIENT ANALYSIS	169

6.3 INITIAL CONDITIONS	180
6.4 FOURIER ANALYSIS	184
6.5 SUMMARY	191
REFERENCES	192

Chapter Seven

FUNCTIONAL AND HIERARCHICAL SIMULATION	193
7.1 HIGH-LEVEL CIRCUIT DESCRIPTION	193
7.2 SPICE SUBCIRCUIT AND CIRCUIT HIERARCHY	194
7.2.1 .SUBCKT Definition	194
7.2.2 Subcircuit Instance	195
7.2.3 Circuit Hierarchy	195
7.3 IDEAL MODELS	204
7.3.1 Operational Amplifiers	205
7.3.2 Logic Gates and Digital Circuits	209
7.4 FUNCTIONAL MODELS	213
7.4.1 Nonlinear (Arbitrary-Function) Controlled Sources in SPICE3	213
7.4.2 Analog Function Blocks	215
7.4.3 Digital Function Blocks	223
7.4.4 Equation Solution	224
7.5 MACRO-MODELS	227
7.5.1 The Opamp Macro-Model	228
7.6 SUMMARY	239
REFERENCES	240

Chapter Eight

DISTORTION ANALYSIS	241
8.1 DISTORTION IN SEMICONDUCTOR CIRCUITS	241
8.2 SMALL-SIGNAL DISTORTION ANALYSIS	241
8.2.1 High-Frequency Distortion	242
8.2.2 Distortion in a One-Transistor Amplifier	244
8.3 LARGE-SIGNAL DISTORTION ANALYSIS	263
8.3.1 One-Transistor Amplifier Distortion	263
8.3.2 Single-Device Mixer Analysis	265
8.4 SUMMARY	276
REFERENCES	277

Chapter Nine

<i>SPICE ALGORITHMS AND OPTIONS</i>	278
9.1 OVERVIEW OF ALGORITHMS	278
9.2 DC SOLUTION OF LINEAR CIRCUITS	280
9.2.1 Circuit Equation Formulation: Modified Nodal Equations	280
9.2.2 Accuracy and SPICE Options	285
9.3 DC SOLUTION OF NONLINEAR CIRCUITS	291
9.3.1 Newton-Raphson Iteration	291
9.3.2 Convergence and SPICE Options	296
9.4 TIME-DOMAIN SOLUTION	298
9.4.1 Numerical Integration	299
9.4.2 Integration Algorithms in SPICE, Accuracy, and Options	307
9.5 SUMMARY OF OPTIONS	312
9.5.1 Analysis Summary	312
9.5.2 Linear Equation Options	314
9.5.3 Nonlinear Solution Options	315
9.5.4 Numerical Integration	315
9.5.5 Miscellaneous Options	316
REFERENCES	317

Chapter Ten

<i>CONVERGENCE ADVICE</i>	319
10.1 INTRODUCTION	319
10.2 COMMON CAUSES OF SOLUTION FAILURE	320
10.2.1 Circuit Description	320
10.2.2 Component Values	326
10.3 DC CONVERGENCE	330
10.4 TIME-DOMAIN CONVERGENCE	353
10.5 CIRCUIT-SPECIFIC CONVERGENCE	362
10.5.1 Oscillators	362
10.5.2 BJT versus MOSFET Specifics	367
10.5.3 Convergence of Large Circuits	373
10.6 SUMMARY	375
REFERENCES	377

APPENDIX A

<i>SEMICONDUCTOR-DEVICE MODELS</i>	378
A.1 DIODE	378
A.1.1 DC, Transient, and AC Models	379
A.1.2 Temperature Effects	379
A.1.3 Noise Model	380
A.2 BIPOLAR JUNCTION TRANSISTOR	380
A.2.1 DC Model	381
A.2.2 Transient and AC Models	382
A.2.3 Temperature Effects	383
A.2.4 Noise Model	383
A.3 MOSFET	384
A.3.1 DC Model	385
A.3.2 Transient and AC Models	389
A.3.3 Temperature Model	390
A.3.4 Noise Model	390
REFERENCES	390

APPENDIX B

<i>ERROR MESSAGES</i>	391
B.1 GENERAL SYNTAX ERRORS	391
B.2 MULTITERMINAL ELEMENT ERRORS	392
B.3 SOURCE SPECIFICATION ERRORS	392
B.4 ELEMENT, SEMICONDUCTOR-DEVICE, AND MODEL ERRORS	393
B.5 CIRCUIT TOPOLOGY ERRORS	394
B.6 SUBCIRCUIT DEFINITION ERRORS	394
B.7 ANALYSIS ERRORS	395
B.8 MISCELLANEOUS ERRORS	398

APPENDIX C

<i>SPICE STATEMENTS</i>	399
C.1 ELEMENT STATEMENTS	399
C.2 GLOBAL STATEMENTS	400
C.3 CONTROL STATEMENTS	401

APPENDIX D**GEAR INTEGRATION FORMULAS****402****APPENDIX E****SPICE INPUT DECK****403****INDEX****405**