

# The Switching Function: Analysis of Power Electronic Circuits

By Dr C.C. Marouchos

The Institution of Electrical Engineers

---

## Contents

---

<b>Part 1</b>	<b>The switching function</b>	<b>1</b>
1	The switching function: Application and properties	3
1.1	Introduction	3
1.2	Application of the switching function technique	3
1.3	Properties of the switching function	6
2	Voltage–current relations in switched circuits	17
2.1	Single switch	18
2.2	Parallel switches	19
2.3	Parallel switched-resistors	20
2.4	Switched-inductors	21
2.5	Parallel switched-capacitors	24
2.6	Kirchoff’s First Law (current law)	27
2.7	Kirchoff’s Second Law (voltage)	27
2.8	Superposition theorem in switched circuits	29
2.9	Current sharing in a parallel RC switched network	31
3	Pulse width modulation	35
3.1	Sinusoidally modulated PWM signal – unipolar	36
3.2	The rectified sine-wave PWM signal	39
3.3	The PWM signal of a composite function	43
3.4	PWM sine-wave – bipolar square wave modulation	45
<b>Part 2</b>	<b>AC to DC conversion</b>	<b>49</b>
4	Analysis of the single phase ac to dc phase controlled converter with R–L load	51
4.1	Introduction	51
4.2	Mathematical modelling	51
4.3	Analysis	55
5	The single phase full-wave diode rectifier – RC load	65
5.1	Introduction	65
5.2	Mathematical modelling	65

5.3	Analysis	72
5.4	Neutral current in three phase systems	77
6	The three-phase half-wave phase controlled converter	83
6.1	Introduction	83
6.2	Mathematical modelling of the three-phase half-wave phase controlled converter	83
6.3	Analysis	91
6.4	Results	98
7	The three-phase full-wave phase controlled rectifier	101
7.1	Introduction	101
7.2	The mathematical modelling of the three-phase full-wave controlled rectifier circuit	101
7.3	Analysis of three-phase full-wave phase controlled rectifier	111
8	Overlap in ac to dc three-phase converters	121
8.1	Introduction	121
8.2	Operation and modes	122
8.3	Analysis	132
<b>Part 3</b>	<b>DC to DC converters</b>	<b>135</b>
9	The step down converter	137
9.1	Introduction	137
9.2	Mathematical modelling of the step down converter	137
10	The step up or boost converter	145
10.1	Introduction	145
10.2	Mathematical modelling of the dc to dc step up (boost) converter	145
10.3	Analysis	152
11	The buck boost dc to dc converter	163
11.1	Introduction	163
11.2	Mathematical modelling of the buck boost converter	164
11.3	Analysis of the buck boost converter	168
12	The CUK dc to dc converter	175
12.1	Introduction	175
12.2	Mathematical modelling of the CUK dc to dc converter	175
12.3	Analysis of the CUK dc to dc converter	180
13	The PWM full bridge dc to dc converter	187
13.1	Introduction	187
13.2	Operation and modes of the PWM full bridge dc to dc converter: bipolar operation	188
13.3	Analysis of the PWM full bridge dc to dc converter: bipolar operation	189
13.4	Operation and modes of the PWM full bridge dc to dc converter: unipolar operation	193

13.5	Analysis of the PWM full bridge dc to dc converter: unipolar operation	197
<b>Part 4</b>	<b>Frequency changers</b>	<b>203</b>
14	Three by three matrix converter	205
14.1	Introduction	205
14.2	Operation and mathematical model	206
14.3	The modes of operation and the switching functions	208
14.4	Analysis of the matrix converter as a three-phase to three-phase system	211
14.5	The matrix converter as an ac to dc voltage converter	218
15	The single pulse PWM inverter	223
15.1	Introduction	223
15.2	Operation and modes of the circuit	223
15.3	The mathematical model and analysis	229
16	The sinusoidally PWM inverter	235
16.1	Introduction	235
16.2	Mathematical modelling	235
16.3	Analysis	241
17	The envelope cyclo-converter	245
17.1	Introduction	245
17.2	The mathematical model	245
17.3	The switching functions	246
<b>Part 5</b>	<b>Active filters</b>	<b>249</b>
18	The thyristor-controlled reactor	251
18.1	Introduction	251
18.2	The single reactor arrangement	251
18.3	The two reactor arrangement	257
19	The switched capacitor active filters	263
19.1	Introduction	263
19.2	The general model for the switched-capacitor active filters	263
19.3	The switching functions	265
19.4	The line current	266
19.5	The double-switch double-capacitor	266
19.6	Reactive power generation	266
20	The inverter configuration active filter	271
20.1	Introduction	271
20.2	Operation and analysis	271
21	Single phase rectification with active line shaping	275
21.1	Mathematical modelling of the active shaping circuit	275
<b>Discussion</b>		<b>289</b>
<b>References</b>		<b>291</b>
<b>Index</b>		<b>293</b>