

Open access • Proceedings Article • DOI:10.1109/ISCAS.2010.5537475

# 32-bit Configurable bias current generator with sub-off-current capability — Source link 🖸

Tobi Delbruck, R Berner, P. Lichtsteiner, Carlos Dualibe Institutions: University of Zurich Published on: 03 Aug 2010 - International Symposium on Circuits and Systems Topics: Current mirror, Biasing, Voltage source, Cascode and Transistor

#### Related papers:

- Neuromorphic Electronic Circuits for Building Autonomous Cognitive Systems
- Synaptic Dynamics in Analog VLSI
- Neuromorphic Silicon Neuron Circuits
- Neuromorphic electronic systems
- A 128 \$\times\$ 128 120 dB 15 \$\mu\$ s Latency Asynchronous Temporal Contrast Vision Sensor





Zurich Open Repository and Archive University of Zurich Main Library Strickhofstrasse 39 CH-8057 Zurich www.zora.uzh.ch

Year: 2010

### 32-bit Configurable bias current generator with sub-off-current capability

Delbruck, T ; Berner, R ; Lichtsteiner, P ; Dualibe, C

Abstract: A fully configurable bias current reference is described. The output of the current reference is a gate voltage which produces a desired current. For each daisy-chained bias, 32 bits of configuration are divided into 22 bits of bias current, 6 bits of active-mirror buffer current, and 4 bits of other configuration. Configuration of each bias allows specifying the type of transistor (nfet or pfet), whether the bias is enabled or weakly pulled to the rail, whether the bias is for a cascode, and whether the bias transistor uses a shifted source (SS) voltage for sub-off-current biasing. In addition, the current reference integrates a pair of voltage regulators that generate stable voltage sources near the rails, suitable for the SS current references. Measurements from fabricated current references built in 180 nm CMOS show that the reference achieves at least 110 dB (22-bit) dynamic range and reaches 160dB when power-rail gate biasing is included. Generated bias currents reach at least 30x smaller current than the transistor off-current. Each current reference occupies an area of  $620 \times 50$  um2. The design kit schematics and layout are open-sourced.

DOI: https://doi.org/10.1109/ISCAS.2010.5537475

Posted at the Zurich Open Repository and Archive, University of Zurich ZORA URL: https://doi.org/10.5167/uzh-47168 Conference or Workshop Item

Originally published at:

Delbruck, T; Berner, R; Lichtsteiner, P; Dualibe, C (2010). 32-bit Configurable bias current generator with sub-off-current capability. In: Circuits and Systems (ISCAS), Proceedings of 2010 IEEE International Symposium, Paris, France, 30 May 2010 - 2 June 2010, 1647-1650. DOI: https://doi.org/10.1109/ISCAS.2010.5537475

## 32-bit Configurable Bias Current Generator with Sub-Off-Current Capability

Tobi Delbruck<sup>1</sup>, Senior Member, IEEE, Raphael Berner<sup>1</sup>, Student Member, IEEE,

Patrick Lichtsteiner<sup>1</sup>, Member, IEEE, Carlos Dualibe<sup>2</sup>

<sup>1</sup>Inst. of Neuroinformatics, University of Zurich and ETH Zürich, Switzerland, <sup>2</sup>Freescale Semiconductor, Brazil

#### ABSTRACT

A fully configurable bias current reference is described. The output of the current reference is a gate voltage which produces a desired current. For each daisychained bias, 32 bits of configuration are divided into 22 bits of bias current, 6 bits of active-mirror buffer current, and 4 bits of other configuration. Configuration of each bias allows specifying the type of transistor (nfet or pfet), whether the bias is enabled or weakly pulled to the rail, whether the bias is for a cascode, and whether the bias transistor uses a shifted source (SS) voltage for sub-offcurrent biasing. In addition, the current reference integrates a pair of voltage regulators that generate stable voltage sources near the rails, suitable for the SS current Measurements from fabricated current references. references built in 180 nm CMOS show that the reference achieves at least 110 dB (22-bit) dynamic range and reaches 160dB when power-rail gate biasing is included. Generated bias currents reach at least 30x smaller current than the transistor off-current. Each current reference occupies an area of  $620x50 \text{ um}^2$ . The design kit schematics and layout are open-sourced.

#### **1. INTRODUCTION**

Mixed signal chip designs sometimes require a wide range of internal currents for biasing. Sometimes during development these are controlled by gate voltages with the disadvantage of severe process and temperature sensitivity, and also supply voltage sensitivity if a stable reference is not used. Parts of the design may run at bandwidth or slew rates of 100MHz while others may run at 1Hz, requiring bias currents that span 8 decades. We previously reported bias current references for generating fixed bias currents [1] over this very wide range. Our experience showed that most chip designs could not be adequately simulated to allow for first-shot fixed biasing. We next developed a 24-bit digitally-programmable bias current generator [2] along with extensive PCB, firmware, and host software infrastructure [3]. Although successful on [4] and several other chips, we learned that these programmable biases placed strain on the designers by forcing them to correctly tie the proper nfet or pfet bias output to their circuit, and not allowing them to disable the on-chip biasing under software control, and not allowing control of the bias voltage buffer strength.

Designers also often wished to tie biases to ground or Vdd explicitly. It proved necessary to still bring the bias voltages out to pads and provide external overriding capability at the board level. Also, given decreasing threshold voltage and consequent increase in transistor off current, we wanted to incorporate the notion of shifted-source (SS) biasing [5, 6] in a fully integrated form, to allow chips to utilize very small currents and long time constants without using off-chip voltage sources.

Here we extend this previous work to generalize the bias current reference to add full configuration capability. We also added the capability of generating sub-off-current values and the required voltage references and regulators to use these SS current sources.

In the rest of this paper we first review SS operation, and describe the new reference and regulator. We then describe the overall bias current architecture, and describe the new bias buffer circuit which supports full configurability. We conclude with characterization results and discussion.

#### 2. SHIFTED SOURCE BIASING

In the following we use the term *off current* to mean the saturation current of a transistor with  $V_{gs}=V_{sb}=0$ , i.e. the pre-exponential  $I_0$  in the saturated subthreshold transistor drain current:  $I_{ds} = I_0 \exp(\kappa V_{gs} / U_T)$ , where  $\kappa$ is the back-gate coefficient and  $U_T$  is the thermal voltage.  $I_0$  is typically several orders of magnitude larger than the junction leakage substrate current. Normally a current mirror can only copy currents down to a few times  $I_0$ .

References [5, 6] presented the principle of SS biasing. The idea is to arrange to allow a current mirror to operate with its gate voltage below its common source voltage. A level-shifting source follower tied from the current mirror drain input to the common gate voltage  $V_g$  holds the drain-source voltage of the input transistor in saturation

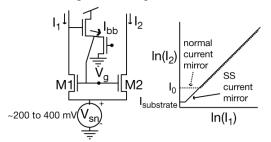


Fig. 1 Principle of shifted-source (SS) current mirror.

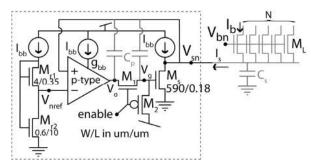


Fig. 2 Shifted-source reference and regulator circuit.

(Fig. 1) even for very small  $I_1$ . The common sources of both M1 and M2 are held at regulated voltage  $V_{sn}$  which is typically 200mV to 400 mV above ground. This SS allows  $V_g$  to drop below  $V_{sn}$  for very small (sub-off) input currents. The current mirror is then capable of copying currents several decades smaller than  $I_0$ . To build a complete system, complementary pairs of such mirrors are required with supplies  $V_{sn}$  and  $V_{sp}$ .

[5, 6] did not propose a means for generating or regulating  $V_{sn}$  and  $V_{sp}$ . The difficulty is that the required voltages are quite close to the power rails. We propose generating the  $V_{sn}$  regulated voltage with the low-dropout regulator circuit [7] in Fig. 2, with the complementary circuit for  $V_{sp}$ . The reference voltage  $V_{nref}$  is generated by the split-gate diode-connected pair  $M_{r1}$  and  $M_{r2}$ .  $M_{r1}$  is wide and short and  $M_{r2}$  is long and narrow.  $M_{r2}$  runs in triode mode, acting as a load resistance and thus allowing generation of a reference voltage of 200mV to 400mV. The programmable buffer bias current sources  $I_{bb}$  sets  $V_{nref}$  and biases the 5T p-type OTA error amplifier, which acts as an opamp. The wide pass transistor  $M_s$  sinks the current  $I_s$  supplied by the N external nmos sources  $M_L$ . The OTA drives  $V_g$  (when the regulator is enabled) in

instability since they provide a positive feedback path from  $V_o$  to  $V_{sn}$ . A large  $C_s/C_p$  capacitive divider ratio reduces the feedback gain to stabilize the regulator.

#### **3. BIAS GENERATOR ARCHITECTURE**

We now describe the overall architecture of the bias generator. Fig. 3 is a block diagram showing the interface between an off-chip controller and a set of N independent bias currents, along with the architecture of a single bias. A master current I<sub>m</sub> with PTAT characteristics which is generated by a single Widlar bootstrapped mirror [1] is shared over all N biases. This PTAT source has proved to be good for our applications, where we generally want constant-g<sub>m</sub> performance from the subthreshold circuits. The 32-bit configuration word for a bias is shifted into shift register stages (SR) and then latched (L). It is partitioned into 22 bits for the bias current  $I_{\rm b}$ , 6 bits for the bias buffer current  $I_{\mbox{\scriptsize bb}},$  and 4 bits of other configuration. Biases are daisy-chained (15 in the case of the present implementation). Bits are loaded on the IN0 bit while clocking CLOCK; after all bits have been loaded, LATCH is toggled to activate new settings.

The configuration bits operate inside the bias buffer circuit BB (Fig. 4). This complicated circuit has many switches that enable various modes, but the principle of operation is simply based on a complementary pair of active SS mirrors as in Fig. 1. The flow of signal current is shown by the dashed arrows. The input to the buffer circuit is the programmed fraction  $I_b$  of  $I_m$ , and the output is a buffered bias voltage  $V_{bias}$ . Internal buffer currents are set by  $I_{bb}$ , which is derived from a 6-bit fraction of  $I_m$ . The configuration bits (DISABLE, CASC, SSEN, NBIAS and the global power-down bit PD) operate switches that switch in or out various parts of the circuit. For example,

negative feedback to regulate V<sub>sn</sub> to V<sub>nref</sub>. If  $V_{sn}$  is too low then  $V_g$  is decreased, and vice versa. The Ibb current source onto V<sub>sn</sub> holds V<sub>sn</sub> up when I<sub>s</sub> sourced externally becomes very small. It also sets the minimum transconductance of M<sub>s</sub>. Switches  $M_1$  and  $M_2$ allow disabling the SS regulator and tying  $V_{sn}$ to ground by disconnecting the OTA and tying  $V_g$  to Vdd. Parasitic capacitances  $C_p$  (especially across the drain-gate capacitance of  $M_s$ ) can lead to

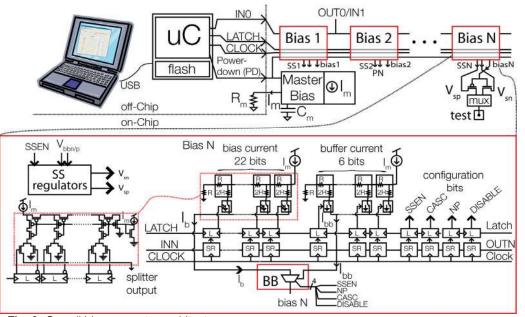


Fig. 3 Overall bias generator architecture.

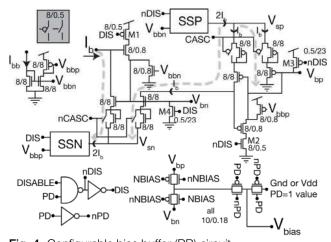


Fig. 4 Configurable bias buffer (BB) circuit.

if an n-type normal bias is desired with shifted-source voltage level, then DISABLE=0 enables the SS regulators, NBIAS=1 enables the n-type output, and CASC=0 shorts across the diode-connected loads in the active mirrors. M1 and M2 are added to prevent parasitic floating node states when the bias is disabled, where intermediate nodes can fight. M3 and M4 weakly clamp the bias voltage to the rail when DISABLE=1. The default state with PD=1 is set by tying V<sub>bias</sub> to Gnd or Vdd in layout, which can be important for power-up state of the chip.

#### 4. IMPLEMENTATION

This bias generator was implemented on a vision sensor in a 180nm 4M 2P MIM image sensor process (UMC CIS 180). Fig. 5 shows a partial micrograph of the chip with layout overlaid and a close up of the layout of the bias buffer/references/regulators layout. Each bias occupies an area of 620 um x 50 um= $0.0033 \text{ mm}^2$ , which is about 80% of a 200x200 um pad. To prevent parasitic photodiode action at low currents, the entire circuit is covered with image sensor black shield and low current parts of the circuit are covered with metal; pfets and nwell guard rings around nfets provide additional shielding.

#### 5. CHARACTERIZATION

Bias currents were measured under GPIB computer control of a Keithley 6430 source-measure unit. An onchip nfet and pfet were included with common gate tied to

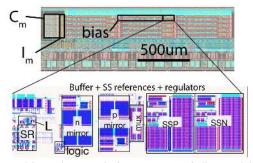


Fig. 5 15-bias micrograph from corner of die overlaid with layout and with close up of BB and SS layout.

one of the generated biases and drains brought to pads (Fig. 3). The sources are tied to the on-chip  $V_{sp}$  and  $V_{sn}$ . One  $V_{sp}$  was also brought out. These test transistors were sized with relative strength of 500 and 625 for n and p type transistors, respectively. These large W/L's allows indirect measurement of very small on-chip bias currents. Current measurements have been corrected by the estimated multiplier ratio.

The master current I<sub>m</sub> was set to 1.3uA by external resistor  $R_x=100k\Omega$ . Im was directly measured through  $R_x$ . The largest generated current is predicted to be  $I_{\rm m}/2$  and the smallest generated current is predicted to be a factor of  $2^{22}$ =4M times smaller than I<sub>m</sub>, or about 310fA. The measured currents are approximately linear with bias code value (Fig. 6a) except for large values of current where they increase more slowly than predicted. This is expected from the differing super-threshold behavior of the wide/short test FETs and the 8um/8um BB FETs and the intervening current multiplexor. The measured off currents  $I_{0n}$  and  $I_{0p}$ , corrected by the same scale factors as the measured currents, are about 3pA. Using SS biasing, the smallest measurable generated currents go down to about 300fA, a factor of 10 smaller, and consistent with the 22-bit resolution of the splitter. Additional testing using a larger  $R_x=390k\Omega$  (resulting in a smaller I<sub>m</sub>=0.22uA) shows a minimum measurable current using SS biasing of about 100fA. By setting an opposite-type bias (e.g. enabling p-type bias for an nfet) or by tying the bias to a rail, higher currents can be obtained; the maximum possible current at Vdd=1.8V is about 15uA from a square nFET in this process, giving a total dynamic range of roughly 160dB. Fig. 6b shows matching across 7 chips, reflecting inter-die threshold voltage mismatch. This constant relative variability (in the lower current

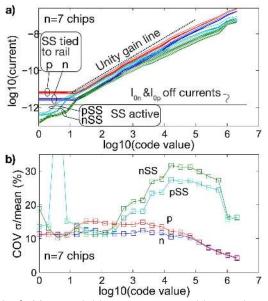


Fig. 6 a) Measured bias currents vs. bias code value. b) Measured coefficient of variation ( $\sigma(I)/I$ ) across 7 chips.

region) at any node of the current splitter is a consequence of the fact that series and parallel resistors combine to have the same total variability as any single element [8]. The lowest variability is obtained from an n-type non-SS bias at low current. The higher variability at higher currents, using p-type, or using the shifted sources, probably arises partly from the BB circuits and the readout pathway.

Results from the SS  $V_{sp}$  regulator are in Fig. 7 and Fig. 8. The effective DC resistance of the regulator is about 100 $\Omega$ , which is sufficiently small since typically the  $M_L$  currents that supply I<sub>s</sub> (Fig. 2) are constant and only a stable  $V_{sn}$  and/or  $V_{sp}$  are required. The time constant of recovery of  $V_{sn}$  and  $V_{sp}$  from a perturbation depends on the load capacitance; with a 10uF bypass capacitance nominal on-chip bias current values of 1nA, the smallsignal recovery time constant is on the order of 2ms. The large-signal perturbation in Fig. 8 exposes the rapid recovery from negative perturbations and the slewing recovery from positive perturbations.

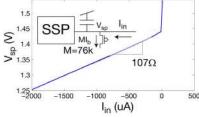


Fig. 7 Measured SS regulator DC regulation.  $V_{\rm sp}$  vs.  $I_{\rm s}$  is shown relative to Vdd, for midrange setting of  $I_{\rm bb}.$ 

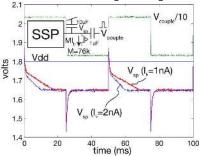


Fig. 8 Measured SS regulator AC regulation.  $V_{\rm sp}$  is shown when a square wave  $V_{\rm couple}$  is capacitively coupled into it.

#### 6. DISCUSSION

Fig. 9 summarizes specifications. The tested implementation is fully functional. The next generation will enhance on it as follows: To speed up bias modification over the external serial link from the ~150us of the current version, the biases will be individually addressable. Instead of generating a pair of SS voltages for each bias, a single programmable pair will be shared over all biases. We may use a coarse-fine strategy or compound mirrors to increase the dynamic range still further.

To promote the use of on-chip biasing and speed up fully-integrated chip development, a design kit for this

bias generator including schematics and layout has been open-sourced in the jAER project [3] which also includes PCB layout, firmware and host software. The design kit is free and has relaxed (LGPL-like) licensing terms. We hope these efforts will help bring silicon to more convincing realization.

Technology	180nm 4M 2P CIS
Supply voltage	1.8V
Master current area incl. Cm	220um x 260um
Per bias area	620um x 50um=0.0033
	mm <sup>2</sup>
Bias dynamic range, not incl.	22 bit fraction of Im=110dB
power rail saturation	
Bias buffer range	6 bit fraction of Im
Configuration bits	4 per bias
Weak disable Idsat	p-type: 2uA; n-type: 12uA
Current consumption per bias	~4Im
SS regulator resistance	110 ohms
Total range incl. Vdd or Gnd	160dB
bias	
Min current with Im=1.3uA	360fA
1- $\sigma$ p-type low-current-mode	12%, n=7 dies.
variation of measured bias currents	
	•

Fig. 9 Specifications

#### 7. ACKNOWLEDGEMENTS

Supported by ETH internal funding TH-18 07-1, Swiss National Science Foundation grant 200021-112354/1, the Univ of Zürich, and ETH Zürich.

#### 8. REFERENCES

- T. Delbruck and A. van Schaik, "Bias current generators with wide dynamic range," *Analog Integrated Circuits and Signal Processing*, vol. 43, pp. 247-268, Jun 2005.
- [2] T. Delbruck and P. Lichtsteiner, "Fully programmable bias current generator with 24 bit resolution per bias," in 2006 IEEE International Symposium on Circuits and Systems (ISCAS 2006), Athens, 2006, pp. 2849-2852.
- [3] T. Delbruck. (2007, *jAER open source project*. Available: http://jaer.wiki.sourceforge.net
- [4] P. Lichtsteiner, et al., "A 128×128 120dB 15us Latency Asynchronous Temporal Contrast Vision Sensor," *IEEE J. Solid State Circuits*, vol. 43, pp. 566-576, 2008.
- [5] B. Linares-Barranco, et al., "Current mode techniques for sub-pico-ampere circuit design," Analog Integrated Circuits and Signal Processing, vol. 38, pp. 103-119, 2004.
- [6] B. Linares-Barranco and T. Serrano-Gotarredona, "On the design and characterization of femtoampere current mode circuits," *IEEE Journal of Solid-State Circuits*, vol. 38, pp. 1353-1363, 2003.
- [7] G. Rincon-Mora, "Current efficient, low voltage, low dropout regulators," PhD, Georgia Institute of Technology, 1996.
- [8] G. Scandurra and C. Ciofi, "RBR ladder networks for the design of high-accuracy static analog memories," *Circuits* and Systems I: Fundamental Theory and Applications, IEEE Transactions on, vol. 50, pp. 605-612, 2003.