

## An Introduction to Radio Frequency Engineering

This book provides a comprehensive introduction to radio frequency (RF) engineering, using a straightforward and easily understood approach combined with numerous worked examples, illustrations and homework problems. The author has focused on minimising the mathematics needed to grasp the subject while providing a solid theoretical foundation for the student. Emphasis is also placed on the practical aspects of radio engineering. The book provides a broad coverage of RF systems, circuit design, antennas, propagation and digital techniques. Written for upper-level undergraduate courses, it will also provide an excellent introduction to the subject for graduate students, researchers and practising engineers.

**CHRISTOPHER COLEMAN** is an associate professor of electrical and electronic engineering at the University of Adelaide. He has held research posts at Imperial College London and the University College of Wales, and faculty positions at the University of Nottingham, UK, and the University of Wollongong, Australia. From 1990 until 1999 he served as a principal research scientist on Australia's Jindalee over the horizon radar project. He is a member of the IEEE and an associate editor of the *IEEE Antennas and Wireless Propagation Letters*.

Cambridge University Press  
978-0-521-83481-0 - An Introduction to Radio Frequency Engineering  
Christopher Coleman  
Frontmatter  
[More information](#)

---

Cambridge University Press  
978-0-521-83481-0 - An Introduction to Radio Frequency Engineering  
Christopher Coleman  
Frontmatter  
[More information](#)

---

# An Introduction to Radio Frequency Engineering

---

**Christopher Coleman**

Department of Electrical and Electronic Engineering,  
Adelaide University



**CAMBRIDGE**  
UNIVERSITY PRESS

Cambridge University Press  
 978-0-521-83481-0 - An Introduction to Radio Frequency Engineering  
 Christopher Coleman  
 Frontmatter  
[More information](#)

CAMBRIDGE UNIVERSITY PRESS  
 Cambridge, New York, Melbourne, Madrid, Cape Town,  
 Singapore, São Paulo, Delhi, Mexico City

Cambridge University Press  
 The Edinburgh Building, Cambridge CB2 8RU, UK

Published in the United States of America by Cambridge University Press, New York

[www.cambridge.org](http://www.cambridge.org)  
 Information on this title: [www.cambridge.org/9780521834810](http://www.cambridge.org/9780521834810)

© Christopher Coleman 2004

This publication is in copyright. Subject to statutory exception  
 and to the provisions of relevant collective licensing agreements,  
 no reproduction of any part may take place without the written  
 permission of Cambridge University Press.

First published 2004  
 Reprinted 2005  
 First paperback edition 2011

*A catalogue record for this publication is available from the British Library*

*Library of Congress Cataloguing in Publication Data*

Coleman, Christopher, 1950–  
 An introduction to radio frequency engineering / Christopher Coleman.  
 p. cm.

Includes bibliographical references and index.

ISBN 0-521-83481-3

1. Radio circuits – Design and construction. 2. Radio – Equipment and supplies – Design and construction.  
 3. Radio frequency. I. Title.

TK6560.C64 2004

621.384 – dc22 2003055893

ISBN 978-0-521-83481-0 Hardback

Cambridge University Press has no responsibility for the persistence or  
 accuracy of URLs for external or third-party internet websites referred to in  
 this publication, and does not guarantee that any content on such websites is,  
 or will remain, accurate or appropriate. Information regarding prices, travel  
 timetables, and other factual information given in this work is correct at  
 the time of first printing but Cambridge University Press does not guarantee  
 the accuracy of such information thereafter.

Cambridge University Press  
978-0-521-83481-0 - An Introduction to Radio Frequency Engineering  
Christopher Coleman  
Frontmatter  
[More information](#)

---

This book is dedicated to the memory of Les France and Peter Hattam.

Cambridge University Press  
978-0-521-83481-0 - An Introduction to Radio Frequency Engineering  
Christopher Coleman  
Frontmatter  
[More information](#)

---

# Contents

<i>List of figures</i>	<i>page xi</i>
<i>Preface</i>	<i>xxi</i>
<i>Acknowledgements</i>	<i>xxii</i>
<hr/>	
<b>1 Basic concepts</b>	<b>1</b>
<hr/>	
1.1 Radio waves	1
1.2 Noise	9
1.3 Sensitivity and selectivity	13
1.4 Non-linearity in RF systems	14
1.5 Digital modulation	19
1.6 Spread spectrum systems	20
1.7 Cellular radio	23
1.8 Radar systems	24
<hr/>	
<b>2 Frequency selective circuits and matching</b>	<b>28</b>
<hr/>	
2.1 Series resonant circuits	28
2.2 Parallel resonant circuits	33
2.3 Inductive transformers	34
2.4 Tuned transformers	36
2.5 Capacitive transformers	37
2.6 L-network matching	38
2.7 $\pi$ - and T-networks	39
2.8 Matching examples	41
2.9 Component reality	44
<hr/>	
<b>3 Active devices and amplifiers</b>	<b>49</b>
<hr/>	
3.1 The semiconductor diode	49
3.2 Bipolar junction transistors	50

<b>viii</b>	<b>Contents</b>	
	3.3 The Miller effect and BJT amplifiers	57
	3.4 Differential amplifiers	64
	3.5 Feedback	67
	3.6 Field-effect transistors	71
	3.7 FET amplifiers	76
	3.8 Amplifier noise	82
<b>4</b>	<b>Mixers, modulators and demodulators</b>	<b>86</b>
	4.1 Diode mixers	86
	4.2 Transistor mixers	89
	4.3 Transconductance mixers	93
	4.4 Amplitude modulation	95
	4.5 Angle modulation	101
	4.6 Gain and amplitude control	103
	4.7 A simple receiver design	105
<b>5</b>	<b>Oscillators and phase locked loops</b>	<b>108</b>
	5.1 Feedback	108
	5.2 The Colpitts oscillator	109
	5.3 Stability and phase noise in oscillators	117
	5.4 Voltage controlled oscillators	120
	5.5 Negative resistance approach to oscillators	121
	5.6 Phase locked loops	123
	5.7 Analysis of a phase locked loop	123
	5.8 Phase locked loop components	125
	5.9 Phase locked loop applications	127
<b>6</b>	<b>Transmission lines and scattering matrices</b>	<b>132</b>
	6.1 The transmission line model	132
	6.2 Time-harmonic variations	135
	6.3 Real transmission lines	139
	6.4 Impedance transformation	142
	6.5 Reflection coefficients	145
	6.6 $S$ parameters	148
	6.7 $S$ parameter amplifier design	154
	6.8 The measurement of $S$ parameters	161



<b>ix</b>	<b>Contents</b>	
	6.9 Some useful multiport networks	162
	6.10 Reflection coefficient approach to microwave oscillators	166
<b>7</b>	<b>Power amplifiers</b>	<b>171</b>
	7.1 Class A	171
	7.2 Class B	173
	7.3 Class C	176
	7.4 Class E	178
	7.5 A design example	179
	7.6 Transmission line transformers	181
<b>8</b>	<b>Filters</b>	<b>187</b>
	8.1 Filter characteristics	187
	8.2 Low- and high-pass filters	191
	8.3 Band-pass filters	194
	8.4 Conversion of filters to microstrip form	196
<b>9</b>	<b>Electromagnetic waves</b>	<b>204</b>
	9.1 Maxwell's equations	204
	9.2 Power flow	206
	9.3 Electromagnetic waves	206
	9.4 Oblique incidence	215
	9.5 Guided wave propagation	218
	9.6 Wave sources	224
<b>10</b>	<b>Antennas</b>	<b>228</b>
	10.1 Dipole antennas	228
	10.2 Effective length and gain	235
	10.3 The monopole antenna	238
	10.4 Feeding an antenna	243
	10.5 Array antennas	247
	10.6 Travelling wave antennas	258
	10.7 Aperture antennas	260
	10.8 Patch antennas	261

<b>x</b>	<b>Contents</b>	
<b>11</b>	<b>Propagation</b>	<b>266</b>
11.1	Reciprocity theorem	266
11.2	Some consequences of reciprocity	269
11.3	Line-of-sight propagation and reflections	271
11.4	Diffraction	275
11.5	Refraction	277
11.6	Ground wave propagation	286
11.7	Propagation by scattering	287
<b>12</b>	<b>Digital techniques in radio</b>	<b>293</b>
12.1	The processing of digitised signals	293
12.2	Analogue-to-digital conversion	298
12.3	Digital receivers	301
12.4	Direct digital synthesis	305
	<i>Index</i>	307

# Figures

1.1	Radiation of a radial pulse.	<i>page</i> 2
1.2	Electromagnetic field generated by a system of accelerating charge.	3
1.3	Development of oscillating dipole field.	4
1.4	A dipole antenna and its gain pattern.	5
1.5	Circuit model of a transmit system.	6
1.6	Conventions for effective length.	6
1.7	A dipole antenna used to collect energy from an electromagnetic wave.	7
1.8	Circuit model of receive system.	7
1.9	Reciprocity principle.	8
1.10	Transmit/receive system.	8
1.11	Noise sources.	9
1.12	Typical antenna noise temperatures for a dipole and a variety of sources.	10
1.13	Cascaded amplifiers.	12
1.14	Measurement of noise figure using matched sources at different temperatures.	13
1.15	Simple receiver architecture.	14
1.16	Superheterodyne receiver.	14
1.17	Set-up for measuring third-order intercept point.	17
1.18	Graph depicting the third-order intercept point and 1 dB compression point.	18
1.19	A direct conversion receiver together with the performance of its individual stages.	18
1.20	Formation of a spread baseband signal.	21
1.21	A simple DSSS transmitter.	22
1.22	A simple DSSS receiver.	22
1.23	A cellular radio system.	23
1.24	A general radar configuration.	25
1.25	Moving target.	26
2.1	Series resonant circuit.	29
2.2	Transient response.	30

**xii**      **List of figures**

---

2.3	Behaviour of transfer function around resonance.	31
2.4	Series resonant circuit with non-ideal source.	32
2.5	Notch filter example.	32
2.6	Parallel resonant circuit.	33
2.7	Transformer conventions.	34
2.8	Ideal transformer.	35
2.9	Non-ideal transformer.	35
2.10	Tuned transformer.	36
2.11	Model of tuned transformer.	36
2.12	Capacitive transformer.	37
2.13	Resonant capacitive transformer.	37
2.14	L matching network.	38
2.15	$\pi$ -network.	40
2.16	Analysis of $\pi$ -network.	40
2.17	T-network.	40
2.18	Analysis of a T-network.	41
2.19	L-network example.	42
2.20	$\pi$ -network example.	42
2.21	Analysis of $\pi$ -network example.	43
2.22	Final $\pi$ -network.	43
2.23	Single layer solenoid and spiral inductor.	44
2.24	Toroidal inductor and realistic inductor model.	45
2.25	Toroidal transformer and circuit model.	46
2.26	Parallel plate and parallel wire capacitors.	47
2.27	High frequency circuit models of realistic resistors and capacitors.	47
3.1	Junction diode.	50
3.2	High frequency model of a diode.	50
3.3	Bipolar junction transistor (BJT).	51
3.4	Typical BJT characteristics.	51
3.5	BJT load line.	52
3.6	Typical bias circuit.	53
3.7	Alternative bias circuits for a BJT common-emitter amplifier.	54
3.8	A common-emitter amplifier.	54
3.9	Simple BJT models.	55
3.10	Small signal model of common-emitter amplifier.	55
3.11	High frequency BJT model.	56
3.12	Alternative bias circuits for a BJT common-emitter amplifier.	56
3.13	Feedback amplifier and Miller equivalent.	57
3.14	Common-emitter amplifier model.	58
3.15	Miller transformed model.	58
3.16	A more complete BJT model.	59

xiii	List of figures	
3.17	A common-base amplifier.	61
3.18	Common-base amplifier model.	61
3.19	The cascode amplifier.	62
3.20	The emitter follower amplifier.	63
3.21	Emitter follower amplifier model.	63
3.22	A BJT differential amplifier.	65
3.23	Differential amplifier with current source.	66
3.24	A current mirror ( $I_0 = (V_{CC} - V_{BE})/R$ and $V_{BE} \approx 0.7\text{ V}$ ).	66
3.25	Active loads.	67
3.26	Differential amplifier with active loads.	67
3.27	A high frequency amplifier.	68
3.28	A feedback system.	68
3.29	BJT amplifier with feedback.	69
3.30	The calculation of resistances for bandwidth calculations.	70
3.31	The n-channel junction field-effect transistor (JFET).	71
3.32	The n-channel enhancement MOSFET (nMOS).	72
3.33	The p-channel enhancement MOSFET (pMOS).	72
3.34	Typical FET characteristics.	73
3.35	Typical $I_D - V_{GS}$ curves for (a) a JFET, (b) an nMOS enhancement FET and (c) a pMOS enhancement FET.	73
3.36	Bias configuration and bias spread characteristics.	74
3.37	FET load line.	74
3.38	Alternative biasing for a JFET.	75
3.39	Low frequency FET model.	75
3.40	Common-source amplifier.	76
3.41	Model of an FET device at RF frequencies.	77
3.42	Common-gate amplifier.	79
3.43	FET cascode amplifier.	79
3.44	Dual-gate MOSFET amplifier.	80
3.45	Source follower amplifier.	81
3.46	A CMOS differential amplifier.	81
3.47	FET active loads.	82
3.48	Amplifier with noise model.	82
3.49	Circuit of d.c.-coupled amplifier for Question 4.	84
3.50	An FET model that is appropriate at very high frequencies.	84
4.1	Diode mixer.	87
4.2	Balanced mixer based on a diode pair.	88
4.3	Diode ring mixer.	88
4.4	A typical single FET mixer.	89
4.5	Dual-gate MOSFET mixer.	91
4.6	BJT mixer.	91

**xiv**      **List of figures**

---

4.7	Alternative BJT mixer.	92
4.8	A basic transconductance mixer.	93
4.9	Gilbert cell mixer.	94
4.10	Simple AM transmitter.	95
4.11	Simple AM detector.	96
4.12	Synchronous detector.	96
4.13	Sideband structure.	97
4.14	Simple SSB transmitter.	97
4.15	Variable frequency SSB transmitter.	98
4.16	Phasing SSB generation.	98
4.17	Analysis of the phasing technique.	99
4.18	Phasing SSB demodulation.	100
4.19	An RC network 90° phase shifter.	100
4.20	Traditional SSB receiver.	100
4.21	Phase modulator.	102
4.22	Simple FM demodulation.	102
4.23	Detector frequency response.	103
4.24	Automatic gain control.	104
4.25	Filter and amplifier for AGC.	104
4.26	Limiting amplifier.	105
4.27	A simple direct conversion receiver.	105
4.28	Modern form of DC receiver.	106
5.1	General feedback system.	109
5.2	Colpitts oscillator.	110
5.3	Simple model of Colpitts oscillator.	110
5.4	FET Colpitts with bias circuits.	111
5.5	General Colpitts oscillator.	111
5.6	Clapp and Hartley feedback circuits.	112
5.7	FET differential oscillator.	112
5.8	The drain current for a Colpitts oscillator.	114
5.9	Alternative Colpitts oscillator.	114
5.10	Source follower amplifier.	115
5.11	Simplified Colpitts oscillator model.	115
5.12	An FET Colpitts oscillator that allows output to be taken from the drain.	116
5.13	Oscillator with series LCR feedback.	117
5.14	Phase noise.	118
5.15	Illustration of reciprocal mixing.	119
5.16	Crystal resonator model.	120
5.17	Crystal Colpitts oscillator.	120
5.18	A Colpitts VCO.	121

xv	List of figures	
5.19	Gunn diode.	121
5.20	Oscillator based on the Gunn diode.	122
5.21	Negative resistance circuit based on an FET.	122
5.22	General phase locked loop.	123
5.23	Response of a phase locked loop to a step change in reference phase.	125
5.24	Phase comparator.	126
5.25	Loop filter.	126
5.26	Phase/frequency detector based on $D$ flip-flops and a charge pump.	127
5.27	Signal levels in the phase/frequency detector.	128
5.28	A simple FET PLL.	129
5.29	Phase locked loop FM demodulator.	129
5.30	Phase locked loop AM detector.	129
5.31	Frequency synthesiser.	129
5.32	Frequency dividers based on $D$ flip-flops.	130
6.1	Coaxial and twin parallel wire transmission lines.	133
6.2	Lumped component model of transmission line.	133
6.3	Propagation on a transmission line with resistive load.	135
6.4	Terminated transmission line.	136
6.5	The input impedance of a loaded line ( $Z_{in} = R_{in} + X_{in}$ ).	138
6.6	Microstrip transmission line.	140
6.7	Realistic model of transmission line.	141
6.8	The short-circuited line.	142
6.9	The open-circuited line.	143
6.10	The $\lambda/4$ transformer.	143
6.11	Stub matching.	144
6.12	Replacing the stub by a lumped component.	144
6.13	Matching example.	145
6.14	Reflection coefficient description of a one-port network.	146
6.15	A complex tuned circuit and associated Smith chart.	147
6.16	Smith charts.	147
6.17	Source and load connected by a transmission line.	147
6.18	$S$ matrix description of two-port network.	149
6.19	$Z$ matrix description of two-port network.	149
6.20	Symmetric T-network example.	150
6.21	Configuration for the derivation of $S$ parameters.	151
6.22	A simple two-port model of an FET.	152
6.23	General amplifier with source and load.	154
6.24	Transistor amplifier.	154
6.25	Smith chart representation of amplifier stability.	157
6.26	Final amplifier design.	160
6.27	A simple directional coupler.	161

**xvi**      **List of figures**

6.28	Set-up for the measurement of $S$ parameters.	162
6.29	Microstrip form of Wilkinson power divider.	162
6.30	Microstrip form of directional coupler.	163
6.31	Analysis of microstrip coupler in terms of even and odd modes.	164
6.32	A branch line quadrature hybrid.	165
6.33	A microwave mixer that is based on a $90^\circ$ hybrid and diode pair.	165
6.34	Microstrip circulator with application.	166
6.35	Amplifier configuration.	167
6.36	An FET negative resistance oscillator.	167
6.37	Model of FET negative resistance generator.	168
6.38	Microstrip implementation of a negative resistance oscillator.	168
6.39	Circuit for Smith chart example in Question 5.	169
6.40	Circuits for two-port $S$ matrix calculations in Question 6.	169
7.1	Basic power amplifier circuit.	172
7.2	Class A operation.	172
7.3	Class B operation.	174
7.4	Push-pull class B amplifier.	175
7.5	A bias circuit for class B operation.	176
7.6	Class C amplifier.	177
7.7	Class E amplifier.	179
7.8	Power amplifier example.	180
7.9	Design of an output matching network.	180
7.10	Input matching network.	181
7.11	Transmission line transformer model.	182
7.12	Twisted pair transmission line.	183
7.13	Practical transformer.	183
7.14	4:1 transformer.	184
7.15	9:1 transformer.	184
7.16	Power combiner.	184
7.17	A 1:1 BALUN.	185
8.1	Ideal filters.	188
8.2	A simple low-pass filter.	188
8.3	A simple high-pass filter.	188
8.4	Two-pole filter example.	189
8.5	Transducer gain for two-pole filter.	189
8.6	Typical low-pass filter characteristics.	190
8.7	Comparison of Butterworth and Chebyshev filters.	191
8.8	Low-pass Butterworth filter characteristics.	191
8.9	Low-pass filters for $K = 1$ and $K = 2$ .	192
8.10	Low-pass filters for $K = 3$ and $K = 5$ .	192
8.11	Alternative low-pass Butterworth configurations.	193



**xvii**      **List of figures**

---

8.12	High-pass filters for $K = 1$ and $K = 2$ .	194
8.13	High-pass filters for $K = 3$ and $K = 5$ .	194
8.14	High-pass filter characteristics.	195
8.15	Band-pass filter derived from a low-pass filter.	195
8.16	Transformation of filter characteristics.	195
8.17	Circuit with three-element filter.	197
8.18	Correspondence between lumped components and transmission lines.	197
8.19	Basic three-element filter.	197
8.20	Some of Kuroda's identities.	198
8.21	Filter with transmission line extensions.	199
8.22	Filter after application of Kuroda identities.	199
8.23	Transmission line realisation.	199
8.24	Prototype lumped component filter.	199
8.25	Prototype transmission line filter.	200
8.26	Final transmission line filter.	200
8.27	Microstrip realisation of the filter.	201
8.28	Simple parallel microstrip filter.	201
8.29	Parallel microstrip filter.	202
9.1	A plane electromagnetic pulse.	208
9.2	The decomposition of linear polarisation into circularly polarised modes.	210
9.3	Dispersion of pulses.	211
9.4	Group speed for a simple two-component signal.	212
9.5	Reflection and transmission at a plane interface.	212
9.6	Transmission through a screen.	213
9.7	Attenuation in a current carrying conductor.	215
9.8	The skin effect on a wire conductor.	215
9.9	Oblique incidence of plane waves.	216
9.10	Coaxial waveguide.	218
9.11	Microstrip geometry and fields.	219
9.12	Hollow rectangular waveguide.	219
9.13	Rectangular cavities with loop and probe coupling.	222
9.14	Dominant modes in rectangular and circular hollow waveguides.	222
9.15	High $Q$ bandstop microstrip formed with dielectric resonator.	223
9.16	High stability oscillator that uses a dielectric resonator.	223
9.17	Field zones in relation to the radiating sources.	225
10.1	A snapshot of the electric field near a dipole.	229
10.2	Circuit model of antenna with transmission line.	229
10.3	The distribution of current on dipole antennas.	230
10.4	Half-wave dipole represented as a series of ideal dipoles.	230
10.5	Dipole and coordinate system.	231

**xviii**      **List of figures**

---

10.6	The folded dipole.	233
10.7	Magnetic dipole antenna and practical realisation.	234
10.8	Biconical and bow tie dipoles.	235
10.9	Gain surface of a short dipole.	237
10.10	Gain of a short dipole in a cross-section through the dipole axis.	238
10.11	Gain pattern of a half wavelength dipole.	239
10.12	Gain pattern of a 5/4 wavelength dipole.	239
10.13	Image current concept.	240
10.14	Connection between monopole and dipole antennas.	240
10.15	Shortening a monopole antenna.	241
10.16	Broadband conical and discone antennas.	241
10.17	Ground reflections from a dipole antenna element.	242
10.18	The effect of a finitely conducting plane.	242
10.19	Antennas located over a lossy plane.	243
10.20	Matching a short monopole to a standard load.	244
10.21	A balanced antenna when fed by (a) balanced and (b) unbalanced transmission lines.	245
10.22	Dipoles with coaxial feeds.	246
10.23	A half-wave dipole with offset feed.	246
10.24	A pair of phased dipoles.	247
10.25	Gain pattern of two dipoles in broadside configuration.	248
10.26	Gain pattern of two dipoles in endfire configuration.	249
10.27	Gain pattern of dipoles with 90° phasing and $\lambda/4$ spacing ( $f = 150$ MHz).	250
10.28	The mutual impedance of half-wave dipoles in parallel and collinear configurations.	250
10.29	Gain pattern of five dipoles in broadside configuration.	251
10.30	A five-element array of dipoles.	251
10.31	Vertical pattern of broadside configuration.	252
10.32	Gain pattern of five dipoles in endfire configuration.	253
10.33	Gain pattern of five endfire dipoles with reduced spacing and phase increment.	253
10.34	Array factors for linear arrays with equally spaced elements.	255
10.35	Log periodic dipole antenna.	255
10.36	Typical gain pattern of an LPDA in a plane perpendicular to the antenna.	256
10.37	Typical gain pattern in the plane of the LPDA.	256
10.38	A general Yagi–Uda parasitic array antenna.	257
10.39	Beverage travelling wave antenna.	258
10.40	Helical antenna construction and gain.	259
10.41	Waveguide antenna and analysis.	260

<b>xix</b>	<b>List of figures</b>	
	10.42 A horn antenna and a reflector antenna.	262
	10.43 Electric field between plates at resonance.	262
	10.44 A practical patch antenna with microstrip feed.	263
	11.1 The excitation of a waveguide.	268
	11.2 Interaction of two antennas.	270
	11.3 Communication system with two stations.	271
	11.4 Propagation with ground reflections.	272
	11.5 Propagation through an urban environment.	273
	11.6 Propagation over a stretch of water.	274
	11.7 Diffractive propagation over a building.	275
	11.8 Huygen’s principle and diffraction over a screen.	276
	11.9 Propagation obscured by a screen.	276
	11.10 The refraction of a plane wave at a plane interface.	278
	11.11 The direction of propagation with refraction by a continuously varying medium.	278
	11.12 Propagation through a spatially varying medium.	280
	11.13 A ray path in a spatially varying medium.	280
	11.14 Ducting propagation in the atmosphere.	281
	11.15 The ionospheric F layer.	282
	11.16 Ray paths in the ionosphere.	283
	11.17 Ground wave propagation over a hill.	286
	11.18 The scattering caused by a flat plate.	288
	11.19 Total power scattered by a plate (normalised on the maximum power).	289
	11.20 Propagation by scatter from a permittivity anomaly.	290
	11.21 Scintillation caused by permittivity irregularity.	291
	12.1 The frequency content of a real signal.	294
	12.2 The sampling of an analogue signal.	294
	12.3 Three signals with identical DFT due to aliasing.	296
	12.4 Spectral contamination caused by aliasing.	296
	12.5 A finite length discrete signal filtering system.	298
	12.6 A simple one-bit analogue-to-digital converter.	299
	12.7 A two-bit analogue-to-digital flash converter.	299
	12.8 Digitisation of a general signal.	300
	12.9 Sampled signals with quantisation noise.	301
	12.10 Simple digital-to-analogue converter.	302
	12.11 A direct conversion receiver with baseband analogue-to-digital conversion.	302
	12.12 A direct digitising receiver.	303
	12.13 A digital oscillator.	304
	12.14 A direct digital synthesiser.	305

Cambridge University Press  
978-0-521-83481-0 - An Introduction to Radio Frequency Engineering  
Christopher Coleman  
Frontmatter  
[More information](#)

---

# Preface

The following text evolved out of a series of courses on radio frequency (RF) engineering to undergraduates, postgraduates, government and industry. It was designed to meet the needs of such groups and, in particular, the needs of working engineers attempting to upgrade their skills. Thirty years ago, it appeared as if the fibre optics revolution would relegate wireless to a niche discipline, and universities accordingly downgraded their offerings in RF. In the past 10 years, however, there has been a renaissance in wireless and to a point where it is now a key technology. This has been made possible by the developments in very large-scale integration (VLSI) and CMOS technology in particular. In order to meet the manpower requirements of the wireless industry, there has been a need to upgrade the status of RF training in universities and to provide courses suitable for in-service training. The applications of wireless systems have changed greatly over the past 30 years, as has the available technology. In particular, there is a greater use of digital technologies, and antenna systems can often be of the array variety. The current text has been written with these changes in mind and there has been a culling of some traditional material that is of limited utility in the current age (graphical design methods for example). Material in the book has been carefully chosen to provide a basic training in RF and a springboard for more advanced study. At the author's own institution, RF engineering is now taught in a unified manner that emphasises the relationship between the individual components and the total system. This is part of an international trend that is gathering pace and is necessitated by the total integration of modern RF systems. The student is now expected to be able to appreciate the operation of a total system including electronics, antennas and propagation. Unfortunately, many of the textbooks covering these individual areas are extremely advanced and inappropriate at the intermediate level to which this text is mainly directed. In particular, propagation is ignored almost totally at this level. The current text is designed to service the needs of a broad RF training and to equip the reader with sufficient knowledge to appreciate the more advanced texts of other authors. As a minimum, this book requires the reader to have a basic foundation in electronics and electro-magnetism. At the author's institution the material in the first five chapters forms the basis of an initial course in RF and this is followed by a more advanced course that is based on Chapters 6 to 11.

# Acknowledgements

The author would like to thank Greg Harmer, Brian Ng and Kiet To for their invaluable help with the LaTeX and diagrams for this book. He would also like to thank Said Al-Sarawi and Ken Sarkies for reading through some of the drafts. Finally, he would like to thank Alex Sharpe for his copy editing work and valuable comments.