

Circuit Simulation with SPICE OPUS

Theory and Practice

Tadej Tuma
Árpád Bűrmen

Birkhäuser
Boston • Basel • Berlin

Contents

Abbreviations	xiii
About SPICE OPUS and This Book	xv
1 Introduction to Circuit Simulation	1
1.1 Signals and Linear Systems	1
1.2 Lumped Circuits	3
1.3 DC Solutions and the Operating Point of a Circuit	10
1.4 Incremental DC Circuit Model	13
1.5 Circuit's Response in the Time Domain	18
1.6 Fourier Series and Fourier Transformation	20
1.7 Incremental Circuit Model in the Time Domain	22
1.8 Incremental Circuit Model in the Frequency Domain	25
1.9 Noise Signals in LTI Systems	27
1.10 Circuit Noise Modeling and Analysis	29
1.11 Laplace Transformation and the s -Domain	32
1.12 Circuit Analysis in the s -Domain, DC Solution Stability	33
2 Short Tutorial	37
2.1 Installation	37
2.2 Starting SPICE OPUS	38
2.3 The Command Window	40
2.4 Describing a Circuit	41
2.4.1 Input File Structure	41
2.4.2 Numbers in SPICE	42
2.4.3 A Simple Circuit	43
2.5 Operating Point (OP) Analysis	45
2.6 Operating Point Sweep (DC), Plotting of Simulation Results	48
2.7 Small Signal Analysis (AC and TF)	53
2.8 Pole-Zero Analysis (PZ)	61
2.9 Small Signal Noise Analysis (NOISE)	65
2.10 Time-Domain Analysis (TRAN)	71

2.11	Interactive Interpreter and Advanced Features	76
2.11.1	Expressions, Vectors, Plots, and Automated Measurements ...	76
2.11.2	Control Structures, Substitution, and Variables	79
2.11.3	Libraries, Raw Files, and File Output	82
2.11.4	Saving Device Quantities During Analyses	85
2.11.5	Tracing and Interactive Plotting	87
3	Input File Syntax	89
3.1	File Structure.....	89
3.2	Numbers.....	90
3.3	Instances and Nodes	90
3.4	Models	91
3.5	Instance and Model Parameters	92
3.6	Device Syntax.....	93
3.6.1	Resistor	94
3.6.2	Capacitor	95
3.6.3	Inductor	96
3.6.4	Inductive Coupling	97
3.6.5	Independent Voltage Source	98
3.6.6	Independent Current Source	104
3.6.7	Linear Voltage-Controlled Current Source.....	104
3.6.8	Linear Voltage-Controlled Voltage Source.....	105
3.6.9	Linear Current-Controlled Current Source.....	106
3.6.10	Linear Current-Controlled Voltage Source.....	107
3.6.11	Nonlinear Controlled Sources	108
3.6.12	Voltage-Controlled Switch	110
3.6.13	Current-Controlled Switch.....	112
3.6.14	Lossless Transmission Line.....	113
3.6.15	Lossy Transmission Line	114
3.6.16	Uniformly Distributed RC Line	115
3.6.17	Semiconductor Diode	117
3.6.18	Bipolar Junction Transistor (BJT).....	119
3.6.19	Junction Field Effect Transistor (JFET).....	123
3.6.20	Metal Semiconductor Field Effect Transistor (MESFET).....	126
3.6.21	Metal Oxide Semiconductor Field Effect Transistor (MOSFET).....	128
3.6.22	Legacy MOSFET Models (Levels 1–6).....	128
3.6.23	BSIM3 and BSIM4 MOSFET Models (Levels 47, 53, and 60).....	137
3.6.24	Silicon on Insulator (SOI) MOSFET Models (Levels 55–58).....	141
3.6.25	UFET and EKV MOSFET Models (Levels 7 and 44).....	147
3.7	Binning of MOS Models	148
3.8	Including Files in the Netlist	152
3.9	Describing Circuits Hierarchically.....	153

3.9.1	Defining a Subcircuit, Subcircuit Instantiation	153
3.9.2	Global Nodes	154
3.9.3	Nesting Subcircuits and Understanding the Flat Circuit	154
3.9.4	Parametrization of Subcircuits.....	156
3.10	Initial Operating Point Solution and Initial Conditions	157
3.11	Joining Multiple Topologies in a Netlist.....	158
3.12	Simulator Parameters	159
4	Analyzing the Circuit	163
4.1	Operating Point (OP) Analysis.....	163
4.1.1	Handling of Initial Solutions (Nodesets).....	164
4.1.2	Solving Convergence Problems	164
4.2	Operating Point Sweep Analysis (DC Analysis).....	167
4.3	DC Transfer Function Analysis (TF Analysis).....	169
4.4	Small Signal Analysis (AC Analysis)	170
4.5	Pole-Zero (PZ) Analysis	171
4.6	Noise (NOISE) Analysis	172
4.7	Transient (TRAN) Analysis	173
5	NUTMEG Scripting Language	177
5.1	Input Handling	177
5.1.1	Splitting the Input Line into Words, Escaped Characters	177
5.1.2	History and History Substitution	179
5.1.3	Aliases and Alias Substitution	180
5.1.4	Control Lines and Statements	181
5.1.5	Evaluation of Statements	181
5.2	Text Output	183
5.3	Plots, Vectors, and Expressions	183
5.3.1	Organization of Numeric Data.....	183
5.3.2	Plot Management.....	184
5.3.3	Storing and Restoring Plots in Files.....	185
5.3.4	Vectors	186
5.3.5	Expressions	189
5.3.6	Operators in NUTMEG Expressions	190
5.3.7	NUTMEG Built-in Functions	192
5.3.8	User-Defined Functions.....	197
5.3.9	Arithmetic Substitution	197
5.4	Variables	198
5.4.1	Variable Basics	198
5.4.2	NUTMEG Control Variables and Simulator Parameters	199
5.4.3	Variable Substitution and Text Input	200
5.5	Circuits	203
5.5.1	Circuit and Script Input (source Command).....	204
5.5.2	Circuit Management	205
5.5.3	Circuit Listing	206

5.5.4	Printing Parameter Values of SPICE Primitives	207
5.5.5	Selecting the Topology and Rebuilding the Circuit.....	208
5.5.6	Changing Nodesets and Initial Conditions	210
5.5.7	Changing Instance, Model, and Subcircuit Parameters.....	211
5.5.8	Parameter Value Propagation in Subcircuits	212
5.5.9	Changing and Accessing Simulator Parameters for the Current Circuit	214
5.5.10	Accessing Instance, Model, and Subcircuit Parameter Values	214
5.6	Simulation.....	215
5.6.1	Choosing What the Simulator Stores in Vectors (Saving).....	215
5.6.2	Tracing Simulation Results During Simulation.....	218
5.6.3	Plotting Simulation Results During Simulation (Iplotting) ...	219
5.6.4	Invoking Simulation.....	220
5.7	Analyzing the Results	224
5.7.1	Linearizing the Scale of a Plot.....	224
5.7.2	Performing Measurements on Vectors	225
5.7.3	Fourier Analysis of Vectors	228
5.7.4	Transforming Vectors to Frequency Domain	229
5.8	Plotting the Results	233
5.8.1	The Plot Window.....	233
5.8.2	Curve Display Styles.....	236
5.8.3	Plot Window Grids	237
5.8.4	Vector Interpretation Modes	240
5.8.5	The plot Command	243
5.8.6	Examples	247
5.9	Control Structures	250
5.9.1	if-elseif-else Block.....	250
5.9.2	while, dowhile, and repeat Loops	251
5.9.3	Breaking and Continuing a Loop.....	252
5.10	Miscellaneous.....	252
5.10.1	Directory and File Management.....	252
5.10.2	Obtaining Statistics from the Simulator.....	253
5.10.3	The spinit File.....	254
6	Mathematical Background	257
6.1	Linear Resistive Networks	257
6.1.1	Circuit Tableau	260
6.1.2	Basic Nodal Equations	262
6.1.3	Modified Nodal Equations	264
6.2	Solving the Set of Circuit Equations.....	266
6.2.1	Sparse Matrices	267
6.2.2	LU Decomposition	267
6.2.3	Successful Pivoting Techniques	269
6.2.4	Numerical Error Control	271

6.3	Introducing Nonlinear Devices	274
6.3.1	Fixed Point Iteration	274
6.3.2	Newton–Raphson Algorithm	276
6.3.3	Convergence Detection	283
6.3.4	Automatic Convergence Helpers	285
6.3.5	Specifying the Initial Point for the Newton–Raphson Algorithm	295
6.4	Dynamic Devices and Frequency-Domain Analysis	295
6.4.1	Small Signal Response (AC) Analysis	295
6.4.2	Poles and Zeros of the Small Signal Transfer Function (PZ)	298
6.4.3	Small Signal Noise Analysis (NOISE)	299
6.4.4	Frequency-Domain Model of an Inductor in SPICE OPUS	302
6.5	Transient (Time-Domain) Analysis (TRAN)	303
6.5.1	Backward Euler Integration	303
6.5.2	Trapezoidal Integration	308
6.5.3	General Linear Multistep Numerical Integration	311
6.5.4	Local Truncation Error (LTE)	314
6.5.5	Inductors in SPICE OPUS Time-Domain Analysis	317
6.5.6	Initial Conditions	318
6.5.7	Predictor-Corrector Integration	319
6.5.8	Choosing the Integration Algorithm	321
6.5.9	Integration Time-Step Control	322
7	Examples	329
7.1	Parametrized Attenuator and Transmission Lines	329
7.2	Modeling a Nonlinear Transformer	335
7.3	Analyzing a CMOS Differential Amplifier	341
7.4	Using Corner Models	350
7.5	Local Variations (Mismatch) and Monte-Carlo Analysis	357
7.6	Drawing Histograms, Yield Analysis	362
7.7	Logic Gates	364
7.8	Flip-Flops	367
7.9	Counters and Frequency Dividers	371
7.10	Phase Frequency Detector	373
7.11	Voltage-Controlled Oscillator	378
7.12	Phase-Locked Loop	381
	References	387
	Index	391