

High Efficiency RF and Microwave Solid State Power Amplifiers

Paolo Colantonio, Franco Giannini, and Ernesto Limiti

*Department of Electronic Engineering, University of Roma,
Tor Vergata, Italy*



A John Wiley and Sons, Ltd., Publication

Contents

Preface	xi
About the Authors	xiii
Acknowledgments	xv
1 Power Amplifier Fundamentals	1
1.1 Introduction	1
1.2 Definition of Power Amplifier Parameters	2
1.3 Distortion Parameters	7
1.3.1 Harmonic Distortion	9
1.3.2 AM-AM/AM-PM	10
1.3.3 Two-tone Intermodulation	10
1.3.4 Intercept Point IP _n	13
1.3.5 Carrier to Intermodulation Ratio	14
1.3.6 Spurious Free Dynamic Range	15
1.3.7 Adjacent Channel Power Ratio	15
1.3.8 Noise and Co-Channel Power Ratio (NPR and CCPR)	17
1.3.9 Multi-tone Intermodulation Ratio	19
1.3.10 Error Vector Magnitude	20
1.4 Power Match Condition	20
1.5 Class of Operation	23
1.6 Overview of Semiconductors for PAs	25
1.7 Devices for PA	28
1.7.1 Requirements for Power Devices	29
1.7.2 BJT	31
1.7.3 HBT	32
1.7.4 FET	32
1.7.5 MOSFET	33
1.7.6 LDMOS	34
1.7.7 MESFET	35
1.7.8 HEMT	37
1.7.9 General Remarks	40
1.8 Appendix: Demonstration of Useful Relationships	42
1.9 References	44

2	Power Amplifier Design	49
2.1	Introduction	49
2.2	Design Flow	49
2.3	Simplified Approaches	57
2.4	The Tuned Load Amplifier	63
2.5	Sample Design of a Tuned Load PA	71
2.6	References	82
3	Nonlinear Analysis for Power Amplifiers	85
3.1	Introduction	85
3.2	Linear vs. Nonlinear Circuits	87
3.3	Time Domain Integration	88
3.3.1	Iterative Algorithm (Newton–Raphson and Fixed-point)	91
3.4	Example	92
3.4.1	Forward Euler Solution	94
3.4.2	Backward Euler Solution	94
3.4.3	Steady-state Analysis and Shooting Method	98
3.4.4	Example	99
3.5	Solution by Series Expansion	101
3.6	The Volterra Series	101
3.6.1	Response to a Single-tone Excitation	103
3.6.2	Response to a Two-tone Excitation	104
3.6.3	The Probing Method	106
3.6.4	Example	107
3.6.5	Cascade of Systems	110
3.7	The Fourier Series	113
3.8	The Harmonic Balance	114
3.8.1	Example	120
3.8.2	Multi-tone HB Analysis	122
3.9	Envelope Analysis	123
3.10	Spectral Balance	125
3.11	Large Signal Stability Issue	126
3.12	References	127
4	Load Pull	131
4.1	Introduction	131
4.2	Passive Source/Load Pull Measurement Systems	132
4.3	Active Source/Load Pull Measurement Systems	137
4.3.1	Two-signal Path Technique	138
4.3.2	Active Loop Technique	138
4.4	Measurement Test-sets	143
4.4.1	Scalar Systems	143
4.4.2	VNA Based Systems	146
4.4.3	Six-port Reflectometer Based Systems	148
4.5	Advanced Load Pull Measurements	151
4.5.1	Intermodulation Measurements	151
4.5.2	Time-domain Waveform Load Pull	153
4.5.3	Pulsed Load Pull	156
4.6	Source/Load Pull Characterization	156

4.7	Determination of Optimum Load Condition	160
4.7.1	Example of Simplified Load Pull Contour	164
4.7.2	Design of an Amplifier Stage using Simplified Load Pull Contours	168
4.8	Appendix: Construction of Simplified Load Pull Contours through Linear Simulations	169
4.9	References	172
5	High Efficiency PA Design Theory	177
5.1	Introduction	177
5.2	Power Balance in a PA	178
5.3	Ideal Approaches	181
5.3.1	Tuned Load	182
5.3.2	Class F or Inverse Class F (Class F^{-1})	182
5.3.3	Class E or General Switched-mode	183
5.4	High Frequency Harmonic Tuning Approaches	184
5.4.1	Mathematical Statements	185
5.5	High Frequency Third Harmonic Tuned (Class F)	190
5.6	High Frequency Second Harmonic Tuned	196
5.7	High Frequency Second and Third Harmonic Tuned	202
5.8	Design by Harmonic Tuning	208
5.8.1	Truncated Sinusoidal Current Waveform	211
5.8.2	Quadratic Current Waveform	214
5.8.3	Rectangular Current Waveform	216
5.9	Final Remarks	219
5.10	References	221
6	Switched Amplifiers	223
6.1	Introduction	223
6.2	The Ideal Class E Amplifier	224
6.3	Class E Behavioural Analysis	225
6.4	Low Frequency Class E Amplifier Design	230
6.5	Class E Amplifier Design with 50% Duty-cycle	234
6.5.1	Practical Implementation and Variants of Class E Power Amplifiers	237
6.5.2	High Frequency Class E Amplifiers	240
6.6	Examples of High Frequency Class E Amplifiers	245
6.6.1	C-Band GaAs Class E Amplifier	246
6.6.2	X-Band GaAs Class E Amplifier	247
6.6.3	S-Band GaN Class E Amplifier	252
6.6.4	S-Band LDMOS Class E Amplifier	254
6.7	Class E vs. Harmonic Tuned	257
6.8	Class E Final Remarks	260
6.9	Appendix: Demonstration of Useful Relationships	261
6.10	References	263
7	High Frequency Class F Power Amplifiers	267
7.1	Introduction	267
7.2	Class F Description Based on Voltage Wave-shaping	268
7.3	High Frequency Class F Amplifiers	273
7.3.1	Effects of Device Output Resistance R_{ds}	277

7.4	Bias Level Selection	280
7.5	Class F Output Matching Network Design	286
7.6	Class F Design Examples	289
7.7	References	295
8	High Frequency Harmonic Tuned Power Amplifiers	297
8.1	Introduction	297
8.2	Theory of Harmonic Tuned PA Design	298
8.3	Input Device Nonlinear Phenomena: Theoretical Analysis	303
8.4	Input Device Nonlinear Phenomena: Experimental Results	309
8.5	Output Device Nonlinear Phenomena	316
8.6	Design of a Second HT Power Amplifier	321
8.7	Design of a Second and Third HT Power Amplifier	328
8.8	Example of 2 nd HT GaN PA	335
8.9	Final Remarks	336
8.10	References	339
9	High Linearity in Efficient Power Amplifiers	341
9.1	Introduction	341
9.2	Systems Classification	342
9.3	Linearity Issue	345
9.4	Bias Point Influence on IMD	347
9.5	Harmonic Loading Effects on IMD	352
9.5.1	High Linearity and High Efficiency PA Design Process	354
9.5.2	High Linearity and High Efficiency PA Design Example	358
9.6	Appendix: Volterra Analysis Example	362
9.7	References	365
10	Power Combining	369
10.1	Introduction	369
10.2	Device Scaling Properties	370
10.3	Power Budget	371
10.4	Power Combiner Classification	373
10.5	The T-junction Power Divider	377
10.5.1	Resistive Divider	379
10.6	Wilkinson Combiner	380
10.6.1	Two-way Equal Splitter Wilkinson Combiner/divider	383
10.6.2	Two-way Unequal Splitter Wilkinson Combiner/divider	385
10.6.3	Two-way Wilkinson with Arbitrary Impedances	386
10.6.4	Other Two-way Wilkinson Structures	387
10.6.5	Planarization of N-way Wilkinson Splitter/combiner	388
10.6.6	Design Considerations on Wilkinson Splitter/combiner	391
10.7	The Quadrature (90°) Hybrid	395
10.7.1	Branch-line	395
10.7.2	Coupled Line Directional Couplers	400
10.7.3	The Lange Coupler	404
10.8	The 180° Hybrid (Ring Coupler or Rat-race)	405
10.9	Bus-bar Combiner	407

10.10	Other Planar Combiners	409
10.10.1	Three-way Power Divider with Variable Output Power Ratios	409
10.10.2	The Bagley Polygon Combiner	411
10.10.3	Composite Coupler	411
10.11	Corporate Combiners	412
10.11.1	Tree Structures	412
10.11.2	Travelling Wave Combiners	417
10.11.3	Multiple-level Combiners	419
10.12	Resonating Planar Combiners	420
10.13	Graceful Degradation	420
10.14	Matching Properties of Combined PAs	424
10.15	Unbalance Issue in Hybrid Combiners	426
10.16	Appendix: Basic Properties of Three-port Networks	427
10.16.1	Three-port Networks	427
10.17	References	428
11	The Doherty Power Amplifier	435
11.1	Introduction	435
11.2	Doherty's Idea	436
11.2.1	Active Load Modulation	438
11.2.2	Impedance Inverting Network Implementation	439
11.3	The Classical Doherty Configuration	440
11.4	The 'AB-C' Doherty Amplifier Analysis	443
11.4.1	Fourier Representation for the Drain Current Waveforms	443
11.4.2	Behavioural Analysis	447
11.5	Power Splitter Sizing	461
11.6	Evaluation of the Gain in a Doherty Amplifier	463
11.7	Design Example	466
11.8	Advanced Solutions	480
11.8.1	Different Drain Bias Voltages	480
11.8.2	Doherty with Main Amplifier in Class F Configuration	483
11.8.3	Multi-way Doherty Amplifiers	487
11.8.4	Multi-stage Doherty Amplifiers	489
11.9	References	493
	Index	495