

0853 - 5049  
+ 100-20M

# SPICE FOR POWER ELECTRONICS AND ELECTRIC POWER

## SECOND EDITION

**MUHAMMAD H. RASHID**

*University of West Florida  
Pensacola, Florida, U.S.A.*

**HASAN M. RASHID**

*University of Florida  
Gainesville, Florida, U.S.A.*



**Taylor & Francis**

Taylor & Francis Group

Boca Raton London New York

---

A CRC title, part of the Taylor & Francis imprint, a member of the Taylor & Francis Group, the academic division of T&F Informa plc.

---

# Table of Contents

<b>Chapter 1</b>	<b>Introduction.....</b>	<b>1</b>
1.1	Introduction.....	1
1.2	Descriptions of SPICE .....	2
1.3	Types of Spice .....	2
1.4	Types of Analysis .....	3
1.5	Limitations of PSpice.....	5
1.6	Descriptions of Simulation Software Tools .....	5
1.7	PSpice Platform.....	6
1.7.1	PSpice A/D .....	6
1.7.2	PSpice Schematics.....	7
1.7.3	OrCAD Capture.....	7
1.8	PSpice Schematics vs. OrCAD Capture .....	9
1.9	SPICE Resources.....	10
1.9.1	Web Sites with Free SPICE Models.....	10
1.9.2	Web Sites with SPICE Models .....	11
1.9.3	SPICE and Circuit Simulation Information Sites.....	11
1.9.4	Engineering Magazines with SPICE Articles.....	12
	Suggested Reading.....	12
<b>Chapter 2</b>	<b>Circuit Descriptions.....</b>	<b>15</b>
2.1	Introduction.....	15
2.2	Input Files.....	15
2.3	Nodes .....	17
2.4	Element Values .....	17
2.5	Circuit Elements .....	19
2.6	Element Models.....	20
2.7	Sources.....	21
2.8	Output Variables .....	22
2.9	Types of Analysis .....	24
2.10	PSpice Output Commands .....	26
2.11	Format of Circuit Files.....	28
2.12	Format of Output Files.....	29
2.13	Examples of PSpice Simulations .....	30
2.13	PSpice Schematics.....	41
2.13.1	PSpice Schematics Layout .....	41
2.13.2	PSpice A/D .....	43
2.13.3	Probe.....	43

2.14	Importing Microsim Schematics in OrCAD Capture.....	45
	Suggested Reading.....	50
	Problems.....	50
<b>Chapter 3</b> Defining Output Variables .....		<b>53</b>
3.1	Introduction.....	53
3.2	DC Sweep and Transient Analysis.....	53
3.2.1	Voltage Output.....	53
3.2.2	Current Output.....	55
3.2.3	Power Output.....	56
3.3	AC Analysis.....	59
3.3.1	Voltage Output.....	59
3.3.2	Current Output.....	59
3.4	Output Markers.....	61
3.5	Noise Analysis.....	61
3.6	Summary.....	62
<b>Chapter 4</b> Voltage and Current Sources.....		<b>65</b>
4.1	Introduction.....	65
4.2	Sources Modeling.....	65
4.2.1	Pulse Source .....	65
4.2.1.1	Typical Statements .....	67
4.2.2	Piecewise Linear Source .....	67
4.2.2.1	Typical Statement.....	68
4.2.3	Sinusoidal Source .....	68
4.2.3.1	Typical Statements .....	69
4.2.4	Exponential Source.....	70
4.2.4.1	Typical Statements .....	71
4.2.5	Single-Frequency Frequency Modulation Source.....	71
4.2.5.1	Typical Statements .....	72
4.3	Independent Sources.....	73
4.3.1	Independent Voltage Source .....	73
4.3.1.1	Typical Statements .....	74
4.3.2	Independent Current Source.....	74
4.3.2.1	Typical Statements .....	75
4.3.3	Schematic Independent Sources.....	75
4.4	Dependent Sources .....	75
4.4.1	Polynomial Source.....	75
4.4.1.1	Typical Model Statements.....	78
4.4.2	Voltage-Controlled Voltage Source .....	78
4.4.2.1	Typical Statements .....	79
4.4.3	Current-Controlled Current Source.....	79
4.4.3.1	Typical Statements .....	80

4.4.4	Voltage-Controlled Current Source .....	80
4.4.4.1	Typical Statements .....	80
4.4.5	Current-Controlled Voltage Source .....	81
4.4.5.1	Typical Statements .....	82
4.4.6	Schematic Dependent Sources .....	82
4.5	Behavioral Device Modeling.....	82
4.5.1	VALUE .....	84
4.5.1.1	Typical Statements .....	85
4.5.2	TABLE.....	86
4.5.2.1	Typical Statements .....	86
4.5.3	LAPLACE .....	87
4.5.3.1	Typical Statements .....	87
4.5.4	FREQ.....	87
4.5.4.1	Typical Statements .....	88
	Summary .....	88
	Suggested Reading.....	89
	Problems.....	90
 <b>Chapter 5</b> Passive Elements .....		<b>95</b>
5.1	Introduction.....	95
5.2	Modeling of Elements .....	95
5.2.1	Some Model Statements.....	97
5.3	Operating Temperature .....	98
5.3.1	Some Temperature Statements .....	98
5.4	RLC Elements .....	98
5.4.1	Resistor .....	98
5.4.1.1	Some Resistor Statements.....	101
5.4.2	Capacitor.....	101
5.4.2.1	Some Capacitor Statements .....	102
5.4.3	Inductor.....	102
5.4.3.1	Some Inductor Statements .....	104
5.5	Magnetic Elements and Transformers .....	106
5.5.1	Linear Magnetic Circuits.....	107
5.5.2	Nonlinear Magnetic Circuits .....	111
5.6	Lossless Transmission Lines .....	119
5.7	Switches.....	119
5.7.1	Voltage-Controlled Switch .....	121
5.7.2	Current-Controlled Switch .....	124
5.7.3	Time-Dependent Switches.....	127
5.7.3.1	Time-Dependent Close Switch .....	128
5.7.3.2	Time-Dependent Open Switch.....	128
	Summary .....	128
	Suggested Reading.....	131
	Problems.....	131

<b>Chapter 6</b>	<b>Dot Commands</b> .....	137
6.1	Introduction.....	137
6.2	Models.....	137
6.2.1	.MODEL (Model).....	138
6.2.2	.SUBCKT (Subcircuit).....	138
6.2.3	.ENDS (End of Subcircuit).....	139
6.2.4	.FUNC (Function).....	140
6.2.5	.GLOBAL (Global).....	141
6.2.6	.LIB (Library File).....	142
6.2.7	.INC (Include File).....	143
6.2.8	.PARAM (Parameter).....	144
6.2.9	.STEP (Parametric Analysis).....	145
6.3	Types of Output.....	147
6.3.1	.PRINT (Print).....	148
6.3.2	.PLOT (Plot).....	148
6.3.3	.PROBE (Probe).....	149
	Probe Statements.....	150
6.3.4	Probe Output.....	150
6.3.5	.WIDTH (Width).....	154
6.4	Operating Temperature and End of Circuit.....	154
6.5	Options.....	155
6.6	DC Analysis.....	156
6.6.1	.OP (Operating Point).....	158
6.6.2	.NODESET (Nodeset).....	158
6.6.3	.SENS (Sensitivity Analysis).....	159
6.6.4	.TF (Small-Signal Transfer Function).....	162
6.6.5	.DC (DC Sweep).....	165
6.7	AC Analysis.....	170
6.8	Noise Analysis.....	174
6.9	Transient Analysis.....	178
6.9.1	.IC (Initial Transient Conditions).....	178
6.9.2	.TRAN (Transient Analysis).....	179
6.10	Fourier Analysis.....	183
6.11	Monte Carlo Analysis.....	186
6.12	Sensitivity and Worst-Case Analysis.....	192
	Summary.....	195
	Suggested Reading.....	195
	Problems.....	196

<b>Chapter 7</b>	<b>Diode Rectifiers</b> .....	201
7.1	Introduction.....	201
7.2	Diode Model.....	201
7.3	Diode Statement.....	204

7.4	Diode Characteristics.....	204
7.5	Diode Parameters.....	206
	7.5.1 Modeling Zener Diodes.....	210
	7.5.2 Tabular Data .....	211
7.6	Diode Rectifiers.....	214
7.7	Laboratory Experiments .....	234
	7.7.1 Experiment DR.1 .....	234
	Single-Phase Full-Wave Center-Tapped Rectifier.....	234
	7.7.2 Experiment DR.2.....	235
	Single-Phase Bridge Rectifier .....	235
	7.7.3 Experiment DR.3.....	236
	Three-Phase Bridge Rectifier .....	236
7.8	Summary.....	237
	Suggested Reading.....	237
	Design Problems .....	237

**Chapter 8 DC–DC Converters..... 241**

8.1	Introduction.....	241
8.2	DC Switch Chopper .....	241
8.3	BJT SPICE Model.....	245
8.4	BJT Parameters.....	248
8.5	Examples of BJT Choppers .....	253
8.6	MOSFET Choppers.....	262
8.7	MOSFET Parameters.....	267
8.8	Examples of MOSFET Choppers .....	274
8.9	IGBT Model .....	276
8.10	Laboratory Experiment.....	281
	8.10.1 Experiment TP.1 .....	281
	DC Buck Chopper .....	281
	8.10.2 Experimental TP-2.....	283
	DC Boost Chopper .....	283
8.11	Summary.....	283
	Suggested Reading.....	284
	Design Problems .....	285

**Chapter 9 Pulse-Width-Modulated Inverters..... 289**

9.1	Introduction.....	289
9.2	Voltage-Source Inverters .....	289
9.3	Current-Source Inverters .....	311
9.4	Laboratory Experiments .....	318
	9.4.1 Experiment PW.1 .....	318
	Single-Phase Half-Bridge Inverter .....	318

9.4.2	Experiment PW.2.....	319
	Single-Phase Full-Bridge Inverter.....	319
9.4.3	Experiment PW.3.....	319
	Single-Phase Full-Bridge Inverter with PWM Control.....	319
9.4.4	Experiment PW.4.....	320
	Single-Phase Full-Bridge Inverter with SPWM Control.....	320
9.4.5	Experiment PW.5.....	320
	Three-Phase Bridge Inverter.....	320
9.4.6	Experiment PW.6.....	321
	Single-Phase Current-Source Inverter.....	321
9.4.7	Experiment PW.7.....	322
	Three-Phase Current-Source Inverter.....	322
	Summary.....	324
	Suggested Reading.....	324
	Design Problems.....	324
<b>Chapter 10 Resonant-Pulse Inverters.....</b>		<b>329</b>
10.1	Introduction.....	329
10.2	Resonant-Pulse Inverters.....	329
10.3	Zero-Current Switching Converters (ZCSC).....	336
10.4	Zero-Voltage Switching Converter (ZVSC).....	341
10.5	Laboratory Experiments.....	345
10.5.1	Experiment RI.1.....	345
	Single-Phase Half-Bridge Resonant Inverter.....	345
10.5.2	Experiment RI.2.....	346
	Single-Phase Full-Bridge Resonant Inverter.....	346
10.5.3	Experiment RI.3.....	347
	Push-Pull Inverter.....	347
10.5.4	Experiment RI.4.....	347
	Parallel Resonant Inverter.....	347
10.5.5	Experiment RI.5.....	348
	ZCSC.....	348
10.5.6	Experiment RI.6.....	349
	ZVSC.....	349
10.6	Summary.....	350
	Suggested Reading.....	350
	Design Problems.....	350
<b>Chapter 11 Controlled Rectifiers.....</b>		<b>355</b>
11.1	Introduction.....	355
11.2	AC Thyristor Model.....	355
11.3	Controlled Rectifiers.....	364
11.4	Examples of Controlled Rectifiers.....	364
11.5	Switched Thyristor DC Model.....	388

11.6	GTO Thyristor Model .....	389
11.7	Example of Forced-Commutated Rectifiers.....	389
11.8	Laboratory Experiments .....	402
11.8.1	Experiment TC.1 .....	403
	Single-Phase Half-Wave Controlled Rectifier .....	403
11.8.2	Experiment TC.2 .....	404
	Single-Phase Full-Wave Controlled Rectifier .....	404
11.8.3	Experiment TC.3 .....	405
	Three-Phase Full-Wave Controlled Rectifier .....	405
	Summary .....	405
	Suggested Reading .....	406
	Design Problems .....	406
<b>Chapter 12</b>	<b>AC Voltage Controllers .....</b>	<b>411</b>
12.1	Introduction.....	411
12.2	AC Thyristor Model .....	411
12.3	AC Voltage Controllers .....	412
12.4	Examples of AC Voltage Controllers .....	412
12.5	Laboratory Experiments .....	437
12.5.1	Experiment AC.1 .....	437
	Single-Phase AC Voltage Controller .....	437
12.5.2	Experiment AC.2 .....	439
	Three-Phase AC Voltage Controller .....	439
12.6	Summary.....	440
	Suggested Reading .....	440
	Design Problems .....	440
<b>Chapter 13</b>	<b>Control Applications.....</b>	<b>443</b>
13.1	Introduction.....	443
13.2	Op-Amp Circuits .....	443
13.2.1	DC Linear Models.....	444
13.2.2	AC Linear Models.....	444
13.2.3	Nonlinear Macromodels .....	445
13.3	Control Systems .....	456
13.4	Signal Conditioning.....	462
13.5	Closed-Loop Current Control .....	472
	Suggested Reading .....	480
	Problems.....	480
<b>Chapter 14</b>	<b>Characteristics of Electrical Motors.....</b>	<b>483</b>
14.1	Introduction.....	483
14.2	DC Motor Characteristics .....	483
14.3	Induction Motor Characteristics.....	490

Suggested Reading.....	494
Problems.....	495

**Chapter 15 Simulation Errors, Convergence Problems, and Other Difficulties ..... 497**

15.1 Introduction.....	497
15.2 Large Circuits .....	497
15.3 Running Multiple Circuits.....	498
15.4 Large Outputs .....	498
15.5 Long Transient Runs .....	498
15.6 Convergence .....	499
15.6.1 DC Sweep.....	499
15.6.2 Bias-Point Calculation.....	501
15.6.3 Transient Analysis .....	504
15.7 Analysis Accuracy.....	505
15.8 Negative Component Values .....	506
15.9 Power Switching Circuits.....	507
15.9.1 Model Parameters of Diodes and Transistors.....	507
15.9.2 Error Tolerances .....	508
15.9.3 Snubbing Resistor.....	508
15.9.4 Quasi-Steady-State Condition .....	508
15.10 Floating Nodes .....	512
15.11 Nodes with Fewer than Two Connections .....	516
15.12 Voltage Source and Inductor Loops.....	517
15.13 Running PSpice Files on Spice.....	518
15.14 Running Spice Files on PSpice.....	518
15.15 Using Earlier Version of Schematics .....	519
Suggested Reading.....	520
Problems.....	520

**Appendix A Running PSpice on PCs ..... 523**

A.1 Installing PSpice Software in PCs .....	523
A.2 Creating Input Circuit Files .....	524
A.3 Running DOS Commands.....	526
A.4 PSpice Default Symbol Libraries.....	528

**Bibliography..... 531**

**Index..... 533**